

① Phys 1402 2014-01-18


$$V = IR$$

$$P = IV$$

Series: $I = I_1 = I_2 = \dots$

$$V_{\text{Tot}} = V_1 + V_2 + \dots$$


$$R_{\text{eq}} = R_1 + R_2 + \dots$$

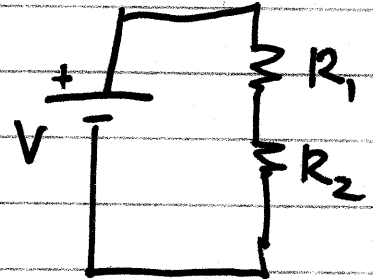


Parallel: $I_{\text{tot}} = I_1 + I_2 + \dots$

$$V = V_1 = V_2 = \dots$$
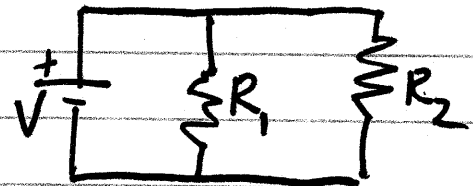
$$R_{\text{eq}} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots \right)^{-1}$$



Parallel Example:

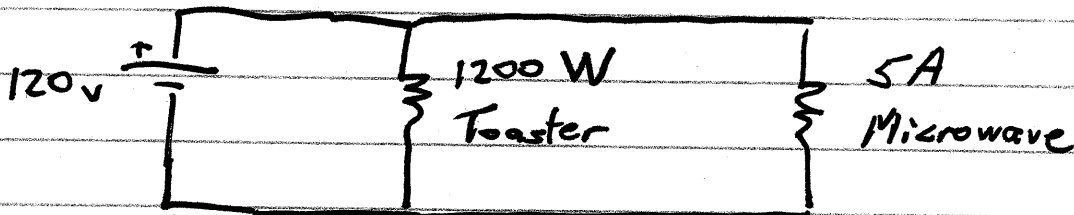

	V	I	R	P
Toaster	120 V	10 A	12 Ω	1200 W
Microwave	120 V	5 A	24 Ω	600 W
Total	120 V	15 A	8 Ω	1800 W

$$\frac{120 \text{ V}}{15 \text{ A}} = 8 \Omega$$

$$\left(\frac{1}{12} + \frac{1}{24} \right)^{-1} = 8 \Omega$$

②

Electrical Measurements

Basic Needs for all measurement:


- Our meter must share the same measurement value as the subject.
- The measurement should not disturb the system.

Voltage: In parallel $V = V_1 = V_2 = V_3 = \dots$


- Hook up voltmeter in parallel.

$$I_{tot} = I_1 + I_2 + I_{meter}$$

- Voltmeter has zero current.

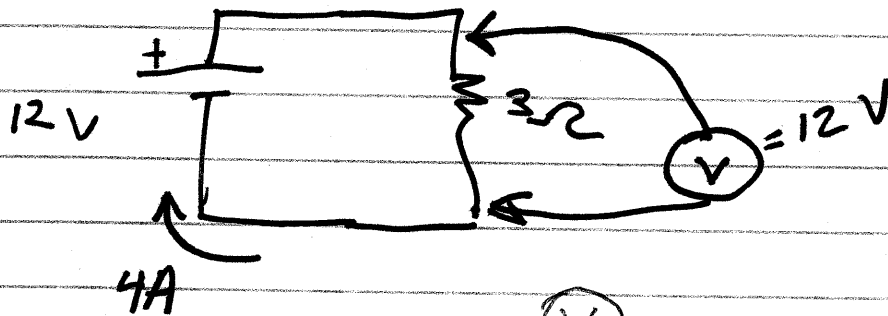

what if:

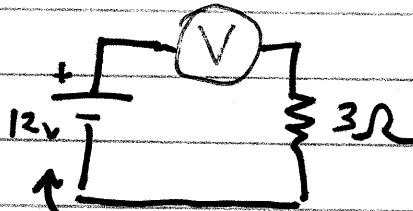

Incorrect Hookup

$$I \approx 0$$

$$V_R = IR = 0 \text{ V}$$


$$V_{Tot} = V_1 + V_2$$

$$12 \text{ V} = V_{meter} + (0 \text{ V})$$

$$V_{meter} = 12 \text{ V} = \text{Battery voltage w/ no current.}$$



③

Measuring voltage of a series circuit

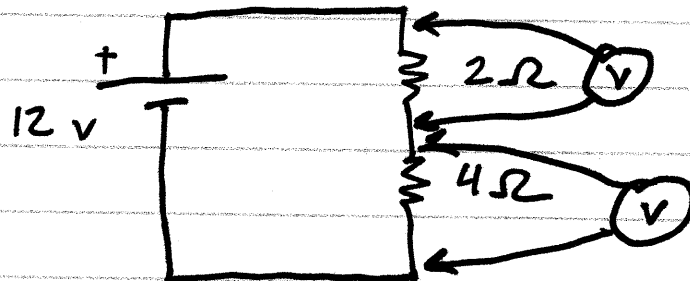

	V	I	R
R_1	4V	2A	2Ω
R_2	8V	2A	4Ω
Tot	12V	2A	6Ω

Note: In series, bigger R gets more V.

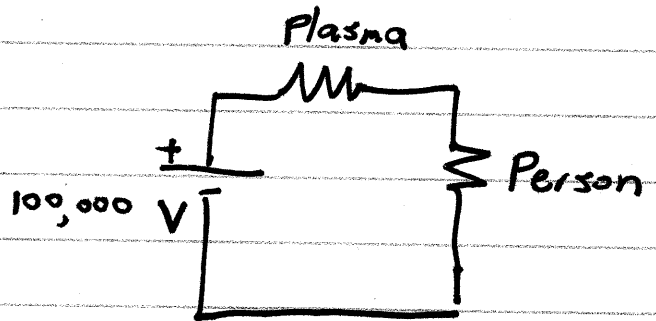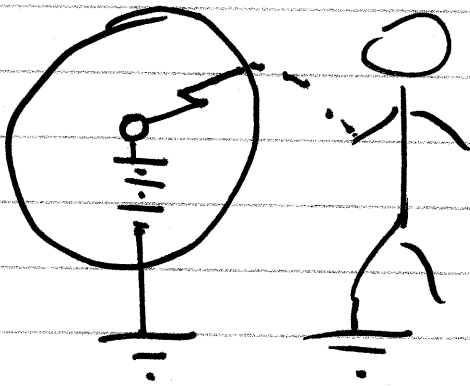

$$V_{\text{tot}} = V_1 + V_2$$
$$100000\text{ V} = V_{\text{plasma}} + V_{\text{person}}$$

4

Measuring Current

- Want same current in meter and device.


$$I = I_1 = I_2 = \dots \text{ in series}$$

Hook meter in series.



- Want to not disturb the system.

$$R_{net} = R_1 + R_2 + R_{meter} + \dots$$

Meter has almost zero resistance.

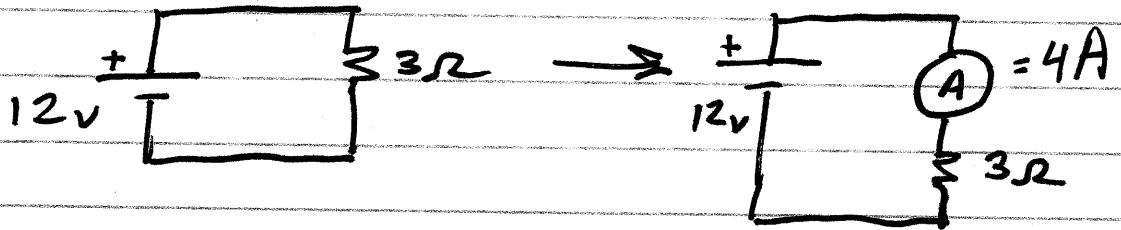

What If:

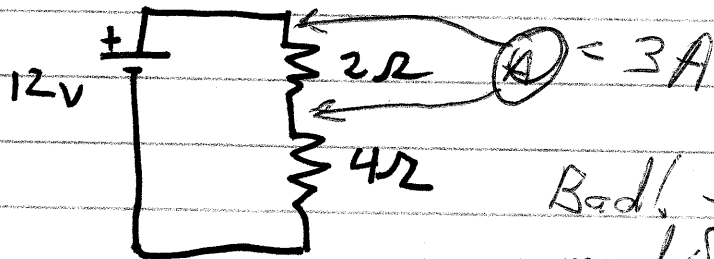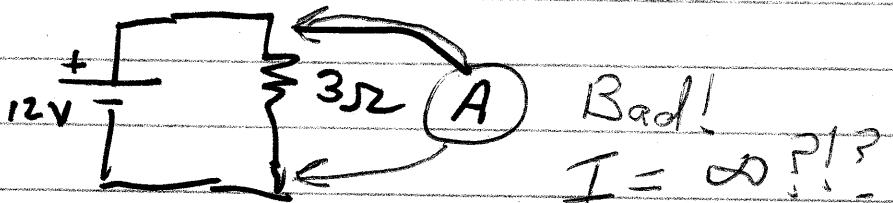


Bad! System modified,

without meter, $I = 2 A$

5

Measuring Resistance

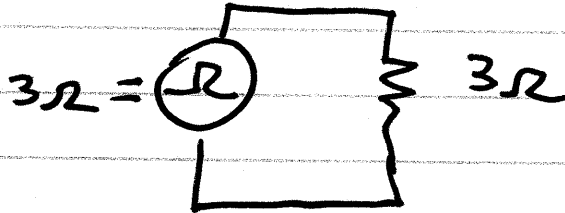- Meter provides V , measures I , calculates R .



Measuring Power

- Need Both I and V

