

① Phys 1402 2014-09-23

Total Amount vs. Rate

Charge $\Delta Q = I \Delta t$

Energy $\text{Energy} = P \Delta t$

Power P in watts ($1 \text{ W} = 1 \text{ J/s}$)

Electric power $P = IV$

IF P in kW and Δt in hours:

Energy in kWh

$$P = 100 \text{ W} = 0.1 \text{ kW}$$


Ex: A bulb for a month

$$\begin{aligned} \text{Energy} &= (0.1 \text{ kW})(720 \text{ hours}) \\ &= 72 \text{ kWh} \end{aligned}$$

$$(72 \text{ kWh}) \cdot (\$0.12/\text{kWh}) = \$8.64$$


②

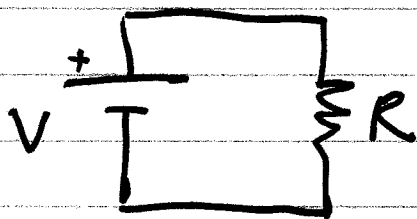What happens when you hook a battery to a resistor?



Current $I = \frac{V}{R}$
is constant.

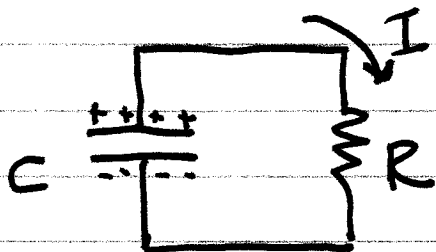What happens if you hook a charged capacitor to a resistor?



$$V_c = Q/C$$

$$C = \frac{\epsilon_0 \epsilon_r A}{d}$$

Current Flows $I = \frac{V_c}{R}$


V_{batt} is steady.

V_c varies depending on Q .


As I flows, Q decreases.

As Q drops, V_c decreases.


As V_c decreases, I decreases.

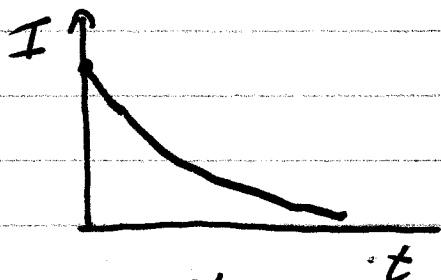

$$I = I_0 e^{-t/\tau}$$

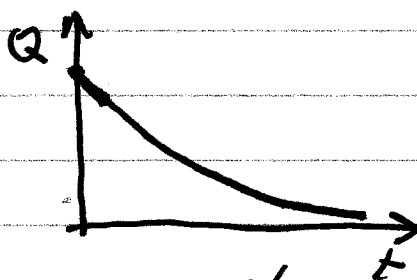
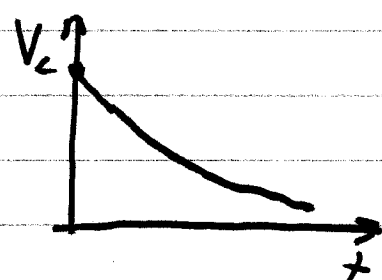
$$Q = Q_0 e^{-t/\tau} \\ = Q_0 \exp(-t/\tau)$$



$$V = V_0 e^{-t/\tau}$$

③

Ex: $\tau = 5\text{ s}$ $V_0 = 100\text{ V}$

$t\text{ (s)}$	$V\text{ (V)} = V_0 e^{-t/\tau}$	
0	$V_0 e^{-0} = V_0 = 100$	} Lost 18V
1	$(100) e^{-1/5} = (100)(0.82) = 82$	
2	$(100) e^{-2/5} = \quad = 67$	} Lost 15V
...		
$5 = \tau$	$(100) e^{-1} = 100/e = 37$	
...		
...	(when $\tau = t$, $V/V_0 = 0.37$)	
...		
10	$\quad = 14$	

N.b. $14 = 37\%$ of 37

$$e^{-2} = (e^{-1})(e^{-1}) = (0.37)(0.37)$$

Every τ , V gets cut to 37% of what it was at the last checkpoint.

When does V get cut in half?

$$V = V_0 e^{-t/\tau} = V_0 (0.5)$$

$$e^{-t/\tau} = 0.5 \quad \ln() \text{ both sides}$$

$$-t/\tau = \ln(0.5)$$

$$t = -\tau \ln(0.5) = 0.693\tau = \lambda_{1/2}$$


4

How big is τ ?


$$\tau = RC$$

Bigger R drains slower

Bigger C needs more draining.

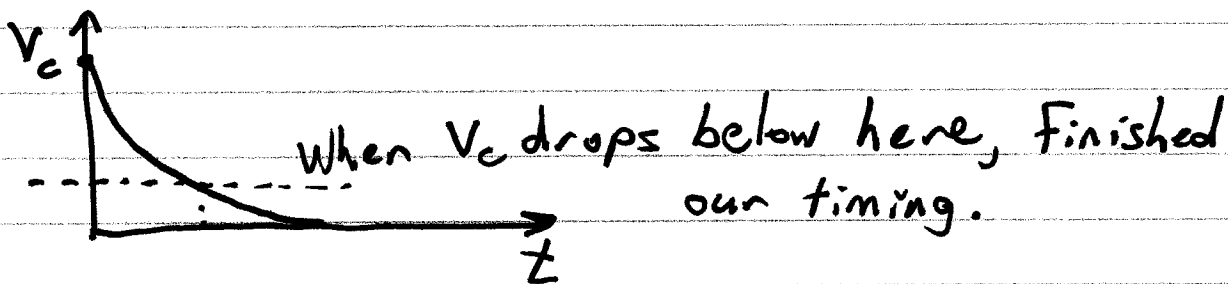


How do we charge a capacitor?

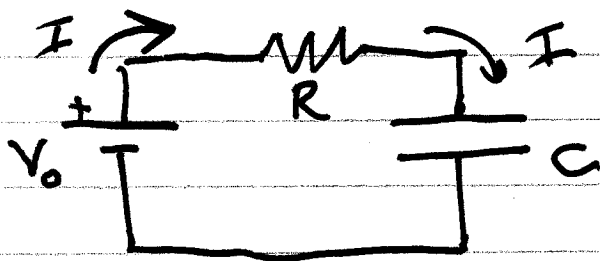


$$V_0 = V_R + V_C$$

	Initial	Then...	... Eventually
Q	$Q = 0$	Q increases	Q is max
V_C	$V_C = 0$	V_C increases	$V_C = V_0$
V_0	V_0	V_0	V_0
V_R	$V_R = V_0$	V_R decreases	$V_R = IR = 0$
I	$I_0 = \frac{V_0}{R}$	I decreases	$I = 0$


5

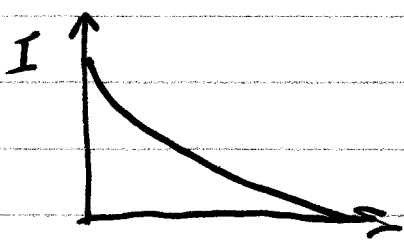

$$I = I_0 e^{-t/\tau}$$

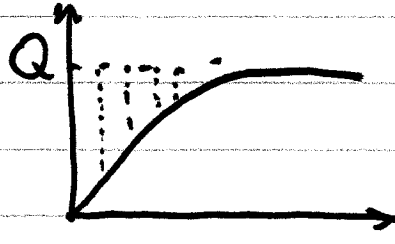

$$Q_0 - Q = Q_0 e^{-t/\tau}$$

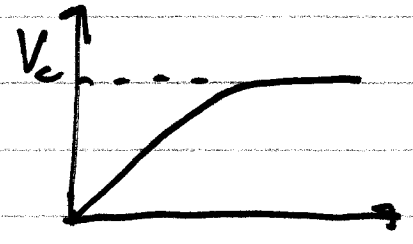

$$V_0 - V = V_0 e^{-t/\tau}$$

Q exponentially approaches Q_0
 V " " " V_0

Summary

Current

$$I = I_0 e^{-t/\tau}$$

Voltage

$$V = V_0 e^{-t/\tau}$$

$$V = V_0 (1 - e^{-t/\tau})$$

Starts @ V_0
 Ends @ 0
 Discharge


Starts @ 0
 Ends @ V_0
 Charge

$$I_0 = V_0 / R$$

$$Q = CV$$

$$\tau = RC$$

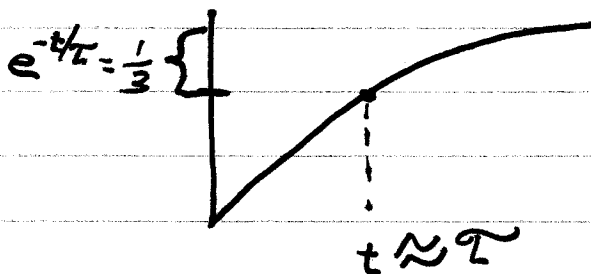$e^{-t/\tau}$ is the fraction of the process remaining.



6

Out of 20Ω and 50Ω R's,
what can you build?

