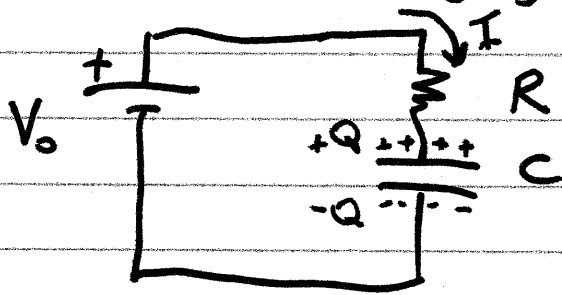


Phys 1402 2014-09-25

Exam 1: Tue 9/30

- I will provide the posted Eqn Sheet.
- Covers chap 15-18
- Review all HW questions
- Review all Prelab Practice
- Review Summer 2014 Exam 1.

HW 2 #22 : Charging Capacitor



$$V_0 = V_R + V_C$$

$$I = \frac{V_R}{R}$$

$$Q = CV_C$$

$$I = I_0 e^{-t/\tau}$$

$$\tau = RC$$

Initially: $Q = 0$ so $V_C = 0$ and $V_R = V_0$

So the current starts at $I_0 = \frac{V_0}{R}$

Finally: $I = 0$ so $V_R = 0$ and $V_C = V_0$

So, the capacitor charges to


$$Q_0 = CV_0 = (6.00 \times 10^{-6} \text{ F})(35.0 \text{ V})$$

②

① $t = 10.0 \text{ s}$

$$I = I_0 e^{-t/\tau}$$
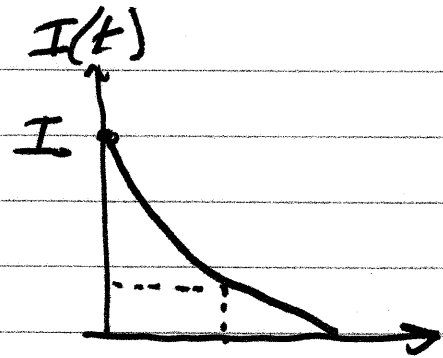
$$I_0 = \frac{V_0}{R} = \frac{(35.0 \text{ V})}{(9 \times 10^5 \Omega)}$$



Step-by-step: $-t/\tau$, press e^x ,
mult by I_0

HW2 #5

$$Q = I \Delta t = \text{charge capacity in C or A}\cdot\text{h}$$

Note $1 \text{ C} = 1 \text{ A}\cdot\text{s}$

$$\text{Energy} = V \cdot Q$$

$$P = IV$$

Ex: $V = 9.0 \text{ V}$

$$Q = 15 \text{ A}\cdot\text{h}$$

$$W$$

$$\begin{aligned} \text{Energy} &= (9.0 \text{ V}) \cdot (15 \text{ A}\cdot\text{h}) = 135 \text{ V}\cdot\text{A}\cdot\text{h} \\ &= 135 \text{ W}\cdot\text{h} = 0.135 \text{ kWh} \end{aligned}$$

A capacitor is hooked to a 6.0 V battery and its charge is 3 mC. If the same cap is hooked to a 12.0 V batt, what is the capacitance? $V_c = Q/C$ $Q = V_c C$

- (A) 4 mF (B) 2 mF (C) 0.5 mF (D) 0.25 mF

Note: Before, $C = 3 \text{ mC} / 6 \text{ V} = 0.5 \text{ mF}$


③

If you double the current going thru a resistor, what happens to R ?

$$V = IR$$

(Ans: R doesn't change)

Multiple equiv. R in parallel:

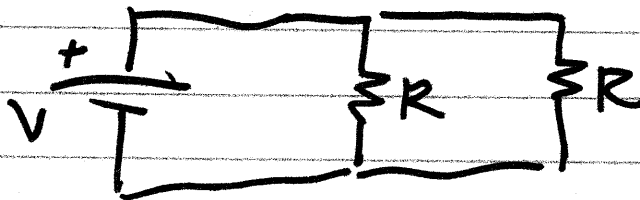

$$\text{Each } I = \frac{V}{R} \quad \# \text{ resistors}$$

$$\text{Total } I_{\text{tot}} = NI$$

$$\text{Equiv Resistance } R_{\text{eq}} = \frac{V}{I_{\text{tot}}} = \frac{V}{NI} = \frac{R}{N}$$

Ex: Three 60Ω in parallel $R_{\text{eq}} = 20\Omega$

④

HW 2 #23 Charging, Capacitor

$$V = V_0 (1 - e^{-t/\tau}) \quad \tau = RC$$

↑
V @ time t

↑
Equilibrium Voltage

$$-\frac{V}{V_0} = -1 + e^{-t/\tau}$$

$$1 - \frac{V}{V_0} = e^{-t/\tau}$$

↑ plug #'s in $m = 1 - V/V_0$

$$\ln(m) = -t/\tau$$

↑ solve for τ

Plug τ into $\tau = RC$

Strategy:

- 1) Solve for $e^{-t/\tau}$
- 2) Plug in known values
- 3) Take $\ln()$ if necessary
- 4) Finish solving.

5

A capacitor is discharging.

$$\begin{array}{l} \text{(a) } t=0, \quad V=60 \text{ V} \\ \text{(b) } t=8 \text{ s}, \quad V=15 \text{ V} \end{array} \left. \vphantom{\begin{array}{l} \text{(a) } t=0, \quad V=60 \text{ V} \\ \text{(b) } t=8 \text{ s}, \quad V=15 \text{ V} \end{array}} \right\} \text{cut in half twice.}$$

What is V @ $t=4 \text{ s}$?

What is τ ?

$$V = V_0 e^{-t/\tau}$$

$$(15 \text{ V}) = (60 \text{ V}) e^{-t/\tau}$$

$$0.25 = e^{-t/\tau}$$

$$\ln(0.25) = -t/\tau = -1.386$$

$$\tau = -t / -1.386$$

$$\tau = 5.77 \text{ s}$$

Plug in $t=8 \text{ s}$