

① Phys 1402 2014-10-16

Mass Spec

$$F = ma$$
$$qvB = mv^2/R$$

$$R = \frac{mv}{qvB}$$

Conversion by substitution

$$5 \times 10^{-5} T = 50 \times 10^{-6} T$$
$$= 50 \mu T$$

Induced Voltages

Faraday's Law $\mathcal{E} = -\frac{\Delta \Phi_B}{\Delta t}$

Magnetic Flux $\Phi_B = NBA \cos \theta$

Inductor: any coil

$$I \rightarrow B \rightarrow \Phi_B \xrightarrow{\text{change}} \mathcal{E} = \text{Voltage}$$

Net result:

$$V = -L \frac{\Delta I}{\Delta t}$$

L = inductance in henries (H)

(2)

Ex: Solenoid coil

magnetic field $B = \mu_0 I N / l$

flux

$$\Phi_B = NBA = \mu_0 I N^2 A / l$$

Change in flux $\Delta \Phi_B = (\mu_0 N^2 A / l) \Delta I$

L

Once the inductor is built, $L = \text{const.}$

The inductor opposes any change in current.


- First plug it in - takes time to get going.
- Try to disconnect - jolt of voltage tries to keep current flowing.
Most motors have a "condenser capacitor" to absorb this jolt.

- Once current is flowing, the inductor is happy and doesn't oppose it.

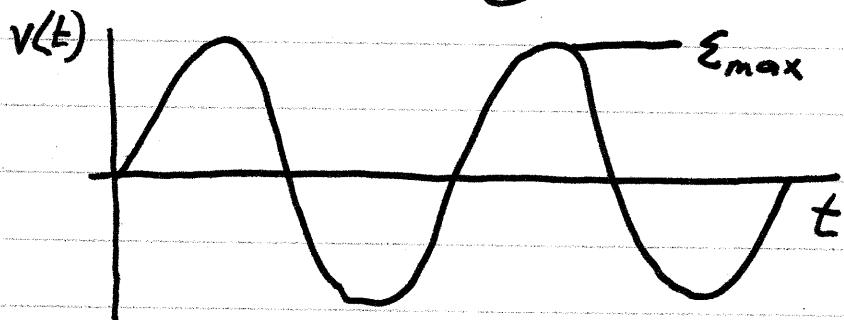(3)

Generators produce a varying voltage.

$$E_{\max} = NBA \omega \text{ rotation in rad/s}$$



If you hook $E_{\max} = 12 \text{ V}$ to a light bulb,
 Sometimes $V(t) = \pm 12 \text{ V} \Rightarrow \text{Bright}$
 other times $V(t) \approx 0 \text{ V} \Rightarrow \text{Dim}$

Average brightness corresponds to a smaller battery.

$$V_{\text{RMS}} = \frac{V_{\max}}{\sqrt{2}} = 0.707 V_{\max}$$


Ex: Want 14 V max voltage. What RMS?

$$V_{\text{RMS}} = \frac{(14 \text{ V})}{\sqrt{2}} = 9.9 \text{ V}$$

In one analysis, stick to either RMS or max.

(4)

Transformers

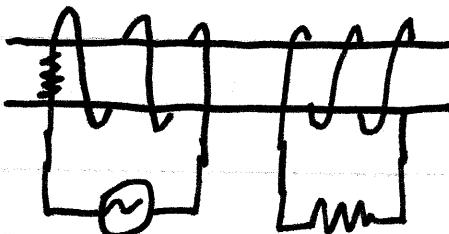

First coil: Primary


$$\frac{dI}{dt} \rightarrow \frac{\Delta B}{\Delta t} \rightarrow \frac{\Delta \Phi_1}{\Delta t} \rightarrow V_1$$

Second Coil: Secondary

$$\frac{\Delta \Phi_2}{\Delta t} \rightarrow V_2$$

The only difference between the coils is N_1 vs. N_2 . This scales the voltages.

Ex:

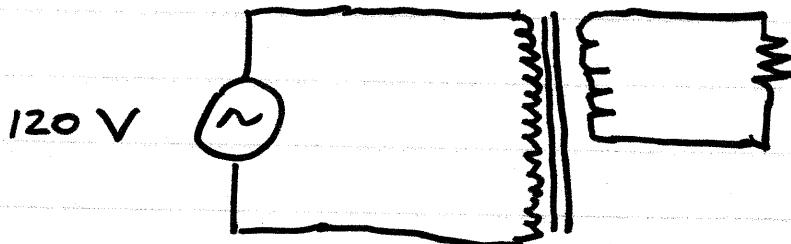

$$N_1 = 240$$

$$N_2 = 20$$

$$\frac{N_2}{N_1} = \frac{V_2}{V_1}$$

Turns ratio (pri : sec) = 12:1

Voltage ratio is also 12:1

$$V_2 = \frac{N_2}{N_1} V_1 = \frac{1}{12} (120V) = 10V$$

(5)


Transformers don't create energy

For resistor-type loads $P_{ave} = V_{RMS} I_{RMS}$

For a transformer

$$P_{in} = P_{out}$$


$$V_1 I_1 = V_2 I_2$$

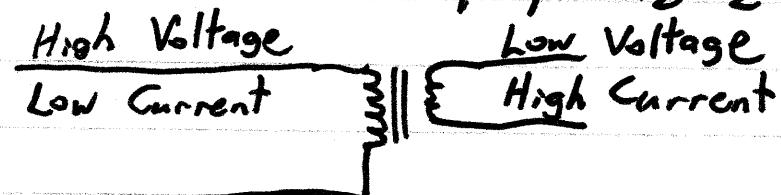

The power lines are resistors.

$$P_{lost} = V_R I_R = I^2 R$$

lower I means less lost power.

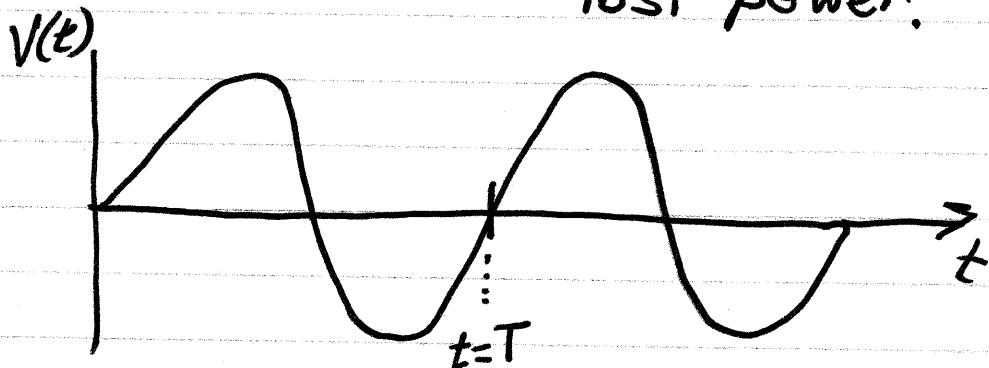

$$V(t) = V_{max} \sin(2\pi ft)$$

f=frequency in hertz (Hz)

= #cycles per second.

T=period in seconds.

= time of one cycle

$$T = \frac{1}{f}$$

In US Power systems, f= 60 Hz.


⑥

How do the basic components deal w/ AC?

Resistor: Same as DC.

$$V_R = IR$$

Inductor: Opposes changing I.

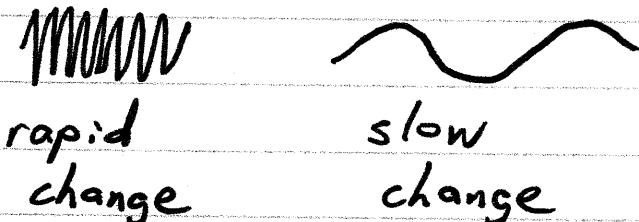

High-f Low-f

More V_L Less V_L

$$V_L = I 2\pi f L = I Z_L$$

Z = impedance (or X = reactance)
in ohms.

¶ Inductor blocks High-f
allows Low-f (and DC)

Capacitor: opposite of inductor

$$V_C = I \left(\frac{1}{2\pi f C} \right) = I Z_C$$