


Phys 1402 2014-10-23

## Power and Energy in AC

Resistor - Can only use power.  
Does not store energy.

$$\text{Power} = \frac{\text{Energy}}{\text{Time}} = \frac{\text{Energy}}{\text{Charge}} \frac{\text{Charge}}{\text{Time}}$$

$$P = VI$$

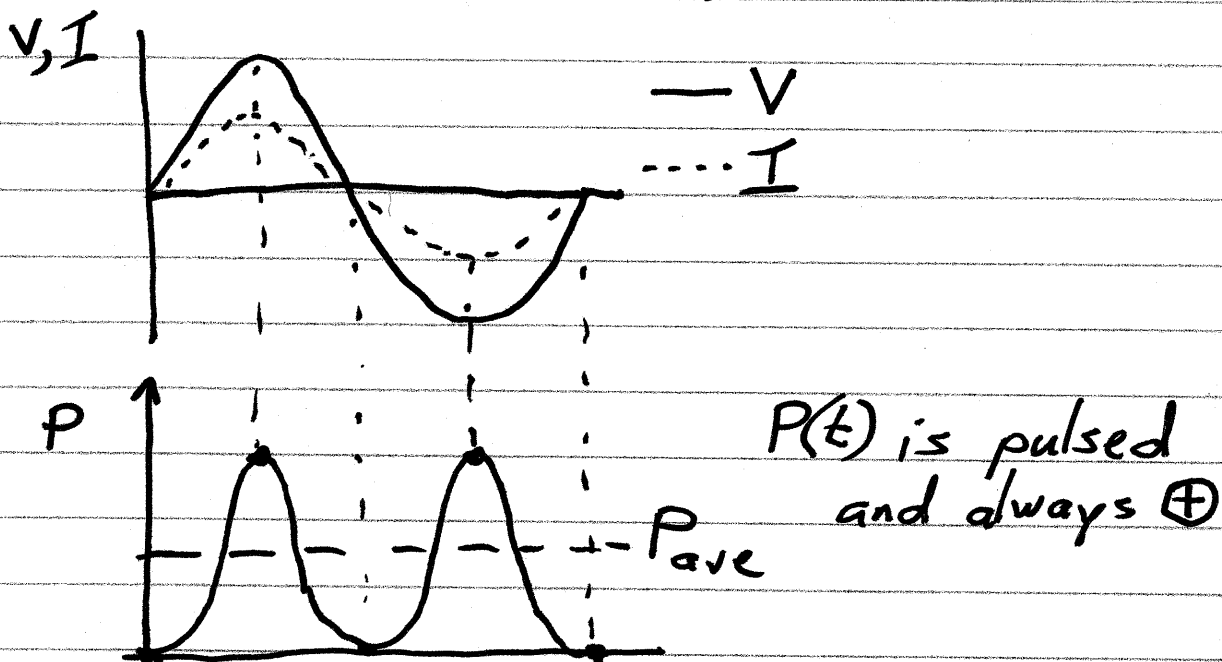

$$P_{ave} = V_{RMS} I_{RMS} \quad (\text{For a resistor})$$

$$P_{ave} = \frac{1}{2} P_{max}$$

Only resistors use power in AC.

②

What about capacitors?  $\frac{1}{2} CV^2$

Capacitors store energy.

- It takes power & time to build up the energy.
- But the energy is released as power for a time.
- The power is sometimes  $\oplus$ , sometimes  $\ominus$ .

(How?  $V = V_0 \sin(\omega t)$ )

$$I = I_0 \cos(\omega t)$$

$$P = V_0 I_0 \sin(\omega t) \cos(\omega t)$$

$$= V_0 I_0 \sin(2\omega t) \left(\frac{1}{2}\right)$$

For a capacitor  $P_{ave} = 0$

What about inductors?

Inductors store energy.  $\frac{1}{2} LI^2$

For an inductor  $P_{ave} = 0$

Summary: To find power used by a circuit, find the  $I$  of each  $R$ .

$$P = IV = I^2 R$$

Add for multiple  $R$ 's.

3

$$V = (120\text{V}) \sin(50\pi t)$$

$$I = I_0 \sin(50\pi t)$$

$$I(t = 0.005\text{ s}) = I_0 \sin(\underbrace{50\pi(0.005)}_{\text{in radians}})$$


Deg/Rad check:  $\sin(45) = 0.707$   
"degrees.

Inductor in AC  $V_{\text{rms}} = V_{\text{max}}/\sqrt{2}$

$$Z_L = 2\pi fL$$

$$V_{\text{rms}} = I_{\text{rms}} Z$$

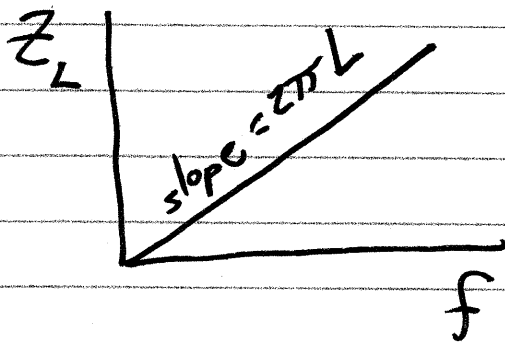Relationship between  $Z_L$  and  $f$ :  $Z \propto f$   
proportional ↗



Ⓐ 60 Hz

$$Z = 57.4\Omega$$

Ⓑ 48 Hz

$$Z = (57.4\Omega) \left(\frac{48}{60}\right) = 41.12\Omega$$

④

## Resonance

$$f_R = \frac{1}{2\pi\sqrt{LC}}$$

$$2\pi f_R = \frac{1}{\sqrt{LC}}$$

$$(2\pi f_R)^2 = \frac{1}{LC}$$

$f_R$  and  $C$  have a inverse relationship.  
(not inversely proportional)

Large  $f_R \rightarrow$  small  $C$


Small  $f_R \rightarrow$  large  $C$

A/T radio: 500 kHz - 1600 kHz

$$L = 2 \mu\text{H} \quad C_{\text{max}} = \frac{1}{(2\pi f)^2 L} = \frac{1}{(2\pi(500 \times 10^3 \text{ Hz}))^2 (2 \times 10^{-6})}$$
$$= 5.066 \times 10^{-8} \text{ F}$$
$$= 50.66 \text{ nF}$$


3

Efficiency

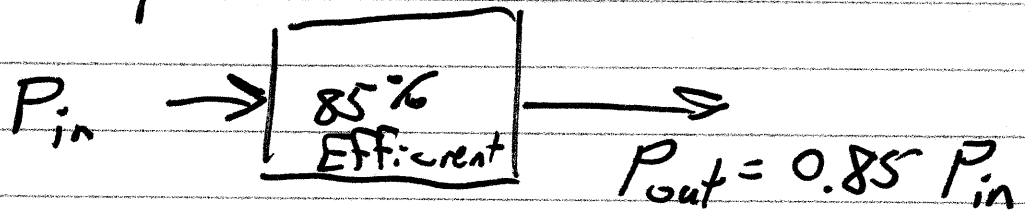

Let's say a car needs 20 BHP to drive up a hill, but the engine is only 25% efficient.

$$1 \text{ HP} = 746 \text{ W}$$

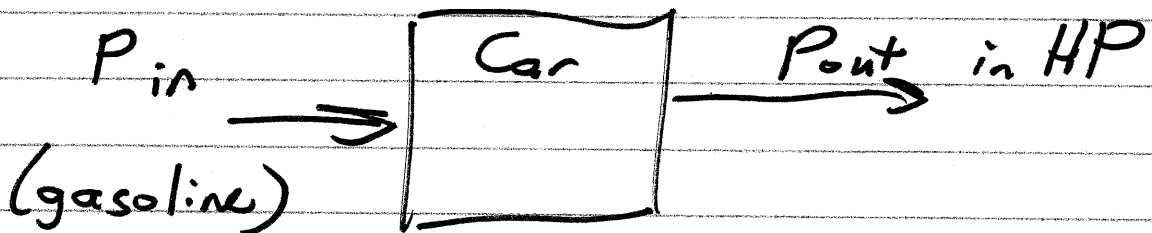

$$\begin{aligned} \text{In one hour, energy} &= P \Delta t \\ &= (20 \text{ HP}) \left( \frac{746 \text{ W}}{\text{HP}} \right) (3600 \text{ s}) \end{aligned}$$

$$= 3.43 \times 10^7 \text{ J}$$


$$= 34.3 \text{ MJ}$$

$$0.25 \left( \frac{E}{P_{in}} \right) = (34.3 \text{ MJ})$$

$$E_{in} = 137 \text{ MJ in gasoline}$$

$$120 \text{ MJ} = 1 \text{ gal gasoline equivalent}$$

6

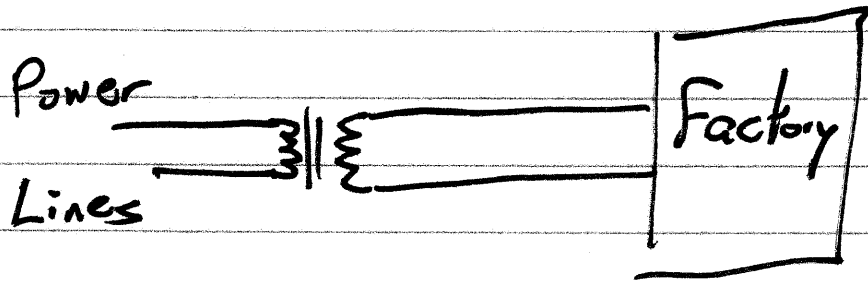

83%

2000 kW

$P_{in} = \text{more}$

$$P_{out} = \epsilon P_{in}$$
$$(2000 \text{ kW}) = (0.83) P_{in}$$

$\epsilon$  always between 0 and 1.