
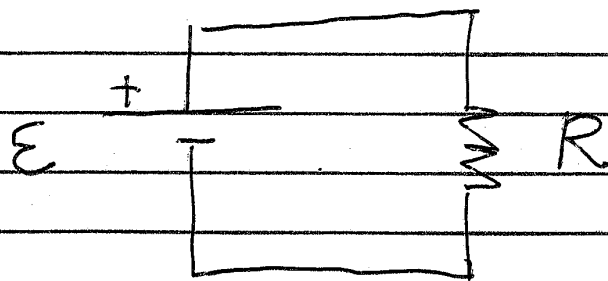


① Phys 1402 2015-09-15 Lec 6

HW2 Thu 9/24
Exam1 Tue 9/29

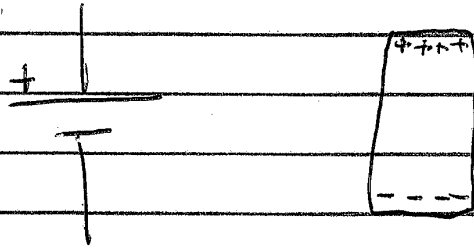

Apply a voltage \mathcal{E}
to a resistor R ,
current I flows.

Ohm's Law: $V = IR$


V = voltage across resistor (\mathcal{E} above)

R = resistance (const if Ohmic)

I = current that flows

$$I = \frac{\Delta Q}{\Delta t}$$

②

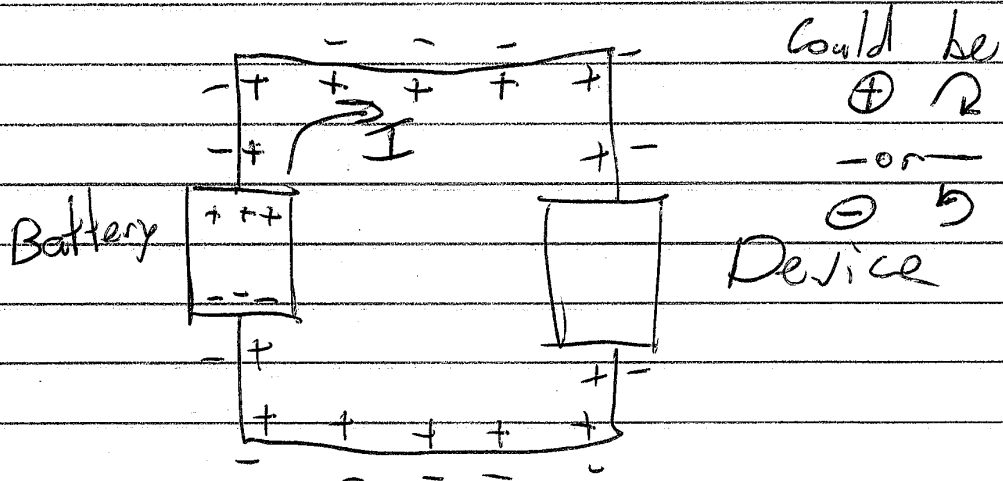


Charges are balanced.

Current is the flow of one (or the other) type of charge.

⊕ charges form current in the same dir they flow.

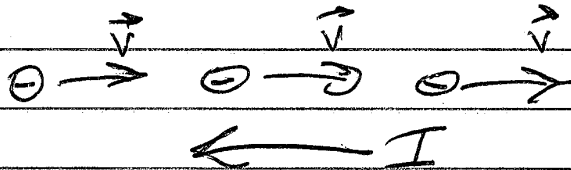
⊖ charges form current opposite to their flow.



③

Measuring Electrical Quantities

Voltage: Working Circuit

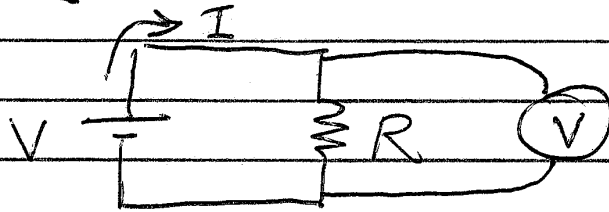


To measure V , our meter has no I .

$$V = IR_{\text{meter}}$$

Voltmeter has a huge R_{meter} .

No current flows thru voltmeter.

Current: Must break the circuit

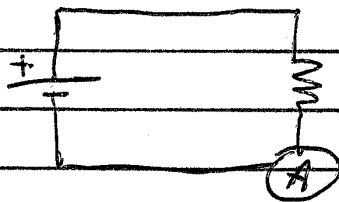

Ammeter is part
of the current path.

To measure I , our meter has no V .

$$V = IR_{\text{meter}}$$

Ammeter has tiny R_{meter} .

No voltage exists across meter.

④

Power is the flow of energy

$$P = \frac{\text{Energy}}{\Delta t} = \frac{\text{Charge}}{\Delta t} \frac{\text{Energy}}{\text{Charge}}$$

$$P = IV$$

Out of I, V, R, P , we have 2 eqns.

$$V = IR \quad P = IV$$

Ex: 60 W light bulb designed for 120 V power supply.

$$P = 60 \text{ W}$$

$$V = 120 \text{ V}$$

$$(60 \text{ W}) = (120 \text{ V}) I \Rightarrow I = 0.5 \text{ A}$$

$$(120 \text{ V}) = (0.5 \text{ A}) R \Rightarrow R = 240 \Omega$$

$$P = I^2 R = \frac{V^2}{R}$$


↑
↳ Tells us ~~the~~ power lost in a wire.

5

Physics of Flow

$$\text{Vol Flow Rate} = v A$$

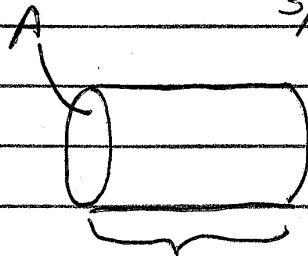(m^3/s) \uparrow speed (m/s) \downarrow cross-section Area (m^2)



$$\text{Vol} = A l$$
$$= A v \Delta t$$

$$\frac{\text{Vol}}{\Delta t} = v A$$

$$\text{Mass Flow Rate} = \rho v A$$

$\rho = \text{density, in } (\text{kg}/\text{m}^3)$

$$\text{Particle Flow Rate} = \eta v A$$

$\eta = \text{particle dens } (\#/ \text{m}^3)$

$$\text{Charge Flow Rate} = e \eta v A$$

$$I = e \eta v A$$

$$\text{Ex: } \eta = 10^{28} \text{ } \#/ \text{m}^3$$

$$e = 1.6 \times 10^{-19} \text{ C}$$

$$A = \pi r^2 = \pi (0.001 \text{ m})^2 = 3.1 \times 10^{-6} \text{ m}^2$$

$$I = 1.0 \text{ A}$$

$$v = 0.0002 \text{ m/s} = 0.2 \text{ mm/s}$$

"Drift Velocity"

⑥

$$\text{People Flow rate} = \frac{\text{People}}{\text{m}^2} \times \text{v} \times \left(\begin{array}{c} \text{Door} \\ \text{Width} \end{array} \right)$$

$$\text{Resistivity} \quad R = \rho \frac{l}{A}$$

↑
resistivity

Thermal Coefficient

$$R = R_0 (1 + \alpha (T - T_0))$$

$$\frac{R}{R_0} = 1 + \alpha (T - T_0)$$

$$\frac{R}{R_0} - 1 = \alpha (T - T_0)$$


$$\frac{R - R_0}{R_0} = \alpha (T - T_0)$$

$$\frac{\Delta R}{R_0} = \alpha \Delta T$$

Fractional Change in resistance = (Temp Change) (Temp Coeff)

$\alpha = 0.01 \text{ } ^\circ\text{F}^{-1}$ means 1% for every $^\circ\text{F}$

5

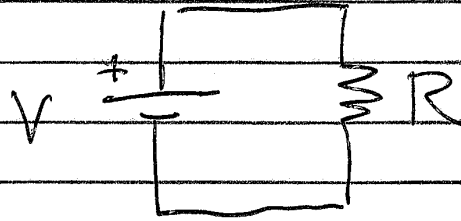

$$I = \frac{V}{R}$$

$$P = IV = \frac{V^2}{R}$$

Power heats the resistor.

$$\text{If } \alpha \text{ is } \oplus: \frac{\Delta R}{R_0} = \alpha \Delta T$$

ΔR is \oplus

R increases

P decreases

System finds equilibrium

$$\text{If } \alpha \text{ is } \ominus: \Delta R \text{ is } \ominus$$

R decreases

P increases

System heats more!
Thermal Runaway.