

① Phys 1402 2015-09-17 Lec 7

HW 2 - Work on it!

- Use "Ask Your Teacher"

Qualcomm Quick Charge (Android)

- Battery charger supplies energy
- Faster rate = less time

$$P = I V$$

$$\text{Usual: } V = 5.0 \text{ V}$$

More power is from more I .

Ex: 500 mA, 1.0 A, 2.0 A

$$\text{Limit } P = (5.0 \text{ V})(2.0 \text{ A}) \\ = 10.0 \text{ W}$$

- New Tech: Allows 9.0V, 12.0V DC

$$\text{Ex: } (12.0 \text{ V})(2.0 \text{ A}) < 24 \text{ W}$$

②

Simultaneous Equations (Linear Eqns)

- * Can use calculator
- * Manually

$$I_1 + I_2 = 5.0$$

$$3I_1 - 2I_2 = -5.0$$

- * Pick an eqn, solve for a variable

$$I_2 = 5 - I_1$$

- * Sub into other eqn(s).

$$3I_1 - 2(5 - I_1) = -5$$

$$3I_1 - 10 + 2I_1 = -5$$

$$5I_1 = 5$$

$$I_1 = 1.0 \text{ A}$$

- * Sub back into other eqn.

$$I_2 = 5 - (1.0 \text{ A}) = 4.0 \text{ A}$$


③

Circuit Analysis Principles

Cons. of Charge

Must account for flow of charge
(Current, I) in circuit.


What goes in must come out

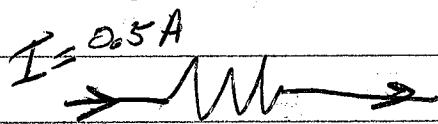

We know $I = 0.5A$ out

Current goes "through."

At a junction, current "splits".

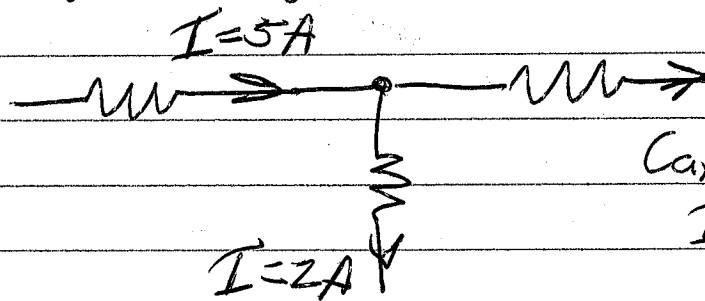


Can deduce
 $I = 3A$

④

Cons of Energy per Charge

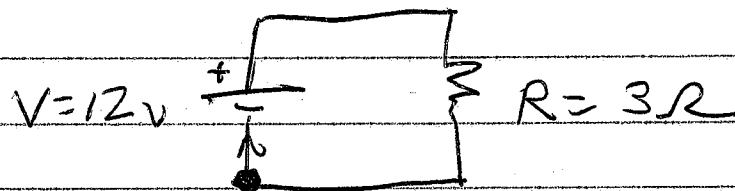- When a charge circulates around a circuit, its energy gains equal its losses.
- Voltage is energy per charge.




- Heading up thru batt $\Delta V = +12V$
- Going down thru R $\Delta V = -12V$

$$\text{Total } \Delta V = 0$$

$$V_{\text{Batt}} = V_R$$

57

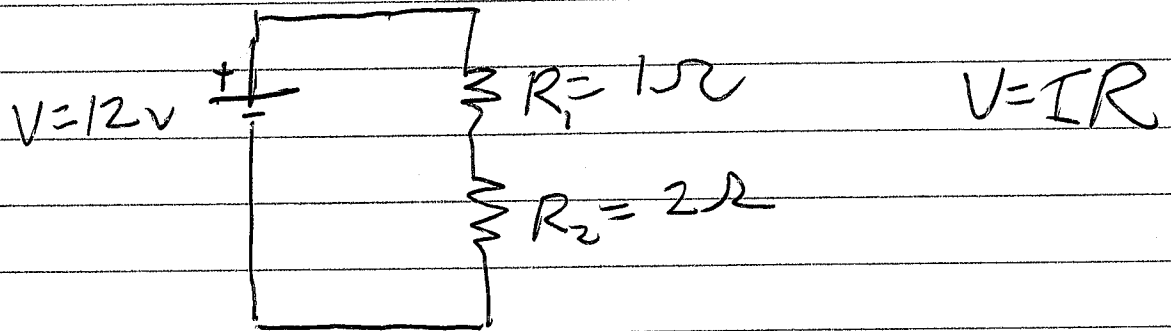Series Circuit - current passes thru components one after another.



- Batt $\Delta V = +12V$
- R_1 $\Delta V = I_1 R_1$
- R_2 $\Delta V = I_2 R_2$

Gains = Losses
 $(12v) = I_1 R_1 + I_2 R_2$

Series - There is only one current.

$$(12v) = I R_1 + I R_2$$
$$12v = I (R_1 + R_2)$$


R_{eq} "seen" by batt.

In series $R_{eq} = R_1 + R_2 + \dots$

$$I = 4A$$
$$V = (4A)(1\Omega) = 4V$$
$$V_2 = (4A)(2\Omega) = 8V$$

⑥

Parallel Circuits

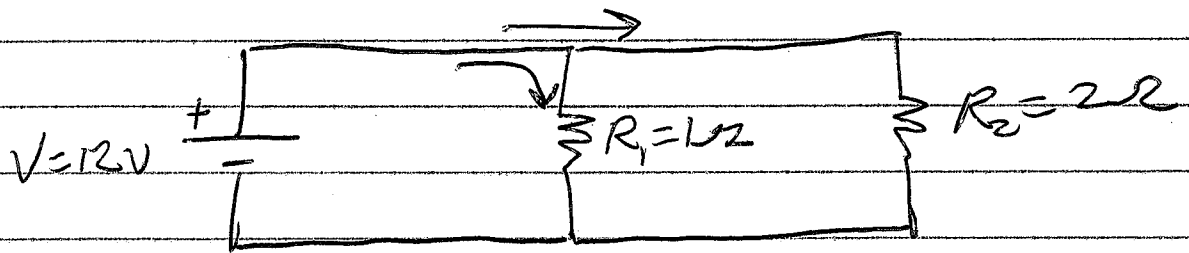

Any charge going thru the battery has a choice about which R to go thru.

R_1 Loop

R_2 Loop

$$(12V) = I_1 R_1$$

$$(12V) = I_2 R_2$$

Both resistors "see" the full voltage.

$$I_1 = 12A$$

$$I_2 = 6A$$

The batt must provide both.

$$I_{\text{batt}} = I_1 + I_2 + \dots$$

$$V_{\text{batt}} = I_{\text{batt}} R_{\text{eq}}$$

$$\frac{12V}{18A} = R_{\text{eq}} = 0.667 \Omega$$

$$\frac{V}{R_{\text{eq}}} = \frac{V}{R_1} + \frac{V}{R_2} + \dots$$

②

Series

Parallel

Current

$$I = I_1 = I_2 = \dots$$

$$I_T = I_1 + I_2 + \dots$$

Voltage

$$V_T = V_1 + V_2 + \dots$$


$$V = V_1 = V_2 = \dots$$

Resistance


$$R_{eq} = R_1 + R_2 + \dots$$

$$R_{eq} = \left(\frac{1}{R_1} + \frac{1}{R_2} + \dots \right)^{-1}$$

Combination Circuit

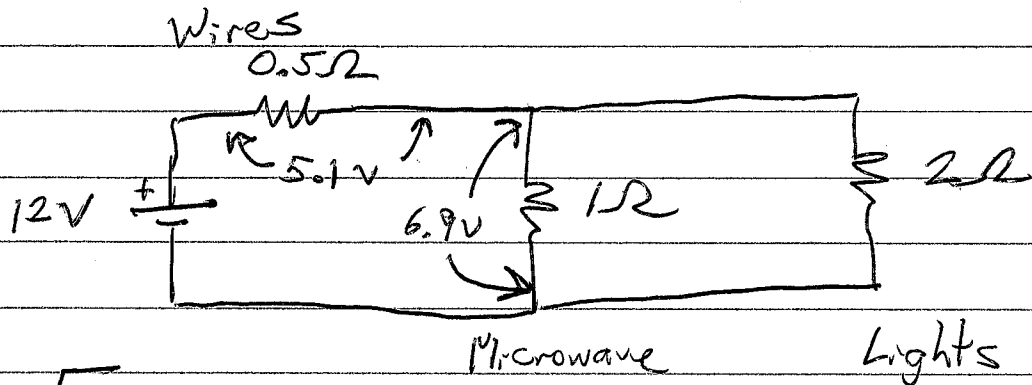

$$V = IR$$

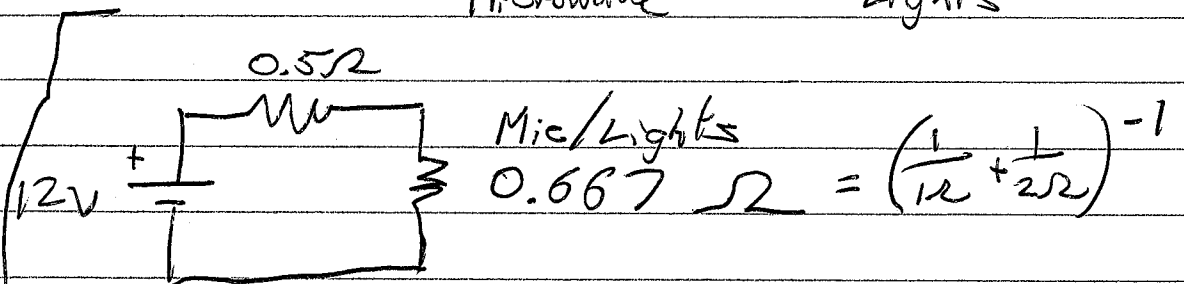

$$(12V) = I (0.5\Omega + 0.667\Omega)$$

$$I = 10.3 \text{ A}$$

$$V_{\text{wire}} = IR_{\text{wire}} = (10.3 \text{ A})(0.5\Omega) = 5.1 \text{ V}$$

$$V_{\text{Mic/L}} = (10.3 \text{ A})(0.667\Omega) = 6.9 \text{ V}$$

$$\left. \begin{aligned} I_M &= \frac{6.9 \text{ V}}{1\Omega} = 6.9 \text{ A} \\ I_L &= \frac{6.9 \text{ V}}{2\Omega} = 3.4 \text{ A} \end{aligned} \right\} \text{Tot} = 10.3 \text{ A}$$