

① Phys 1402 2015-09-22 Lec 8

Exam 1 Tue 9/29


Kirchoff's Laws

- Cons. Charge - Kirchoff's Current Law

$$\sum I_{in} = 0 \quad (\text{outward is } \ominus)$$

$$\sum I_{in} = \sum I_{out}$$

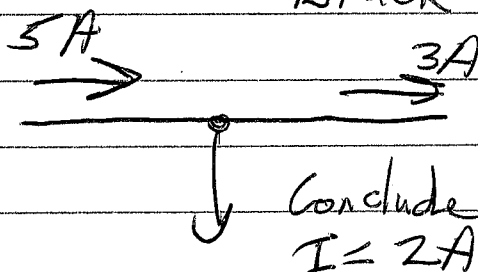Applies to : Junction
Component
Black Box



$$I_5 = I_3 + I_2$$

②


• Cons. Energy per Charge (Voltage)

$$\sum \Delta V = 0$$

$$\sum V_{\text{rises}} = \sum V_{\text{drops}}$$

Applies to: Any "closed" loop.

Ex: Series Circuit

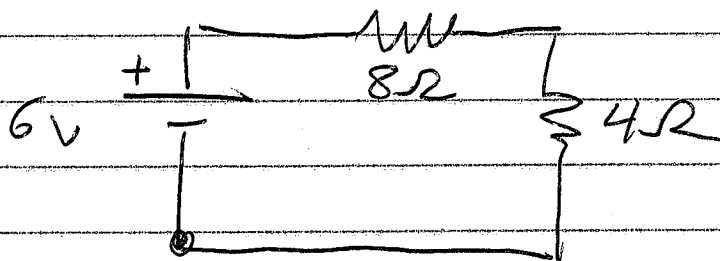

Start @ Lower Left, go CW.

Battery	$V_{\text{rise}} = 6 \text{ V}$	$\Delta V = +6 \text{ V}$
8Ω	$V_{\text{drop}} = I(8 \Omega)$	$\Delta V = -(8 \Omega)I$
4Ω	$V_{\text{drop}} = I(4 \Omega)$	$\Delta V = -(4 \Omega)I$

$$(6 \text{ V}) = I(8 \Omega) + I(4 \Omega) \rightarrow I = 0.5 \text{ A}$$

$$(6 \text{ V}) - (8 \Omega)I - (4 \Omega)I = 0 \rightarrow$$


Follow the currents and R's are "drops".
Batteries are rises if you go \ominus to \oplus .

③

Why use Kirchoff's Laws?

- Two Batteries
- Complicated meshes,

Ex: Car Battery Charger

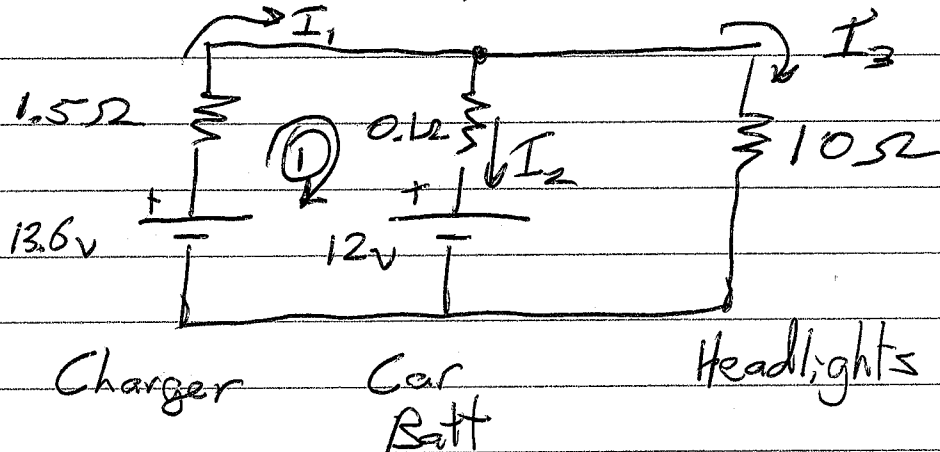

Method: Mesh Currents - avoid
Node Voltages - ok, but not covered
Currents - typical method

- Choose measurable currents.
- Build current Egn.

$$I_1 = I_2 + I_3$$

- Build voltage eqns.

$$\textcircled{1} \quad +13.6\text{V} - 12\text{V} = 1.5 I_1 + 0.1 I_2$$

$$\text{(Outside)} \quad +13.6 = 1.5 I_1 + 10 I_3$$

simultaneous eqns

$$I_1 = 1.07 \text{ A}$$

linear eqns

$$I_2 = -0.12 \text{ A}$$


$$I_3 = 1.20 \text{ A}$$

(4)

Capacitors and RC Circuits

5 Far: Steady state is $I = 0$,
Charge is $Q = CV$


Compare a battery to a charged cap:

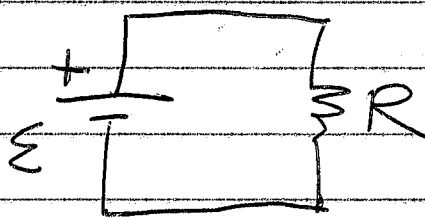

$$V_R = \varepsilon = \text{const}$$

$$I = \frac{V_R}{R} = \text{const}$$

Battery provides
steady voltage.

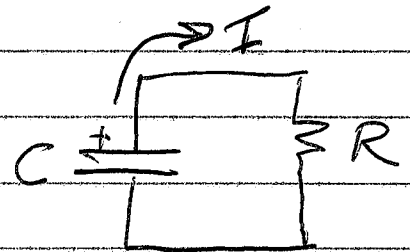

$$V_R = V_C = \text{not const}$$

$$I = \frac{V_R}{R} \text{ drains cap}$$

$Q = CV$ decreases

Cap still drains, but
more slowly.

Eventually, $I \approx 0$

Like a Faucet.


Steady Pressure.

Like a bucket/tank.
Pressure depends on
fullness.

1402

⑤


Math of Discharging Capacitor

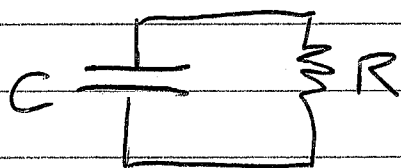

$$V_R = IR$$

$$V_C = Q/C$$

All Quantities decrease exponentially

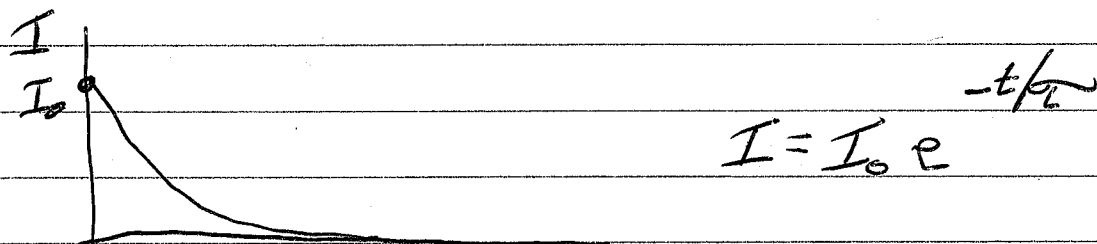

I = current at any moment in time

I_0 = initial current

$\tau = RC$ = time constant

e = Euler's constant ≈ 2.718

$e^{-t/\tau}$ = fraction of process remaining
 0.5 means halfway done

$$e^x = 0.5$$

$$x = \ln(0.5) = -0.693$$

$$-t/\tau = -0.693$$

$$t = 0.693 \tau$$

Time needed to get halfway done.
 Called "half-life".

1402 ⑥

Ex 18.6, but discharging

$$V_0 = 12.0 \text{ V}$$

$$C = 5.0 \mu\text{F}$$

$$R = 800 \text{ k}\Omega$$

$$\text{Initial Current } I_0 = \frac{V_0}{R} = 0.000015 \text{ A} \\ = 15 \mu\text{A}$$

$$\text{Initial Charge } Q_0 = CV_0 = (5 \times 10^{-6} \text{ F})(12.0 \text{ V}) \\ = 0.00006 \text{ C} \\ = 60 \mu\text{C}$$

$$\text{Time Const } \tau = RC = (5 \times 10^{-6} \text{ F})(800 \times 10^3 \Omega) \\ = 4.0 \text{ s}$$

Time to get down to 1.0 V:

$$V = V_0 e^{-t/\tau} \\ (1.0) = (12) e^{-t/\tau}$$

$$\frac{1}{12} = 0.0833 = e^{-t/\tau} \\ -2.48 = -t/\tau \quad (\text{ln both}) \\ t = (4)(2.48) = 9.94 \text{ s}$$