

1902 ① Phys 1402 2015-09-24 Lec 9

Exam 1 Tue 9/29

My Calendar: tinyurl.com/spirkocal

Topics:

Electrostatics, charge, E-Field

Elec Potential, Batteries & Capacitors

DC Current, Ohm's Law


Complex DC Circuits, Equivalent R.

Measuring DC Values: V I R

RC Circuits, Discharging.

Definition

$$V = \frac{\text{Energy}}{\text{Charge}}$$

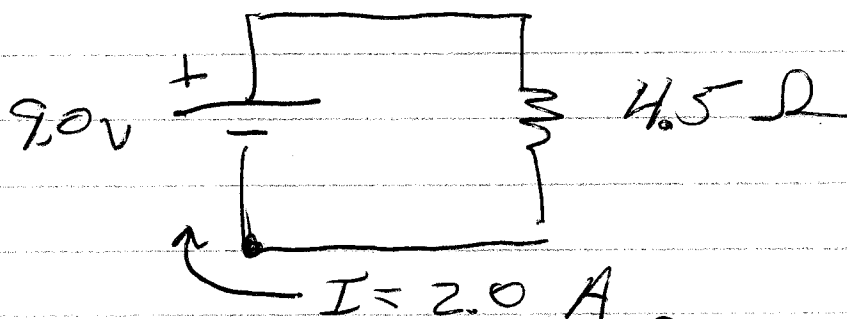

The 2.0 A is formed from charges.

Starting at L.L., each \oplus goes:


- Thru batt gains 9.0 J/c.

$$P = (9 \text{ J/c})(2 \text{ c/s}) = 18 \text{ J/s}$$

- Thru R, lose 9.0 J/c

1402 (2)

Charge in elec field

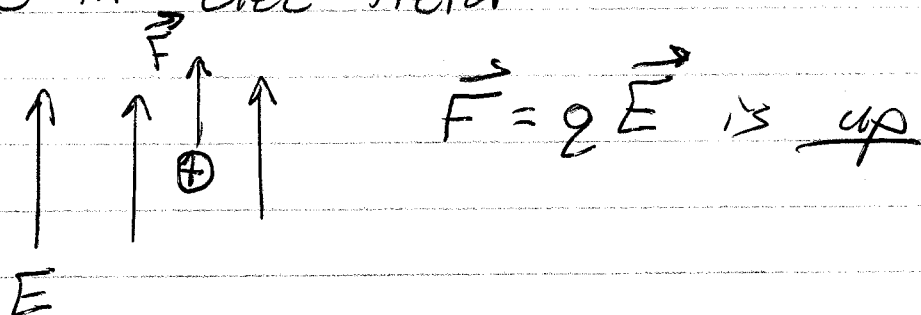

As the charge is pushed up it gains Kinetic Energy. Where does that KE come from? It was potential energy.

$$|\Delta PE| = F \cdot \text{Dist}$$


$$\frac{|\Delta PE|}{q} = \frac{E \cdot \text{Dist}}{q}$$

$$|V| = E \cdot \text{Dist}$$



E points "downhill" toward lower (or negative) V.

1402 (3)


Series Dc Circuit

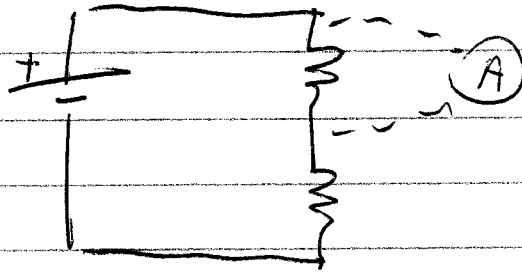

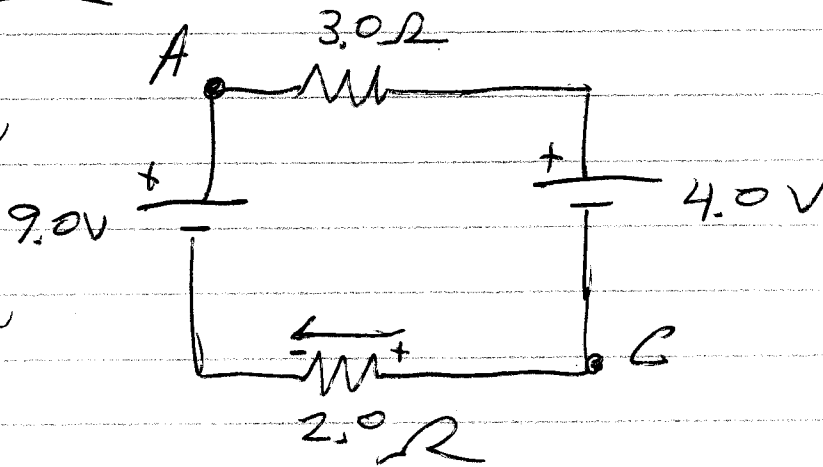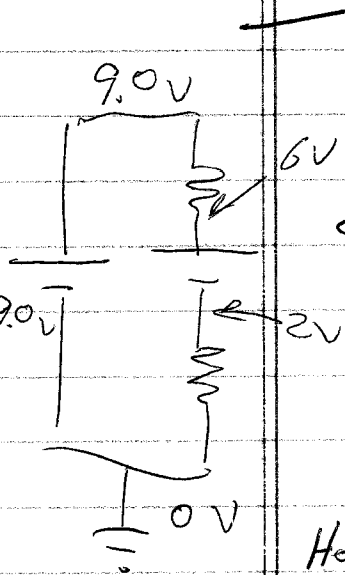What if (A) is placed across one bulb,
 What if (V) is hooked in series?



What is $V_A - V_C$?
 $+7V$

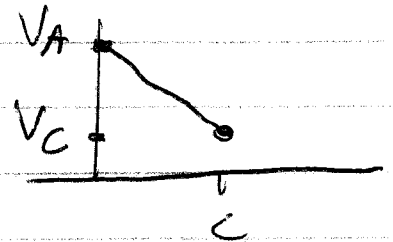

How much current flows?

- $9/5$ A
- 3 A
- 1 A
- $13/5$ A

Steps: $+9 - I \cdot 3 - 4 - I \cdot 2 = 0$
 $(9-4) = I \cdot 5$
 $(5V) = I \cdot (5\Omega) \Rightarrow I = 1.0A$

1402 (4)

A capacitor ($4 \mu\text{F}$) is charged to 9.0 V . What R will drain it halfway in 10.0 s ?

$$V = V_0 e^{-t/\tau}$$

$$\tau = RC$$

$$(4.5) = (9.0) e^{-10/\tau}$$

$$(4.4) = R (4 \times 10^{-6})$$

Half


$$0.5 = e^{-10/\tau}$$

$$R = 3.6 \times 10^6 \Omega = 3.6 \text{ M}\Omega$$

$$\ln(0.5) = \frac{-10}{\tau}$$

$$-0.693 \tau = -10$$

$$\tau = 14.4 \text{ s}$$

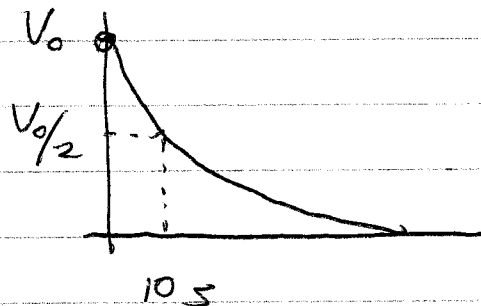

After 1 time const how much charge is left (as a % of full).

$$Q = Q_0 e^{-t/\tau}$$

$$\frac{Q}{Q_0} = e^{-t/\tau}$$

Answer

$$e^{-\tau/\tau} = e^{-1} = 0.37$$

Answer = 37%

$$\text{After } 2\tau ? \quad e^{-2\tau/\tau} = e^{-2} = 0.14 \Rightarrow 14\%$$

1402 ⑤

If you use a light bulb for 4 hours/day and electricity costs \$0.12/kWh, how much is saved in a year by using a ~~13~~ 13W CFL vs 60W incandescent?

$$\text{Total hours} = 4 \frac{\text{h}}{\text{day}} \cdot 365 \text{ day} = 1460 \text{ h}$$

$$\text{Cost} = \frac{\text{Cost}}{\text{item}} (\text{items})$$

$$= \left(\$0.12 \frac{\text{}}{\text{kWh}} \right) (0.013 \text{ kW}) (1460 \text{ h})$$

$$= \$2.28$$

$$\text{Incandescent} \left(\frac{\$}{\text{kWh}} \right) (0.060 \text{ kW}) (1460 \text{ h})$$

$$= \$10.51$$