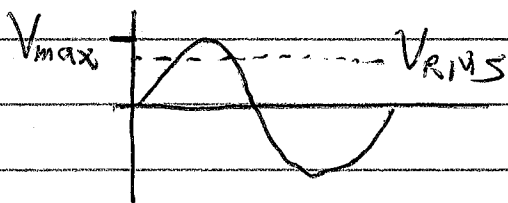


① Phys 1402 2015-10-20 Lec 16

Exam 2 Thu 10/29

Covers	Magnetism	Chap 19
	EM Induction	20
	AC Circuits	21

AC Voltages oscillate



$$V_{RMS} = \frac{V_{max}}{\sqrt{2}}$$

$$V_{RMS} = (70.7\%) V_{max}$$

RMS is most like the "standard deviation".

$$V(t) = V_{max} \sin(2\pi F t)$$

f = Frequency in hertz (Hz)

$T = \frac{1}{f}$ = period in seconds (s)

Ex: US outlets:

$$V_{RMS} = 120 \text{ V}$$

$$F = 60 \text{ Hz}$$

②

Resistors in AC

In DC: $V = IR$

In AC: $V(t) = I(t) R$

$$\boxed{V_{RMS} = I_{RMS} R}$$

f is shared
by V and I

In DC $P = VI$

In AC $P(t) = V(t) I(t)$

$$= (V_{RMS} \sqrt{2}) \sin(2\pi f t) (I_{RMS} \sqrt{2}) \sin(2\pi f t)$$


$$P(t) = 2 V_{RMS} I_{RMS} \sin^2(2\pi f t)$$

$$\sin^2(\theta) = \frac{1}{2} (1 - \cos(2\theta))$$

$$P(t) = V_{RMS} I_{RMS} (1 - \cos(2\pi(2f)t))$$

$$\text{Average } [P(t)] = V_{RMS} I_{RMS}$$

P_{avg}

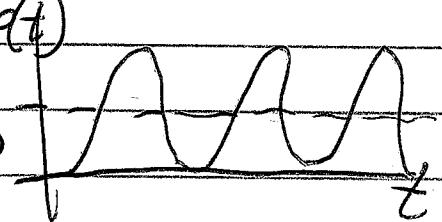

③

Ex: ~~100 W~~ ~~120 V~~ 60 W Light bulb
120 V RMS voltage

$$P = IV$$
$$(60 \text{ W}) = I (120 \text{ V}) \Rightarrow I = 0.5 \text{ A}$$

RMS Current is 0.5 A.

$$V = IR$$
$$(120 \text{ V}) = (0.5 \text{ A}) (R) \Rightarrow R = 240 \Omega$$

$$P = VI = (IR)I = I^2 R$$

This is the ~~ONLY~~ power used in AC.

(4)

Inductors (L)


In DC: Inductor is a wire.
Low R \rightarrow high current

Inductors oppose change in current and B.

In AC, I varies continually.
The inductor responds by opposing w/ voltage.

$V_L \propto I$ because $I(t) = I_{\max} \sin(2\pi ft)$
bigger $I_{\max} \rightarrow$ steeper graph

$V_L \propto f$

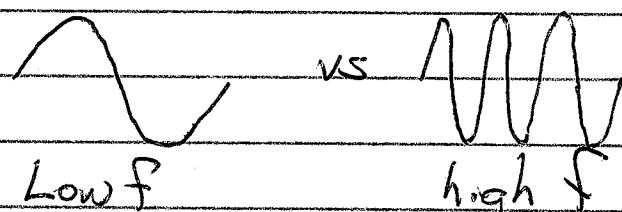

vs

$$V_{L,rms} = \underbrace{(2\pi fL)}_{X_L} I_{rms}$$

X_L Reactance

Z_L Impedance (generic term)

Impedance is like resistance for AC.

$$V_{RMS} = Z I_{RMS} \quad \text{AC Ohm's Law}$$

$$P_{L,avg} = 0 \quad \text{Inductor doesn't use energy.}$$

5

Capacitors (C)



In DC, capacitor has an insulator
 $R = \text{high} \rightarrow \text{No current}$

Capacitors take time to charge.
Changing the voltage is difficult.

In AC, V is changing continually.
The faster V changes, the more current
must flow to charge & discharge
the capacitor. $Q = CV$

$$I = \frac{\Delta Q}{\Delta t} = C \frac{\Delta V}{\Delta t}$$

$I \propto V_{\text{max}}$  vs 

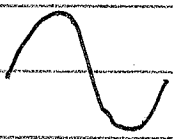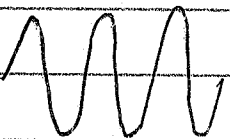$I \propto f$  vs 

$$I_{\text{rms}} = (2\pi f C) V_{\text{rms}}$$

$$V_{\text{rms}} = \left(\frac{1}{2\pi f C} \right) I_{\text{rms}}$$

X_c Capacitive Reactance
 Z_c Impedance

6

$$V_{RMS} = I_{RMS} Z$$

Resistor $Z = R$

$$P = I_{RMS}^2 R$$

Inductor $Z = 2\pi f L$

$$P = 0$$

Capacitor $Z = \frac{1}{2\pi f C}$

$$P = 0$$


Series RLC Circuit

Impedances add like vectors

Z_R in $+x$

Z_L in $+y$

Z_C in $-y$

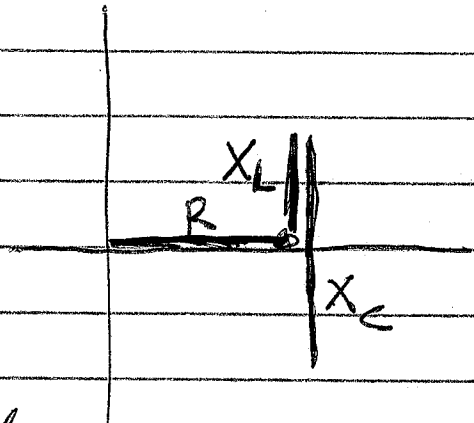

R $\quad x \quad y$
R

L

$$X_L = 2\pi f L$$

C

$$-X_C = -\left(\frac{1}{2\pi f C}\right)$$

Tot

R

$X_L - X_C$

$$|Z| = \sqrt{R^2 + (X_L - X_C)^2}$$

