

Phys 1402 2015-10-22 Lec 17

Exam 2 Thu 10/29

AC Voltage pushes AC Current,

$$V_{rms} = Z I_{rms}$$

$Z = \text{impedance}$



Series Impedance $Z = \sqrt{R^2 + (X_L - X_C)^2}$

$X_L = 2\pi f L$ Inductor blocks high-f

$X_C = \frac{1}{2\pi f C}$ Capacitor blocks low-f

Resonant AC Circuit

If $X_L = X_C$, they exactly cancel.

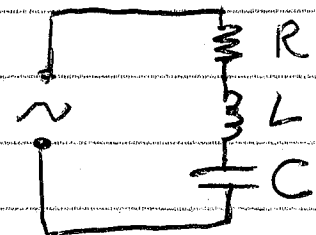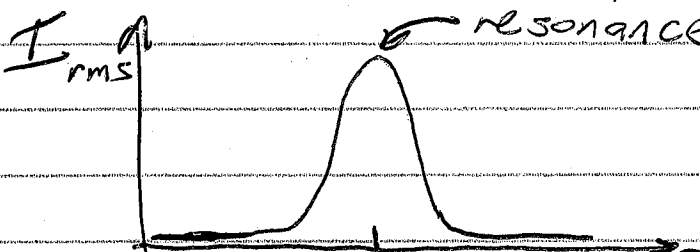

Fixed V_{rms} , vary f

Cap blocks low f

Inductor blocks high-f

②

What Frequency is resonant?

$$X_L = X_C$$

$$2\pi fL = \frac{1}{2\pi fC}$$

$$(2\pi f)^2 = \frac{1}{LC}$$

$$2\pi f = \frac{1}{\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

Ex: $C = 0.1 \mu\text{F}$ $f = 93.7 \text{ MHz}$

$$(93.7 \times 10^6) = \frac{1}{2\pi\sqrt{L(0.1 \times 10^{-6})}}$$

$$2\pi fL = \frac{1}{2\pi fC}$$

$$L = \frac{1}{(2\pi f)^2 C} = \frac{1}{(2\pi(93.7 \times 10^6))^2 (0.1 \times 10^{-6})}$$

$$= 2.9 \times 10^{-11} \text{ H}$$

$$= 0.029 \text{ nH}$$


$$L = \frac{\mu_0 N^2 A}{l} = \text{tiny for physically small inductor.}$$

What if C is smaller? $\rightarrow L$ must be bigger.

3

Filters


	Low-f	High-f
Inductor	Passes	Blocks
Capacitor	Blocks	Passes

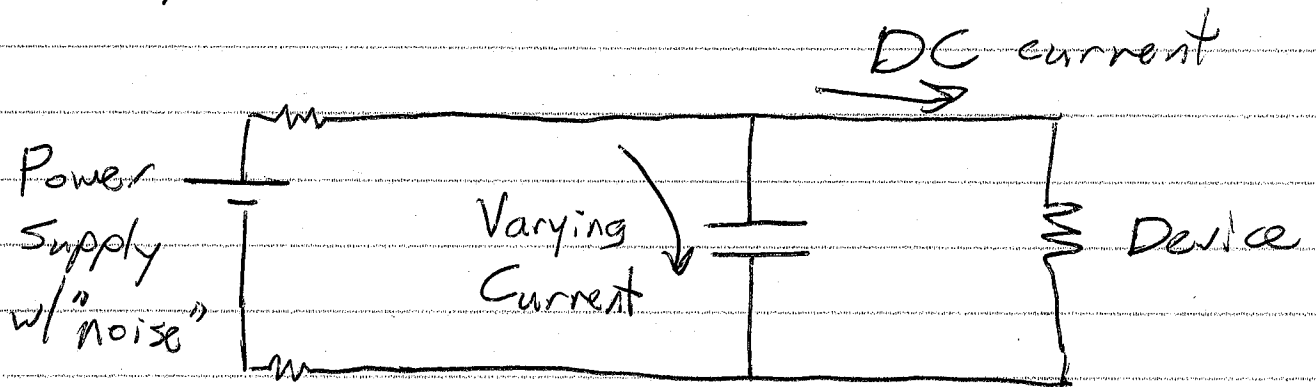

Want $V = \text{const.}$

Any changing V is noise.


Same effect with inductor in series

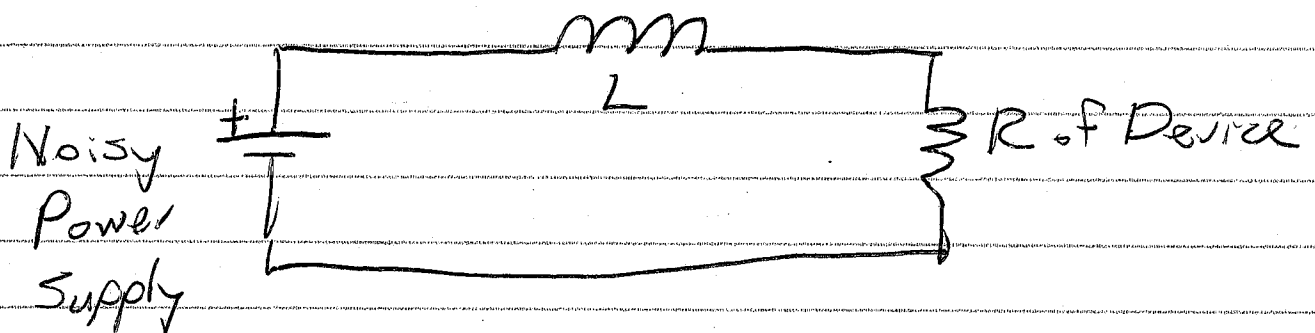

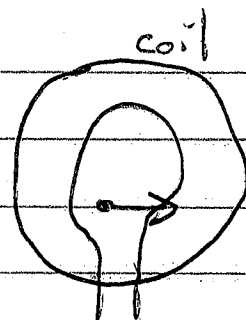(4)

In Lab, an electron beam
was directed to the right.
The magnetic force made
them bend upward.

Dir of magnetic field? (Out of page,
toward us)



$$F_B = qv_{\perp} B$$

B points N, proton is dropped.
Dir of initial deflection? (East)

In series, a huge Z_i makes Z larger.

103 K capacitor


$$10 \overbrace{000}^{\text{m}} \times 10^{-12} \text{ F} = 0.01 \mu\text{F}$$

⑤

Wire length 5.73 m
 $r = 0.0125$ m
 $l = 0.0615$ m } solenoid

$$\frac{\Delta I}{\Delta t} = 5.5 \times 10^2 \text{ A/s}$$

Loops?

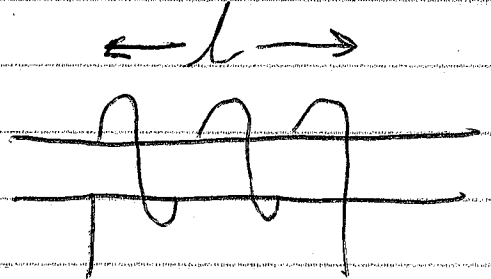

1 loop is how much wire?

$$l_{\text{loop}} = 2\pi r$$

$$l_{\text{wire}} = N 2\pi r$$

$$(5.73) = N 2\pi (0.0125) \rightarrow N = 73$$

Inductance?

$$\pi r^2$$

$$L = \frac{\mu N^2 A}{l}$$

$$L = 5.35 \times 10^{-5} \text{ H}$$

EMF?

$$\mathcal{E} = L \frac{\Delta I}{\Delta t}$$

$$\mathcal{E} = 5.35 \times 10^{-5} \times 5.5 \times 10^2 \\ = 0.029 \text{ V}$$