

① Phys 1402

2016-10-20 Lec 17

Components of AC Circuits

Voltage Source

Resistors

$$V_R = IR$$

$$P = VI$$

$$V_{rms} = I_{rms} R$$

$$P_{avg} = V_{rms} I_{rms}$$

Inductors - basically coils

$$V_L = L \frac{\Delta I}{\Delta t}$$

$$(\text{Energy})_L = \frac{1}{2} LI^2$$

- Voltage makes the current increase
- Constant current requires no voltage.
- Inductor doesn't use energy


$$V_{rms} = I_{rms} X_L$$

$$P_{avg} = 0$$


$$X_L = \text{inductive reactance}$$
$$= 2\pi fL$$

- Passes Low f
- Blocks High f

Compare:

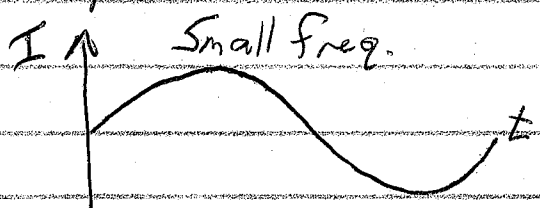

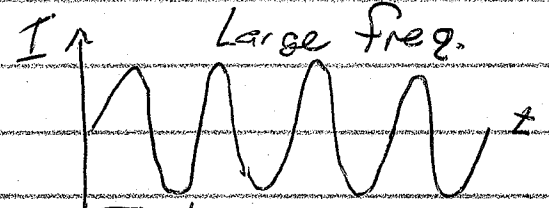Slow changes in I.
Small $\Delta I/\Delta t$



Fast changes in I.
Large $\Delta I/\Delta t$

②

Capacitors - Breaks in the circuit w/
lots of surface area.

$$V_c = Q/C$$
$$Q = CV_c$$

$$(\text{Energy})_c = \frac{1}{2} CV^2$$

- Current changes Q , which changes V_c .
(opposite of inductor)
- Constant Voltage \rightarrow const $Q \rightarrow$ no current
- Cap doesn't use power.

$$V_{rms} = I_{rms} X_c$$


$$P_{avg} = 0$$

$X_c =$ capacitive reactance

$$X_c = \frac{1}{2\pi fC}$$

- Blocks Low-f
- Passes High-f

Compare:

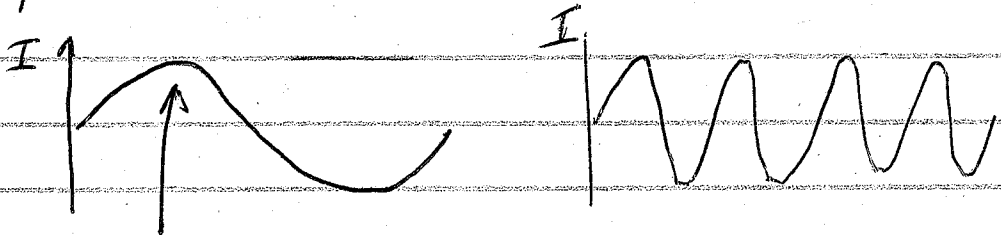

- Lots of time to charge capacitor
- Q gets large
- V_c gets large
- Low $f \rightarrow$ High X_c
- Low $C \rightarrow$ High X_c

③

$$E_x = \begin{aligned} V_{rms} &= 120 \text{ V} \\ f &= 60 \text{ Hz} \end{aligned}$$

Attach a $0.1 \mu\text{F}$ capacitor

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi (60) (0.1 \times 10^{-6})} = 26500 \Omega$$


$$V_{rms} = I_{rms} X_C$$

$$I_{rms} = \frac{120 \text{ V}}{26500 \Omega} = 0.0045 \text{ A} = 4.5 \text{ mA}$$

This capacitor mostly blocks 60 Hz AC.

(A)

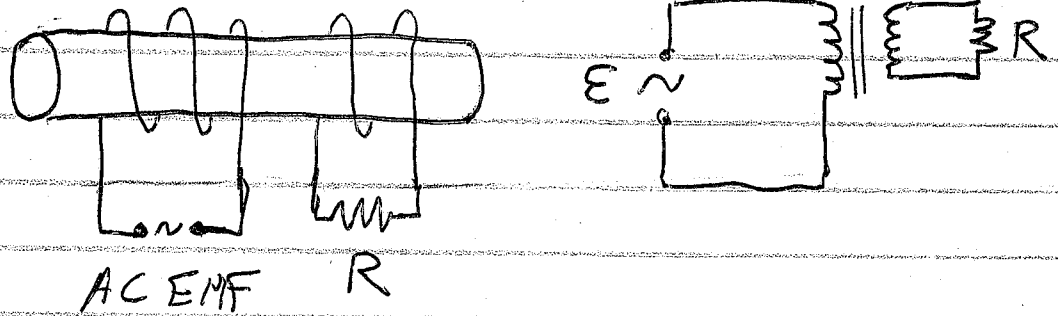Transformer - Two coils with overlapping magnetic fields.



In a transformer:

- EMF applied to primary, must be AC!
 - AC current flows
 - B oscillates
- Secondary coil "feels" B .
 - Φ_B oscillates
 - Generates EMF in secondary
- Load (R) attached to secondary
 - E_2 pushes current in load.

The EMF's are related

$$\text{Voltage Ratio} = \frac{E_2}{E_1} = \frac{N_2}{N_1} = \text{Turns Ratio}$$

$$E_1 = 120 \text{ V}$$

$$N_2 = 50$$

$$E_2 = 5 \text{ V}$$

$$\frac{5}{120} = \frac{50}{N_1}$$

$$N_1 = 1200$$

3

Transformers pass energy fairly efficiently.

$$P_{in} = P_{out}$$


$$E_1 I_1 = E_2 I_2$$

If our 5V is at 2.0 A

$$120 \cdot I_1 = 5 \cdot 2$$

$$I_1 = \frac{10}{120} = 0.08 \text{ A}$$

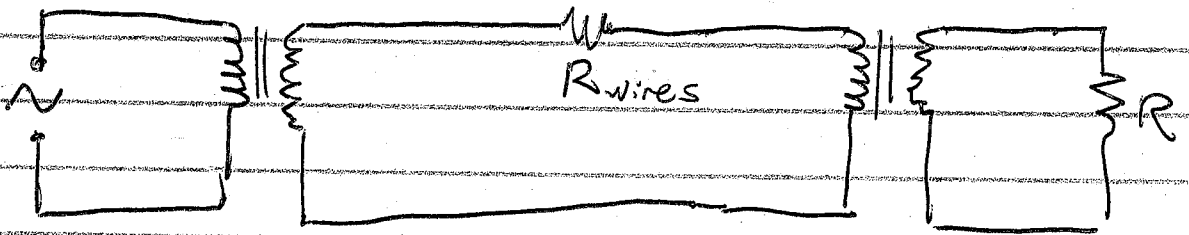This transformer increases the current!
The voltage is decreased \rightarrow step-down



Generator

Transmission
Wires

House

R_{wires} wastes energy $P = I^2 R$
High voltage \rightarrow Low current