

① Phys 1402

2016-10-25

Lec 18

## Passive Components

Resistor - Opposes Current.

$$V = IR$$

$$V_{rms} = I_{rms} R$$

Inductor - Opposes change in current.

$$V = L \frac{\Delta I}{\Delta t}$$

$$X_L = 2\pi f L$$

↗ opposes high-f

$$V_{rms} = I_{rms} X_L$$

Capacitor - Current fills capacitor


$$I = \frac{\Delta Q}{\Delta t} \quad V = Q/C$$

$$X_C = \frac{1}{2\pi f C}$$

↗ passes high-f

$$V_{rms} = I_{rms} X_C$$

AC Current

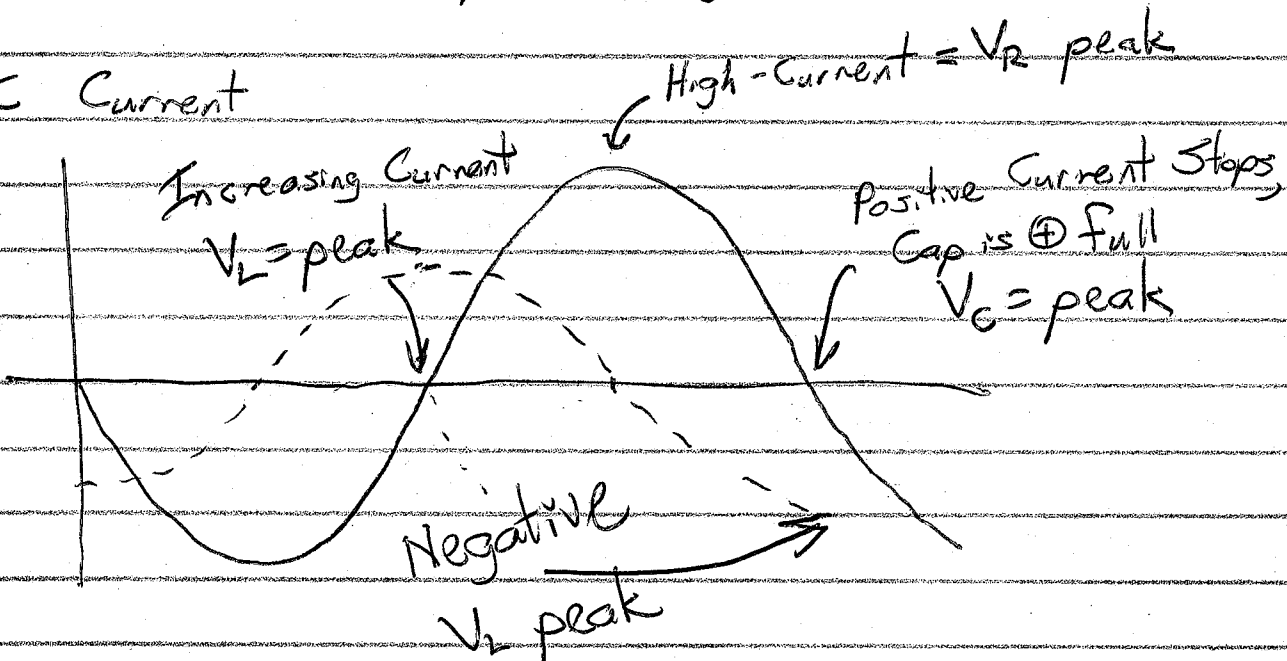

② Phys 1402

2016-10-25

## Series DC Circuit

$$I = \text{const}$$

Same  $I$  in each component

Voltage adds  $V_{\text{tot}} = V_1 + V_2 + \dots$

Inductors:  $X_L = 2\pi fL = 0$

Doesn't get in the way

Acts like a wire

Capacitor:  $X_C = \frac{1}{2\pi fC} = \infty$  Blocks current

Caps get all of the voltage.

Resistors:

$$R_{\text{eq}} = R_1 + R_2 + \dots$$

$$IR_{\text{eq}} = IR_1 + IR_2 + \dots$$

$$V_{\text{tot}} = V_1 + V_2 + \dots$$

## Series AC Circuit

$$I = I_0 \sin(2\pi ft)$$

Same  $I$  in each component

$$V_L = +I_0 X_L \cos(2\pi ft)$$

$$V_R = I_0 R \sin(2\pi ft)$$

$$V_C = -I_0 X_C \cos(2\pi ft)$$

opposite


Must Add these voltage graphs.

- Know lots of trig identities
- Graphical Method

③ Phys 1402 2016-10-25

Add Voltages as vectors!
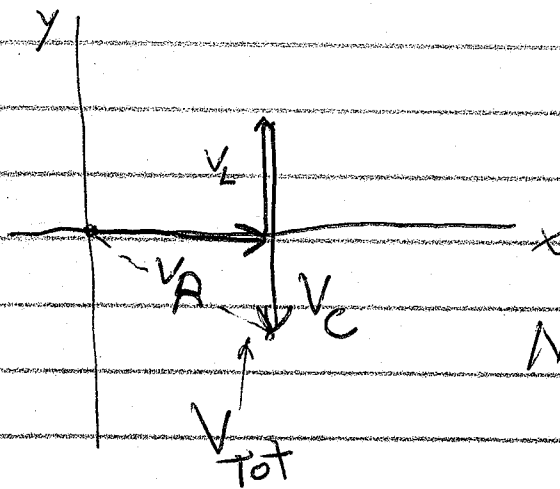
$$\begin{aligned} V_R &\rightarrow V_R \hat{x} && \text{(in the x-dir)} \\ V_L &\rightarrow V_L \hat{y} && \text{(in the y-dir)} \\ V_C &\rightarrow V_C (-\hat{y}) \end{aligned}$$



$$\text{Total } x: V_R$$

$$\text{Total } y: V_L - V_C$$

$$\text{Net Tot} = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$IZ = I \sqrt{R^2 + (X_L - X_C)^2}$$

$$V_R = IR$$

$$V_L = X_L I$$

$$V_C = X_C I$$

(All RMS or All peak)

↑  
Net Impedance

① Calculate Reactance

$$X = X_L - X_C$$

② Calc Impedance

$$Z = \sqrt{R^2 + X^2}$$

③ Apply AC Ohm's Law

$$V_{\text{tot}} = IZ$$

④

$$E_x: V = 140 \sin(500 t) = \mathcal{E}$$

$$\bullet V_{rms} = \frac{140}{\sqrt{2}} = 99 \text{ V}$$

$$\bullet 2\pi f = 500 \quad f = \frac{500}{2\pi} = 79.6 \text{ Hz}$$

$$\bullet R = 1000 \Omega$$

$$\bullet X_L = 2\pi f L \\ = (500)(1.0) \\ = 500 \Omega$$

$$\bullet X_C = \frac{1}{2\pi f C} = \frac{1}{(500)(1 \times 10^{-6})} \\ = 2000 \Omega$$

$$\bullet X = X_L - X_C = -1500 \Omega$$

$$\bullet Z = \sqrt{R^2 + X^2} = \sqrt{1000^2 + 1500^2} \\ = 1803 \Omega$$

$\curvearrowright$  Z is always  $\oplus$


$$\bullet I = \frac{V}{Z} = (99 \text{ V}) / (1803 \Omega)$$

$$= 0.0549 \text{ A} = 54.9 \text{ mA}$$

• Power is only used by the resistor

$$P = VI = I^2 R = (0.0549)^2 (1000) \\ = 3.02 \text{ W}$$
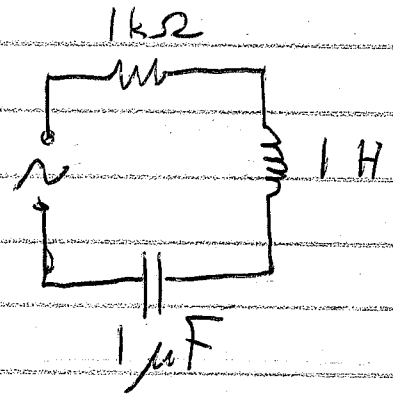
$$\bullet \text{ Volt-Amp rating} = (99 \text{ V})(0.0549 \text{ A}) = 5.44 \text{ VA}$$



⑤ Phys 1402

2016-10-25

Resonance - If  $X_L = X_C$ , they cancel.


$$X_L = X_C$$

$$2\pi fL = \frac{1}{2\pi fC}$$

$$f^2 = \frac{1}{(2\pi)^2 LC}$$

$$f = \frac{1}{2\pi \sqrt{LC}}$$

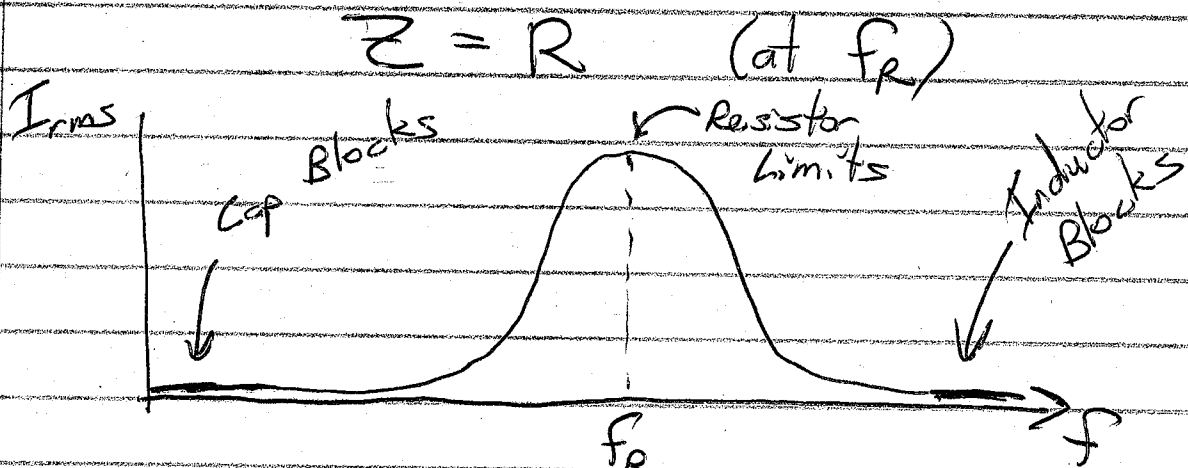This is a special frequency: resonant frequency. The inductor & capacitor cooperate to pass current at  $f_R$ . Only the resistor impedes the current.



Same  $V_{rms}$  @ every point