


① Phys 1402 2016-09-13 Lec 6

Up to now: Electrostatics - charges didn't move.

Electric Current - Flow of charges

A battery is like a pump that pressurizes the charges.

By itself:

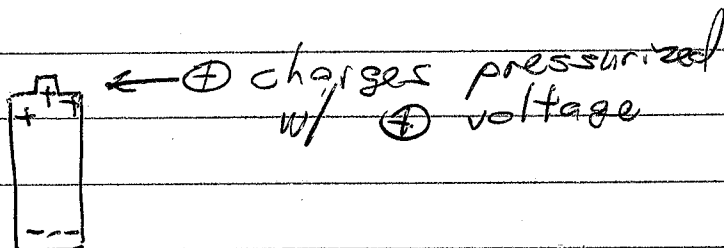

Given the opportunity, the \oplus charges will flow away from the \oplus end. As they flow, they give us energy. Conductive wires allow flow of charge.

How do we measure flow of charge?

$$\text{Flow} = \frac{\text{Amount of stuff}}{\text{Time Interval}}$$

$$\text{Current} = I = \frac{\Delta Q}{\Delta t} = \frac{\text{Charge}}{\text{Time}}$$

$$1.0 \text{ A} = 1.0 \text{ C/s}$$

②

How big is an amp?

Cell Phone: uses $0.1 \text{ A} \rightarrow 1.0 \text{ A}$

$100 \text{ mA} \rightarrow 1000 \text{ mA}$

Household Motor: $2.0 \rightarrow 10.0 \text{ A}$

Electric shock: 1.0 mA to just feel

What determines the amount of water coming out of a hose?

• Pressure, Valve

with electricity:

$$\text{Current} = I = \frac{V}{R} = \frac{\text{Voltage}}{\text{Resistance}}$$

Note: High $R \Rightarrow$ Low I

Ex: Flashlight w/ 3.0 V battery and a bulb w/ 15Ω resistance.


$$I = \frac{V}{R} = \frac{3.0 \text{ V}}{15 \Omega} = 0.2 \text{ A}$$

Change the bulb or battery and the current changes

③

Weird Facts about electricity:

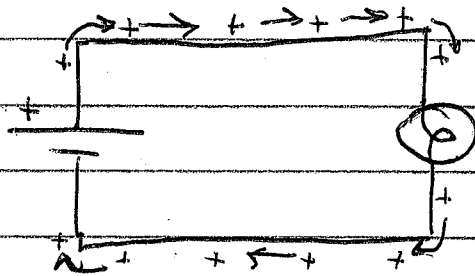- Seems to be instantaneous.
- Wires are always filled with charges, but they're not always pressurized with voltage.
- The actual charges move slowly.
($\sim 1 \text{ mm/s}$ in a cell phone charger)



- The instant the circuit is connected, the entire top wire is instantly pressurized w/ voltage. The charges touching the light bulb go thru it & lose energy. The energy is turned into light.
- \oplus charges going one way have the same effect as \ominus charges going the other way.

$$\oplus \rightarrow \oplus \rightarrow \oplus \rightarrow \quad I = \rightarrow$$

$$\leftarrow \ominus \leftarrow \ominus \leftarrow \ominus \quad I = \rightarrow$$

- With \ominus , the current is opposite to the velocity.

4

- Current always flows in loops, going through things along the way.
- Voltage sits in place, motivating the current to flow.

$$\text{Voltage} = \frac{\text{Energy}}{\text{Charge}}$$


$$\text{Current} = \frac{\text{Charge}}{\text{Time}}$$

$$V \cdot I = \frac{\text{Energy}}{\text{Charge}} \cdot \frac{\text{Charge}}{\text{Time}} = \frac{\text{Energy}}{\text{Time}}$$

= Power = flow rate of energy

$$E_x: V=3V \quad R=15\Omega \quad I=0.2A$$
$$P=VI=(3V)(0.2A)=0.6W$$

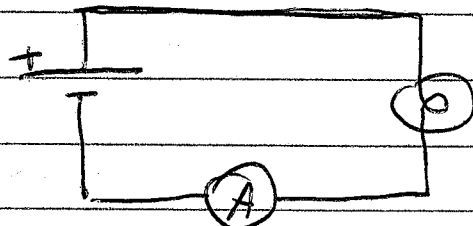Measuring Current: Current must flow thru our meter.



Hope this is equiv to previous circuit

current meter measures amps, ammeter