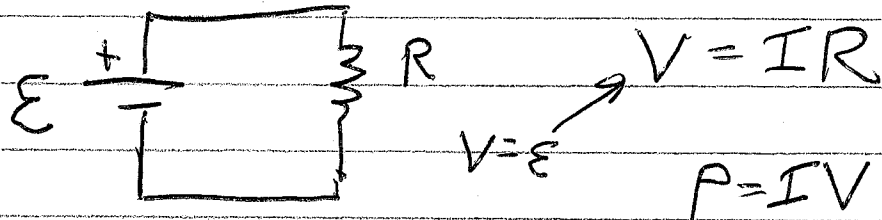



Basic Circuit w/ Ideal Battery



$\epsilon = \text{EMF} = \text{Voltage generated by battery.}$
 $R = \text{Resistance of Load}$

Series Configuration

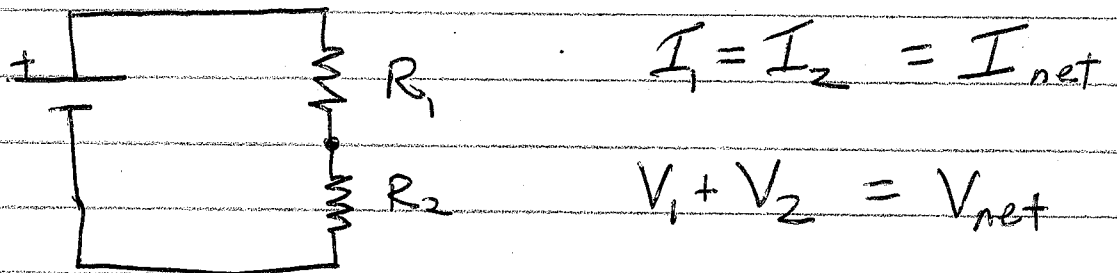- The current leaving one device has no choice but to go into the next.



- In series, devices have the same current.
- In series, the energy gained/lost by each charge adds/subtracts.

$$V_1 + V_2 = IR_1 + IR_2 = I(R_1 + R_2)$$


$$V_{net} = IR_{net}$$

$$\therefore R_{net} = R_1 + R_2$$

Resistance adds in series.



②

From the battery's perspective:

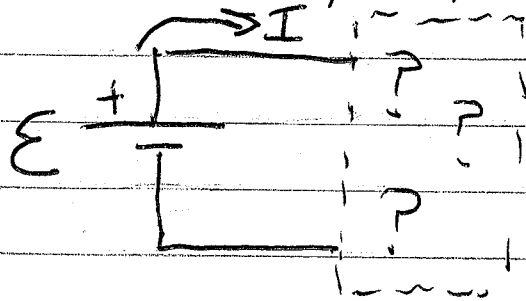

$$\text{Ex: } \mathcal{E} = 12 \text{ V} \quad R_{\text{net}} = \frac{12 \text{ V}}{0.1 \text{ A}} = 120 \Omega$$
$$I = 0.1 \text{ A}$$

Equivalent Circuits

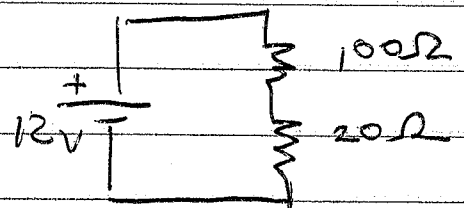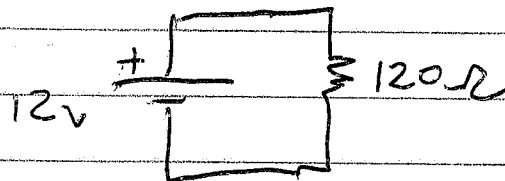

To analyze:

① $I = \frac{12 \text{ V}}{120 \Omega}$ in easy circuit.

② $I = 0.1 \text{ A}$ in the battery in both.

③ $V_1 = (0.1 \text{ A})(100 \Omega) = 10 \text{ V}$

$$V_2 = (0.1 \text{ A})(20 \Omega) = 2 \text{ V}$$

↙ "connected wire"

Note: $R_1 = 0$ in series does nothing

$R_1 = \infty$ in series forces $I = 0$.

↖ "broken wire"

3

Internal Resistance - A realistic battery has some built-in series resistance.

- R_{int} increases the circuit resistance, making I smaller.
- R_{int} causes voltage loss in the battery, depending on I .

$$V_{net} = V_1 + V_2$$
$$\mathcal{E} = V_{int} + V_{ext}$$

$$\mathcal{E} - V_{int} = V_{ext}$$
$$\mathcal{E} - IR_{int} = V_{ext}$$

Ex: $\mathcal{E} = 120 \text{ V}$

$$R_{int} = 1 \Omega$$

$$R_{ext} = 240 \Omega$$

$$\left. \begin{array}{l} R_{int} = 1 \Omega \\ R_{ext} = 240 \Omega \end{array} \right\} R_{net} = 241 \Omega$$

$$I = \frac{V}{R} = \frac{120 \text{ V}}{241 \Omega} = 0.498 \text{ A}$$

For the resistor $P = IV = (0.498)(119.5) = 59.5 \text{ W}$

$$V_{ext} = IR_{ext} = (0.498)(240) = 119.5 \text{ V}$$

- Ideal: $R_{int} = 0$ $I = 0.5 \text{ A}$ $P = 60 \text{ W}$
- I is a little smaller than ideal case.
- V_{ext} is a little smaller.
- P is a little smaller.

④

HW2-5

$$8.25 + 3.5 I_1 - 2.35 I_2 = 0$$

$$-2.2 I_1 + I_2 = 0$$

Simultaneous Equations

Manually, choose a method.

Method 1:

- Pick the easy eqn, solve for the easy variable.

$$I_2 = 2.2 I_1$$

- Substitute everywhere for this variable.

$$8.25 + 3.5 I_1 - 2.35 (2.2 I_1) = 0$$

Method 2: Find a way to add/subtract eqns to eliminate a variable.

$$(8.25)(2.2) + 3.5 I_1 (2.2) - 2.35 I_2 (2.2) = 0$$

$$-2.2 I_1 (3.5) + I_2 (3.5) = 0$$


Add:

$$(8.25)(2.2) - 2.35 I_2 (2.2) + I_2 (3.5) = 0$$

5

Parallel Configuration

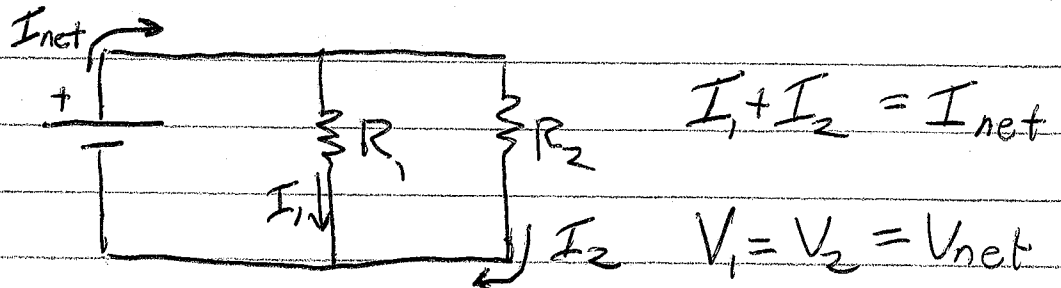- The circuit provides different branches for current to choose from.



- In Parallel, the current splits, and the branch currents add up to the total.
- The energy of each charge can only be lost in a single branch. No matter which branch is chosen, the voltage lost is the same.

$$I_1 + I_2 = I_{net}$$

$$\frac{V}{R_1} + \frac{V}{R_2} = \frac{V}{R_{net}}$$

$$\frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{R_{net}}$$

Resistors combine as inverses in parallel.