

① Phys 1402 2017-09-19 Lec 5

Electrostatic Force

$$F_E = q_0 E$$

Electric Field

$$E = \frac{kQ}{r^2}$$


In circuits,  $V$  means  $\Delta V$

DC Electricity

Current is rate of flow of charge.

$$I = \frac{\Delta Q}{\Delta t}$$

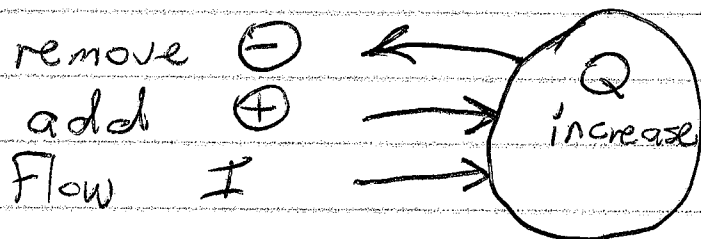If we had a metal ball, how could we make it more positive?



Current Flowing in is a synonym for:

- $\oplus$  Charges flowing in.
- $\ominus$  Charges flowing out.

In wires, only  $\ominus$  move.

②

Our DC Electricity always flows in circuits.

Resistors allow current to flow, with effort.

$$\text{Effort} = \text{Result} * \text{Difficulty}$$

$$V = I R$$

Voltage = (Current) (Resistance)

Electricity Carries Energy

$$\text{Power} = \frac{\text{Energy}}{\Delta t} = \left( \frac{\text{Energy}}{\text{Charge}} \right) \left( \frac{\text{Charge}}{\text{Time}} \right)$$

$$\text{Power} = P = V I$$

Ex: Flashlight w/ 3.0V Battery  
Current is 0.2 A.

Resistance is  $R = \frac{V}{I} = \frac{3.0V}{0.2A} = 15 \Omega$

Power is  $P = VI = (3.0V)(0.2A) = 0.6 W$

Power (P) is measured in watts (W).

③

Cost of Energy

\$0.12/kWh

$$\text{Power} = \frac{\text{Energy}}{\Delta t} \Rightarrow \text{Energy} = P \Delta t$$

In S.I. Units

On elec bill:

$$1 \text{ J} = (1 \text{ W})(1 \text{ s})$$

$$1 \text{ kWh} = (1000 \text{ W})(3600 \text{ s})$$

$$= 3.6 \text{ MJ}$$

Ex: Cost to leave a light on:

$$P = 9 \text{ W} \quad (\text{Reading Lamp})$$

$$\Delta t = 1 \text{ month}$$

$$= 30 \text{ days} \left( \frac{24 \text{ h}}{\text{day}} \right) = 720 \text{ hours}$$

$$\begin{aligned} \text{Energy} &= (9 \text{ W})(720 \text{ h}) = 6480 \text{ Wh} \\ &= 6.48 \text{ kWh} \end{aligned}$$

$$\begin{aligned} \text{Net Cost} &= \text{Amount} \cdot \text{Rate} \\ &= (6.48 \text{ kWh})(\$0.12/\text{kWh}) \\ &= \$0.78 \end{aligned}$$

9

Circuits consist of sources and loads.

Sources


- Wall outlet
- Battery
- Power Supply
- Generator

Loads

- Resistor
- Light Bulb
- Heater
- Motor
- Battery being charged.

Hooking up multiple loads.

Series

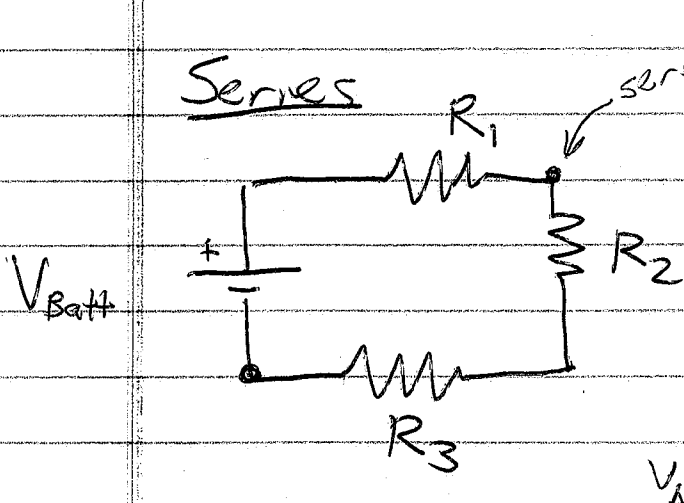

Current same everywhere.


$$I = I_1 = I_2 = I_3 = \dots$$

Voltage adds.

$$V_{Tot} = V_1 + V_2 + V_3 + \dots$$

Parallel

- Branches give charges a choice.

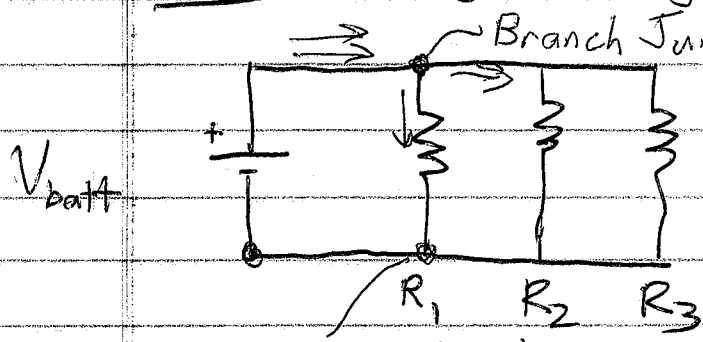

Voltage is the same

$$V = V_1 = V_2 = V_3 = \dots$$

Current adds


$$I_{tot} = I_1 + I_2 + \dots$$

Unbranch = Merge

⑤


# Measuring Current

Circuit


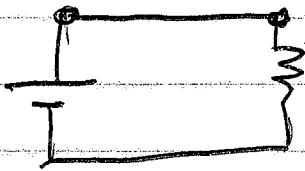


Replace  
1 wire



With Ammeter

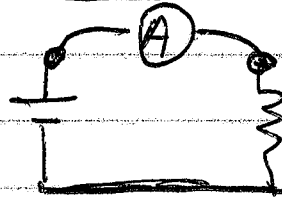

Break  
at Connection

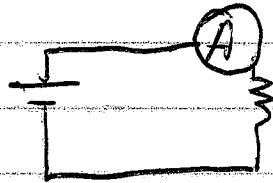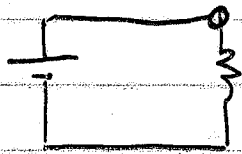

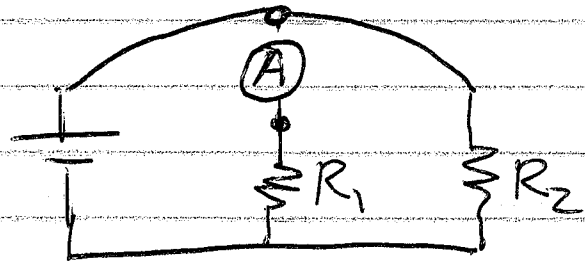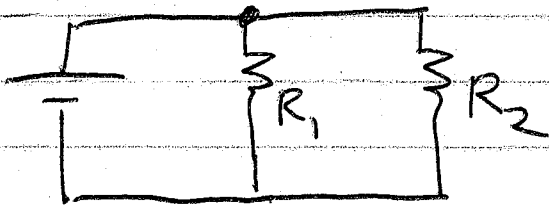Either way,  $(A)$  in series with  $\text{---}\text{---}$



Measuring  $I_1$

Measuring  $I_2$

