



①

Phys 1402



2017-10-17

Lec 13



## Cool Magnetic Effects

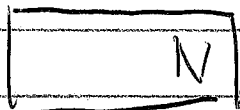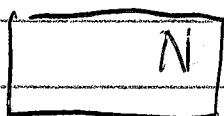

Attracted

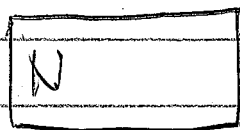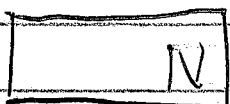


Repelled

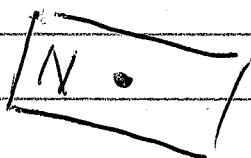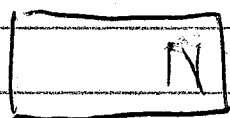


Flips then  
attracted

(pivoting)

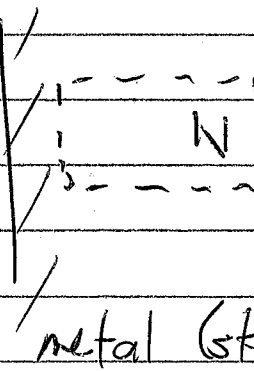

Induced temporary  
magnet


metal (steel)

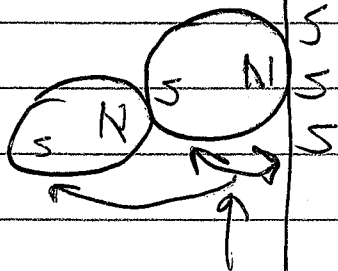

repulsion


②

Magnet falls slowly in a copper tube.

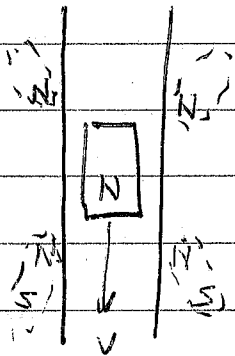
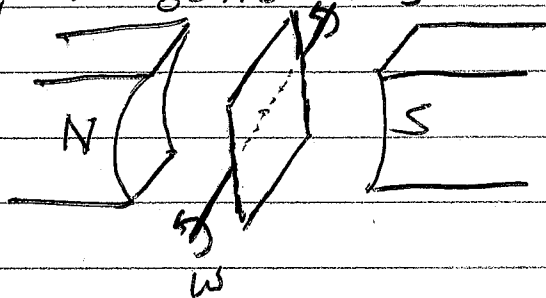
## AC Electricity

- Varying voltage causes varying  $I$ .
- Varying  $I$  causes varying  $B$ .
- Varying  $B$  generates voltage.
- Easy to generate.



Voltage Generated  $\mathcal{E} = NBA \omega \sin(\omega t)$

$\omega =$  rotation speed in rad/s

$f =$  rotation frequency in rot/s = rev/s = Hz


$$\omega = 2\pi f$$

$$\mathcal{E} = NBA 2\pi f \sin(2\pi f t)$$

$$= \mathcal{E}_{\max} \sin(2\pi f t)$$

Amplitude  $\rightarrow$

③

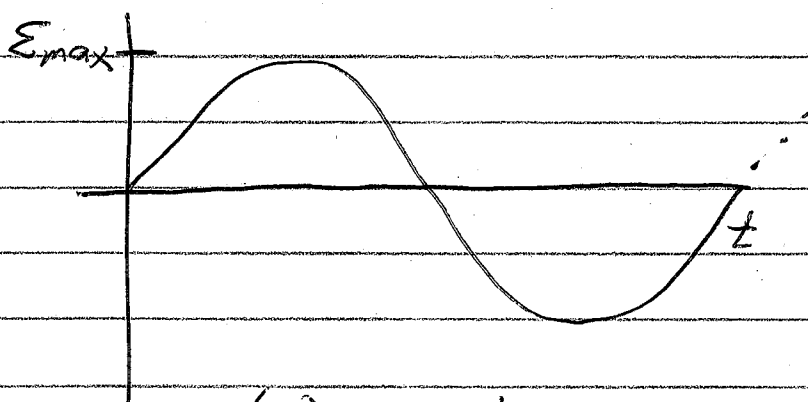

$\sin(\theta)$  repeats every  $2\pi = \theta$

$\sin(2\pi ft)$  repeats when  $2\pi = 2\pi ft$

$$\frac{1}{f} = t \quad \begin{matrix} 1 = ft \\ 1/t = f \end{matrix}$$

This special time is called the period symbolized by  $T$ .

$$f = \frac{1}{T}$$

### Resistors and AC

Mostly same as DC.

$$I(t) = \frac{V(t)}{R} = \frac{V_{max}}{R} \sin(2\pi ft)$$

$$= I_{max} \sin(2\pi ft)$$

Amplitudes obey Ohm's Law:  $V_{max} = I_{max} R$


Power:

④

## Resistor Power

$$P = VI = V_{\max} \sin(2\pi ft) I_{\max} \sin(2\pi ft)$$

$$= V_{\max} I_{\max} \sin^2(2\pi ft)$$

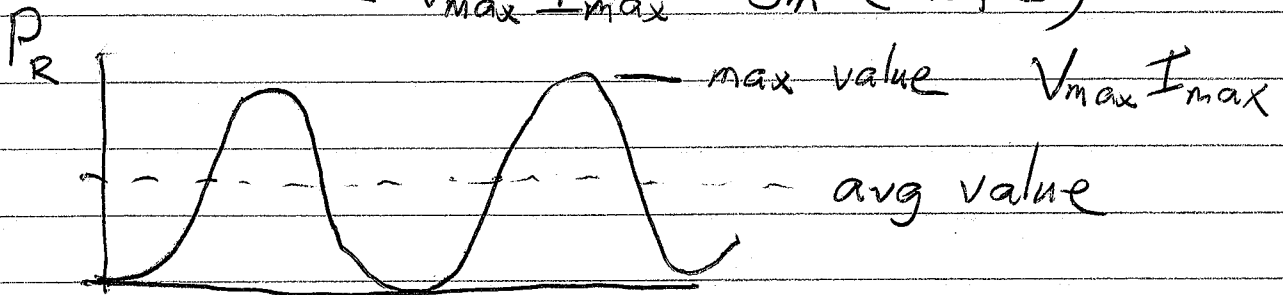

$$P_{\max} = V_{\max} I_{\max} = I_{\max}^2 R$$

$$\frac{\Delta \text{Energy}}{\Delta t} = P_{\text{avg}} = \frac{1}{2} P_{\max}$$

$$I_{\text{RMS}}^2 R = \frac{1}{2} I_{\max}^2 R$$

$$I_{\text{RMS}} = \frac{1}{\sqrt{2}} I_{\max}$$

$I_{\text{RMS}}$  is just another way to describe the amount of current.

It works in Ohm's Law

$$V_{\text{RMS}} = I_{\text{RMS}} R$$

$$V_{\text{RMS}} = \frac{V_{\max}}{\sqrt{2}}$$

In the US:  $V_{\text{RMS}} = 120 \text{ V}$

$$f = 60 \text{ Hz}$$


$$V(t) = (120 \text{ V}) \sqrt{2} \sin(2\pi (60 \text{ Hz}) t)$$

$$= (170 \text{ V}) \sin(377 t)$$

5A

# Capacitors in AC

$$Q = CV$$

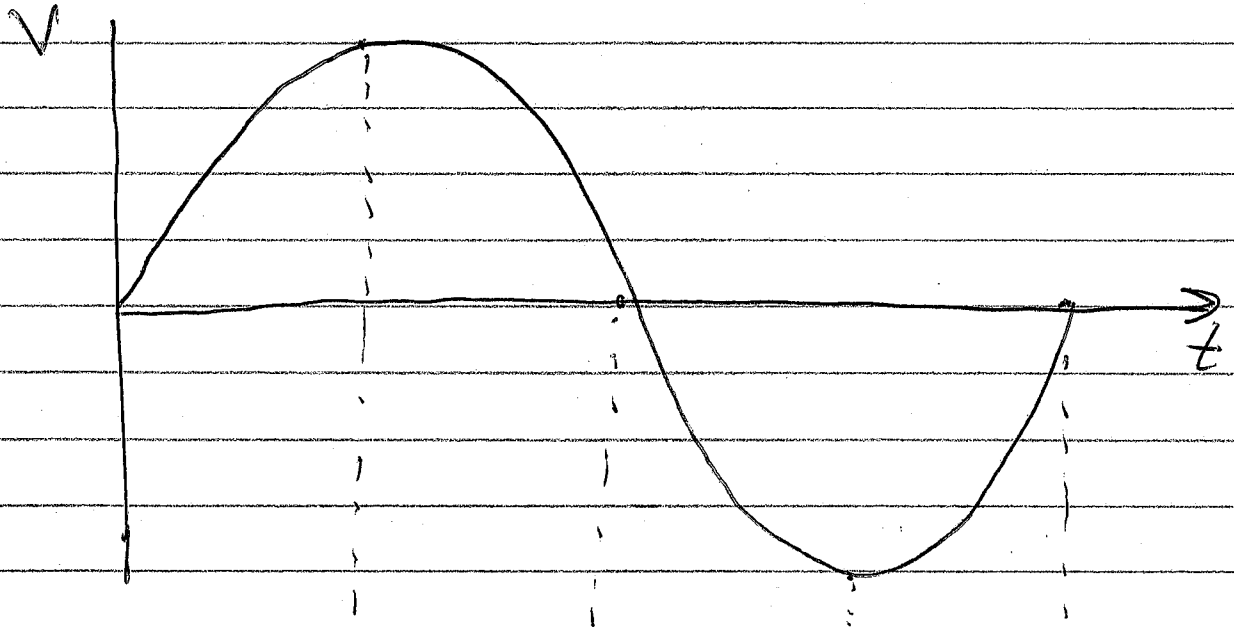

$$Q=0$$

$$Q=+Q_{max}$$

$$Q=0$$

$$Q=-Q_{max}$$

$$Q=0$$

Q increasing  
 $I = +I_{max}$

Q decreasing  
 $I = -I_{max}$

Q increasing  
 $I = +I_{max}$

$$I=0$$

$$Q = CV$$

Capacitor

$$I_{max} = 2\pi f C V_{max}$$