

Today

- Inductor & Capacitor together
- Transformers

AC Ohm's Law $V_{rms} = I_{rms} Z$

Impedance (Z) is like resistance for AC.

Resistor: $Z = R$

Inductor $Z = X_L = 2\pi f L$

Capacitor $Z = X_C = \frac{1}{2\pi f C}$

What happens when R , L , C are combined?

In general: Need different math.


In series: Can use vector math.

Resistors: $+x$ direction

Inductors: $+y$ direction

Capacitors: $-y$ direction

} these can cancel!

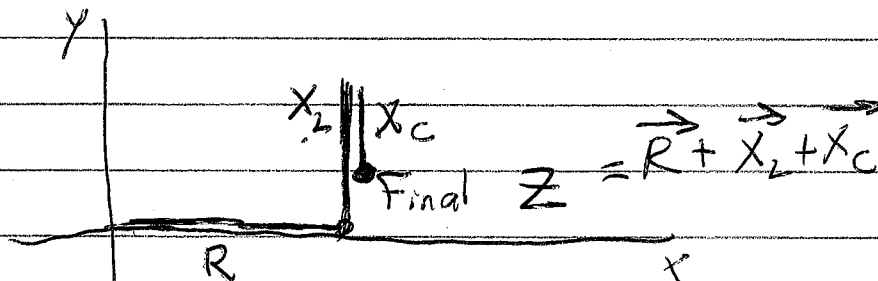

$$\left. \begin{array}{l} \text{Total } x: R \\ \text{Total } y: X_L - X_C \end{array} \right\} \text{Total } Z = \sqrt{R^2 + (X_L - X_C)^2}$$

②

Ex: $1\text{ k}\Omega$, 1.0 H , $1\text{ }\mu\text{F}$ in series

$$V_{\text{Tot}} = 140 \sin(500t) \quad I_{\text{rms}} = ?$$

$$V_{\text{max}} = (140\text{ V})$$

$$2\pi f = 500$$

$$f = 500 / (2\pi) = 79.6\text{ Hz}$$

$$V_{\text{rms}} = \frac{140\text{ V}}{\sqrt{2}} = 99\text{ V}$$

To find I_{rms} , use AC Ohm's Law

$$V_{\text{rms}} = I_{\text{rms}} Z$$

$$R = 1000\text{ }\Omega$$

$$(99\text{ V}) = I_{\text{rms}} (1803\text{ }\Omega)$$

$$X_L = 2\pi f L = 500\text{ }\Omega$$

$$I_{\text{rms}} = 0.0549\text{ A}$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{(500)(1 \times 10^{-6})}$$

$$= \frac{1}{0.0005} = 2000\text{ }\Omega$$

Total Reactance

$$X = X_L - X_C = -1500\text{ }\Omega$$

$$Z = \sqrt{1000^2 + 1500^2} = 1803\text{ }\Omega$$

Power in AC: Only the resistor!

$$P = V_R I_R = I^2 R = (0.0549\text{ A})^2 (1000\text{ }\Omega) = 3.02\text{ W}$$

$$\text{Compare to } (99\text{ V})(0.0549\text{ A}) = 5.4\text{ VA}$$

VA Rating \rightarrow

③

Since $X = X_L - X_C$, $X = 0$ is possible.

Cause :

$$X_L = X_C$$

$$2\pi f L = \frac{1}{2\pi f C}$$

$$(2\pi f)^2 L = \frac{1}{C}$$

$$(2\pi f)^2 = \frac{1}{LC}$$

$$2\pi f = \frac{1}{\sqrt{LC}}$$

$$\text{Resonant freq: } f = \frac{1}{2\pi \sqrt{LC}}$$

For 1.0 H , $1 \mu\text{F}$

$$f = \frac{1}{2\pi \sqrt{(1.0)(1 \times 10^{-6})}} = 159 \text{ Hz}$$

If we changed to the resonant freq with the same voltage... ($R = 1000 \Omega$)

Effect: $X = X_L - X_C = 0$


$$Z = \sqrt{R^2 + X^2} = \sqrt{R^2} = R$$

$$I_{\text{rms}} = \frac{V_{\text{rms}}}{Z} = \frac{99 \text{ V}}{1000 \Omega} = 0.099 \text{ A}$$

More Current!

④

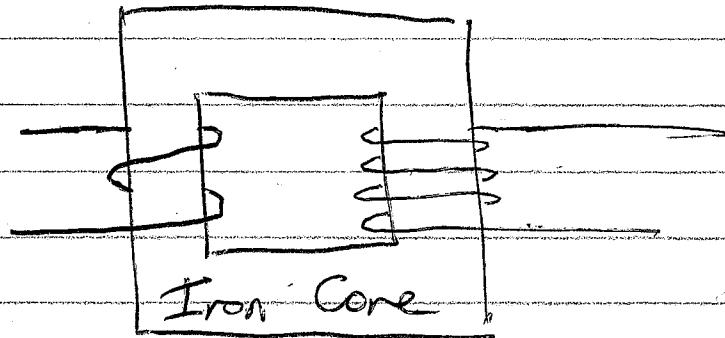Transformers - two coils with interconnected magnetic fields.



Apply voltage to one coil. This is the primary.
Current flows in the primary.

~~If the current is AC~~

The current causes B in the iron core.
Both coils "feel" the magnetic flux.

$$\text{Flux per loop: } \Phi = BA$$

$$\begin{array}{l} \text{Primary Flux } \Phi_p = N_p BA \\ \text{Secondary Flux } \Phi_s = N_s BA \end{array}$$

If the current is AC, the flux is AC
and it generates EMF.


EMF depends on flux proportionally.

$$\frac{E_s}{E_p} = \frac{\Phi_s}{\Phi_p} = \frac{N_s BA}{N_p BA} = \frac{N_s}{N_p}$$

Current? $E_p I_p = E_s I_s$ (Ideally)

⑤

Ex: Transformer in a cell phone charger

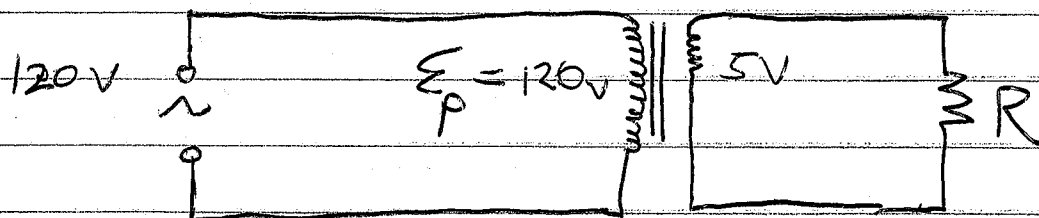

IF $N_s = 100$, what is N_p ?

$$\frac{E_s}{E_p} = \frac{N_s}{N_p}$$

~~$$\frac{120V}{5V} = \frac{100}{N_p}$$~~

$$\frac{5V}{120V} = \frac{N_s}{N_p}$$

~~$$120 N_p = (100)(5)$$~~

~~$$N_p = \frac{(100)(5)}{120} = 4.1\bar{6}$$~~

$$5 N_p = (120)(100)$$

$$N_p = \frac{(120)(100)}{5} = 2400$$

More voltage in primary \rightarrow more loops in primary

IF $I_R = 1.5 A$, what is I_p ?

$$E_p I_p = E_s I_s$$
$$(120V) I_p = (5V)(1.5A)$$

$$I_p = \frac{5}{120} (1.5A) = 0.0625 A$$