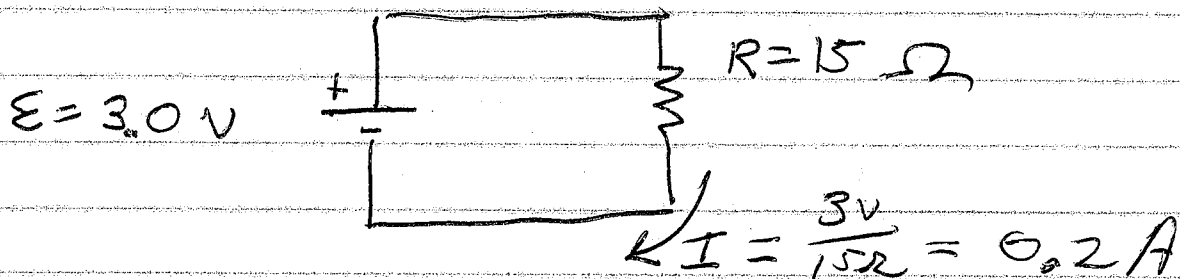


① Phys 1402 2017-07-11 Lec 5

Applying voltage across something pushes current through the thing.

Ex: Flashlight



In the resistor, current flows  $\oplus$  to  $\ominus$ .

It could be  $\oplus$  flowing  $\oplus$  to  $\ominus$ ,  
or  $\ominus$  flowing  $\ominus$  to  $\oplus$ .

Either way, the current is the same direction.

### Drift Velocity

- Actual charges move slowly.  $\sim 1 \text{ mm/s}$ .
- Effect of electricity is fast  $\sim 300 \text{ Mm/s}$

Calculating drift velocity

$$\Delta Q = I \Delta t$$

$$Q = \rho l A$$

$\rho$  charge/volume

$$v = l / \Delta t$$

$$v = \frac{I}{\rho A}$$

②

Ex: Copper has  $10^{28}$  electrons /  $m^3$

$$\rho = (1.6 \times 10^{-19} \text{ C}) (10^{28} \text{ per } m^3) \\ = -1.6 \times 10^9 \text{ C/m}^3 \quad (1000 \text{ C/cm}^3)$$

radius  $r = 1 \text{ mm}$

current  $I = 1.0 \text{ A}$

$$v = \frac{I}{\rho A} = \frac{(1.0 \text{ A})}{(-1.6 \times 10^9 \text{ C/m}^3) (\pi (0.001 \text{ m})^2)} \\ = -0.0002 \text{ m/s} = -0.2 \text{ mm/s}$$

Very slow and opposite to dir of current.

Resistivity (See Ohm's Law prelab)

- Intrinsic version of resistance, (Independent of shape & size)

$$R = \frac{\rho l}{A}$$

resistivity


- Longer  $\rightarrow$  more  $R$
- Thinner  $\rightarrow$  more  $R$

3

## Components in combination
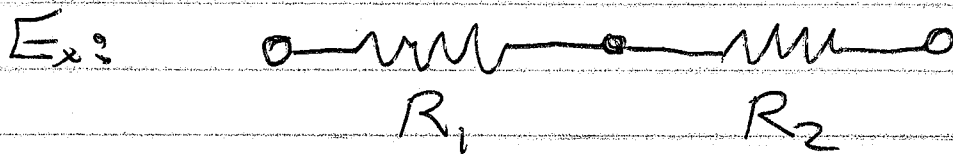
### Building Blocks:

Series • Two things connected at one junction with no fork in between.



• All current that goes thru  $R_1$  must also go thru  $R_2$ .

Series:  $I_1 = I_2 = \dots$

- Each component takes some energy from each charge.
- Each component takes (or gives) some voltage.

Series  $V_{\text{Tot}} = V_1 + V_2 + \dots$

• Effective resistance (equivalent  $R$ )




$$R_{\text{eq}} = \frac{V_{\text{Tot}}}{I} = \frac{(V_1 + V_2 + \dots)}{I} = \frac{IR_1 + IR_2 + \dots}{I}$$

Series  $R_{\text{eq}} = R_1 + R_2 + \dots$

④

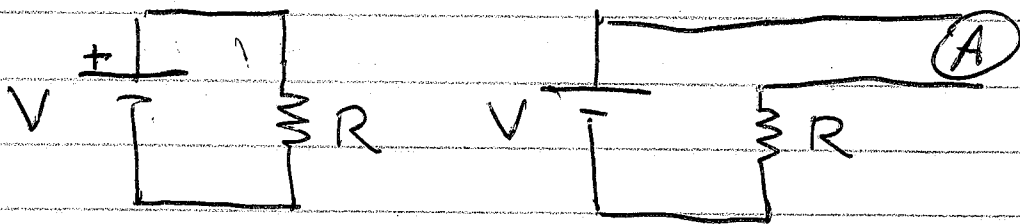
## Measuring Things

- Our instrument must have the same value as the experiment.
- In series, components have the same  $I$ .
- Use series to measure current.




- All current of the Ammeter goes thru  $R$ .
- When we measure, we don't want to disturb the circuit.
  - $V_{\text{Tot}} = V_{\text{meter}} + V_R$
  - Need  $V_{\text{meter}} \approx 0$ ,  $V_R$  is the same in both circuits.
  - How? ~~R~~ Ammeter is a wire w/  $R=0$ .
- Current flows freely thru Ammeter.

Incorrect Hookup

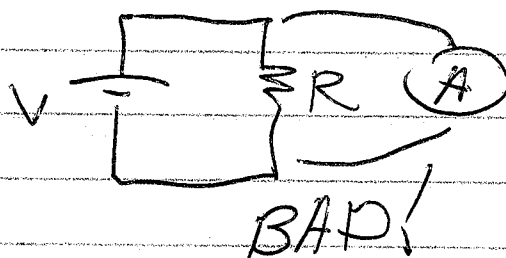

5

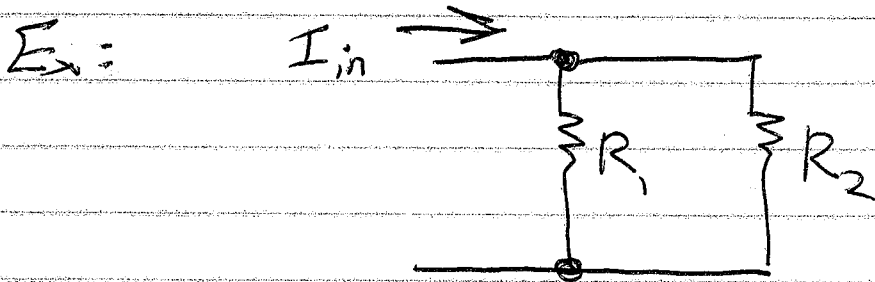Parallel • Components connected at both ends,



- Any given charge could take either path. Either way, the voltage must be the same.

Parallel:  $V_1 = V_2 = \dots$

- The charges that enter ( $I_{in}$ ) must choose a path ( $R_1$  or  $R_2$ ). So the count of charges in each path adds up to the total.

Parallel:  $I_{tot} = I_1 + I_2 + \dots$

- The equivalent is more complex:

$$R_{eq} = \frac{V}{I_{tot}} = \frac{V}{I_1 + I_2 + \dots} = \frac{V}{\frac{V}{R_1} + \frac{V}{R_2} + \dots}$$

$$R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots} = \left( \frac{1}{R_1} + \frac{1}{R_2} + \dots \right)^{-1}$$


⑥

Series Resistors Add.

If one is HUGE, it dominates the total.  
Adding a tiny value doesn't do much.

Parallel Resistors Add Inversely.

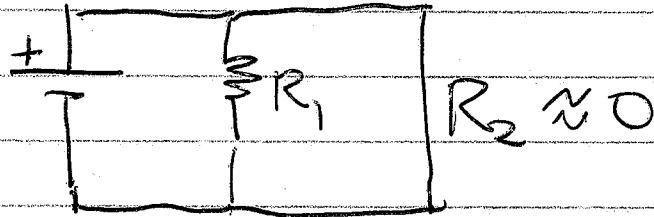
- A tiny resistor has a HUGE inverse.  
A tiny  $R$  in parallel dominates.  
Ex: Short Circuit.



$$R_{eq} = \left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1} = \left( \frac{1}{R_1} + \infty \right)^{-1} = \frac{1}{\infty} = 0$$

All current takes the  $R=0$  path.

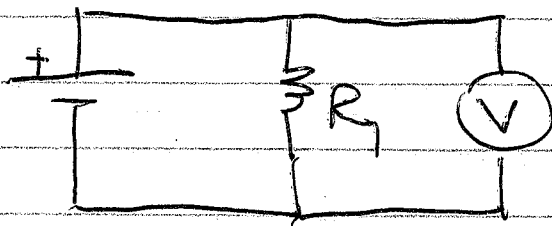- A HUGE  $R$  in parallel has a tiny inverse




- Same Voltage
- No current in  $V$
- $V$  huge  $R$

②
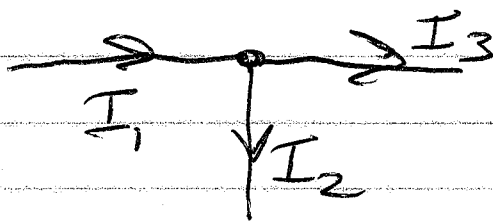
## Kirchoff's Laws

- Generalization of series & parallel Laws for  $I$  and  $V$ .

- Current Law - what goes in must come out.



$$I_1 = I_2 + I_3$$

- Voltage Law - what goes up must come down


Up  $\rightarrow$  positive  $\Delta V$

Down  $\rightarrow$  negative  $\Delta V$

Pick any loop. Find  $\Delta V$ 's, even if they have variables in them. Write their total and set it equal to zero.

Battery:  $\Delta V = \pm \mathcal{E}$

Resistor:  $\Delta V = \pm IR$

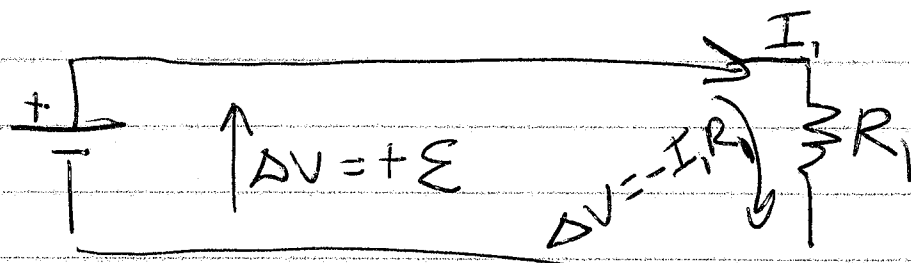

$$\Delta V_B + \Delta V_R = 0$$

$$+\mathcal{E} - I_1 R_1 = 0$$

$$\mathcal{E} = I_1 R_1$$

$$I_1 = \mathcal{E} / R_1$$

SerCP10 18.P.017. (3487981)

Test / Preview

Code

## Previewer Tools


Show New Randomization

Open in Editor

Print Show: All, None  Key  Solution  Help/Hints Mark  Answer Format Tips

The ammeter shown in the figure below reads 2.08 A. Find  $I_1$ ,  $I_2$ , and  $\mathcal{E}$ . (Assume  $R = 6.90 \Omega$ .)

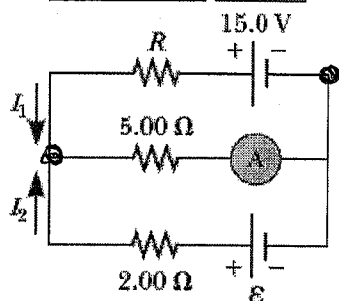$I_1 =$   A  
 $I_2 =$   A  
 $\mathcal{E} =$   V



$$\text{Left node: } I_1 + I_2 = (2.08 \text{ A})$$

$$\text{Top Loop: CCW from upper-right corner}$$

$$(+15 \text{ V}) - I_1 R - (2.08 \text{ A})(5.0 \Omega) = 0$$

$$(15 \text{ V}) - (10.4 \text{ V}) = I_1 (6.90 \Omega)$$

$$\frac{4.6 \text{ V}}{6.9 \Omega} = I_1 = 0.667 \text{ A}$$

## Question Details

Name (QID): SerCP10 18.P.017. (3487981)

Usable/Draft: Usable

Locked: Yes

Mode: Numerical

Author: WebAssign Staff (support@webassign.net)

Permission: Copyright

## Textbook

Serway and Vuille, "College Physics", ed.10

## Chapter

18

Last Saved: Dec 16, 2015 09:30 AM CST