


Phys 1402

2017-07-12

Lec 6

## RC Circuits


We know  $Q = CV$  for a capacitor

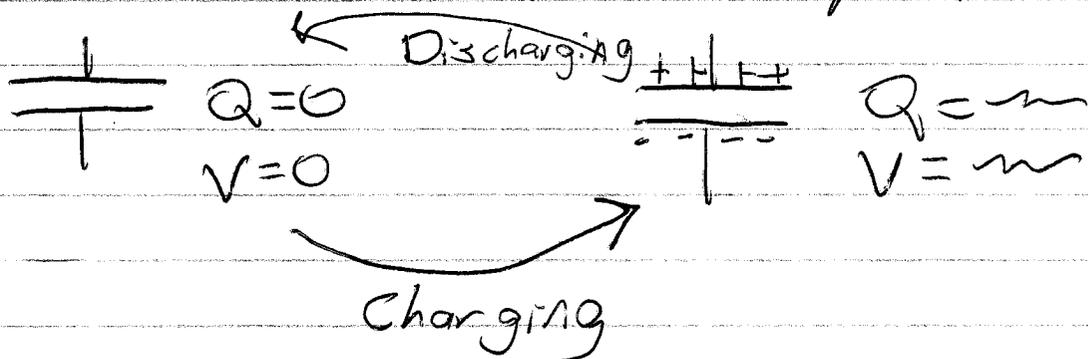

Discharge - starting with a "Full" capacitor,  
 $V =$  as much as we can give it.

Phet Circuit Construction Kit (AC+DC)

Measure Voltage while Discharging

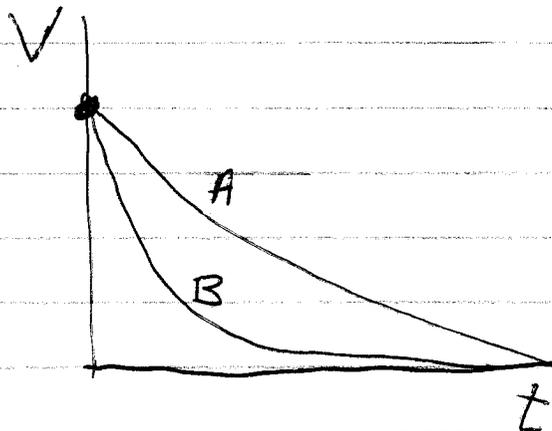

A = Slower, more time  
B = Faster, less time

Shape is Exponential Decay

$$V(t) = V_0 \exp(-t/\tau)$$

Initial Value  $\uparrow$

$\tau$  Time Constant

②

What is  $\exp(-t/\tau)$ ?

Also written  $e^{-t/\tau}$

$t/\tau$	$e^{-t/\tau}$	
0	1	100%
1	0.37	37%
2	0.14	14%
3	0.05	5%
4	0.02	2%
5	0.01	1%
6	0.00	0%



How much charge is left, fractionally?

How many time constants have gone by?

Ex:  $t/\tau = 2$      $t = 2\tau$

This is "two time constants".

How long does it take to be 50% done?  
Inverse of exponential is natural log.


$$e^{-t/\tau} = 0.5 \rightarrow -t/\tau = \ln(0.5) = -0.693$$

#  $\ln()$  both sides  $t = 0.693 \tau$

③

"How Fast" can mean two things:

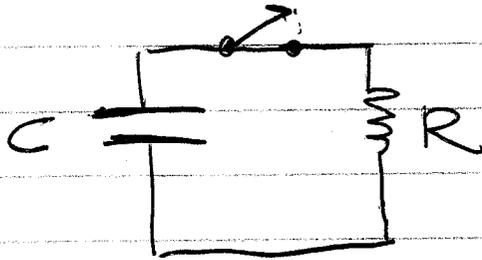- Relative measurements.  
It takes 0.7 time constants to drain half way.
- Absolute measurements.



Initially, cap is "charged".

When connected, current flows.

Constants:

$$C = 0.2 \text{ F}$$

$$R = 10.0 \Omega$$

$$\tau = RC$$

$$= (10.0 \Omega)(0.2 \text{ F})$$

$$= 2.0 \text{ s}$$

Eventually, the capacitor is "empty"

In between, everything decreases exponentially.

Variables:

$$V_c = V_0 e^{-t/\tau}$$

$$Q = Q_0 e^{-t/\tau}$$

$$I = I_0 e^{-t/\tau}$$

$$V_R = V_c$$

$$Q = VC \leftarrow \text{capacitance}$$

$$V = IR$$

$$Q_0 = V_0 C$$

$$V_0 = I_0 R$$

Ex:  $V_0 = 10.0 \text{ V}$

$$10.0 \text{ V} = I_0 (10.0 \Omega)$$

$$Q_0 = (10.0 \text{ V})(0.2 \text{ F})$$

$$1.0 \text{ A} = I_0$$

$$Q_0 = 2.0 \text{ C} \leftarrow \text{coulombs}$$

4

What is the current at  $t = 7.0 \text{ s}$ ?

$$I = I_0 e^{-t/\tau}$$

$$\frac{t}{\tau} = \frac{7.0 \text{ s}}{2.0 \text{ s}} = 3.5$$

$$e^{-t/\tau} = e^{-3.5} = 0.03$$

$$\begin{aligned} I &= (1.0 \text{ A})(0.03) \\ &= 0.03 \text{ A} = 30 \text{ mA} \\ &= 30 \times 10^{-3} \text{ A} = \end{aligned}$$

How long to get below  $1.0 \text{ V}$ ?

$$V = V_0 e^{-t/\tau}$$

$$\frac{V}{V_0} = \frac{1.0 \text{ V}}{10 \text{ V}} = 0.1 = e^{-t/\tau}$$

$$\ln(0.1) = -t/\tau$$

$$-2.3 = -t/\tau$$


$$t = 2.3 \tau$$

$$= 2.3 (2.0 \text{ s})$$

$$= 4.6 \text{ s}$$

⑤

How is "charging" different?

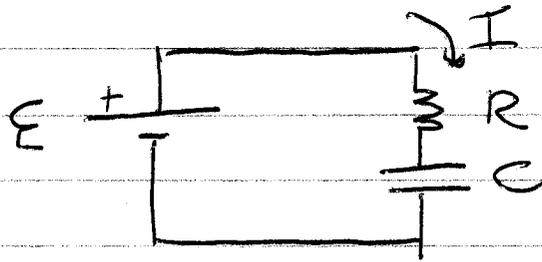

Kirchoff's Law for Voltage



CW Loop

$$\mathcal{E} - IR - V_C = 0$$

$$\mathcal{E} = IR + V_C$$

Initial:  $\mathcal{E} = I_0 R + 0$

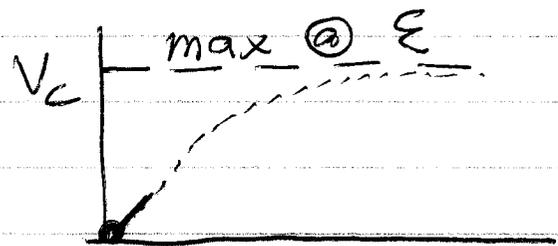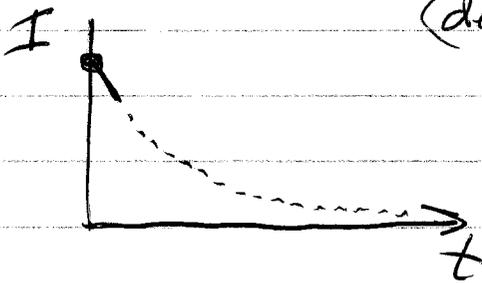Next:  $\mathcal{E} = IR + V_C$   
 (same)  $\uparrow$  (decreases) (increase)



99% @  $t = 5\tau$

$$I = I_0 e^{-t/\tau}$$

$$V_C = \mathcal{E} (1 - e^{-t/\tau})$$

$$V_R = \mathcal{E} e^{-t/\tau}$$

$$Q = Q_{\max} (1 - e^{-t/\tau})$$

Kirchoff Eventually:  $\mathcal{E} = 0 + \mathcal{E}$

①

Ex:  $C = 250 \mu\text{F}$   
 $\mathcal{E} = 12 \text{ V}$

Want to get to 10.0 V on capacitor in 5.0 s. What R? Charging

$$V_c = \mathcal{E} (1 - e^{-t/\tau})$$

$$(10.0 \text{ V}) = (12.0 \text{ V}) (1 - e^{-t/\tau})$$

$$\frac{10}{12} = 0.833 = (1 - e^{-t/\tau})$$

$$e^{-t/\tau} = 1 - 0.833 = 0.167$$

ln() both:  $-t/\tau = -1.79$

$$\frac{-5.0 \text{ s}}{\tau} = -1.79$$

Mult by  $\tau$ ,  
div -1.79

$$\frac{-5.0 \text{ s}}{-1.79} = \tau = 2.79 \text{ s}$$

$$\tau = RC$$

$$(2.79 \text{ s}) = R (250 \times 10^{-6} \text{ F})$$

$$\frac{2.79 \text{ s}}{250 \times 10^{-6} \text{ F}} = 11200 \Omega = 11.2 \text{ k}\Omega = R$$

$$e = 1.6 \times 10^{-19} \text{ C} = 1.6 \text{ e-19 C}$$

Careful:  $e = 2.718$