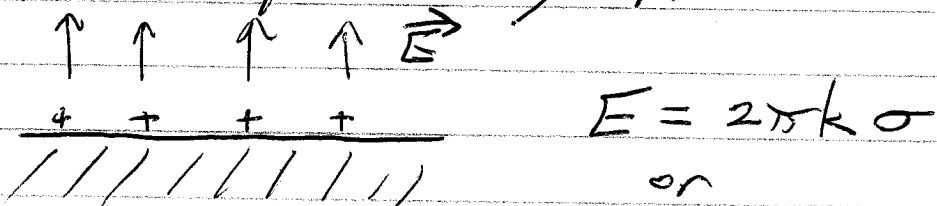


Phys 1402

2017-07-13

~~Exam~~ Quiz 1 #16

Metal w/ $+1.5 \mu\text{C}/\text{m}^2$ on surface.



$$E = 2\pi k \sigma$$

or

$$E = 4\pi k \sigma$$

$\sigma =$ charge per area

" $2\pi k \sigma$ " has E split above & below surface. But here, there is metal below w/ $E = 0$. Must use " $4\pi k \sigma$ " version.

$$E = 4\pi k \sigma = 4\pi \left(9 \times 10^9 \frac{\text{Nm}^2}{\text{C}^2}\right) \left(1.5 \times 10^{-6} \frac{\text{C}}{\text{m}^2}\right)$$

$$= 1.7 \times 10^5 \text{ N/C}$$

$$= 170000 \text{ N/C}$$

Ways to calculate E :

Point $E = \frac{kq}{r^2}$


$$|E| = \frac{\Delta V}{\Delta x}$$

Line $E = \frac{2k\lambda}{r}$


Surface $E = \begin{cases} 2\pi k \sigma \\ 4\pi k \sigma \end{cases}$

②

Quiz 1 #11
Negative Balloon


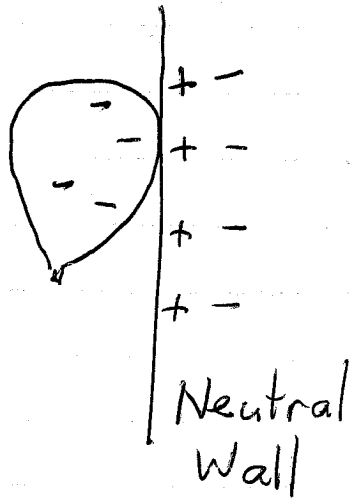


Positive Balloon

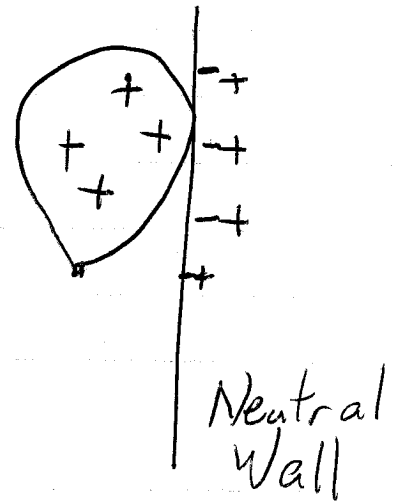


Wall gets polarized by charged balloon.

Compare Magnet & refrigerator

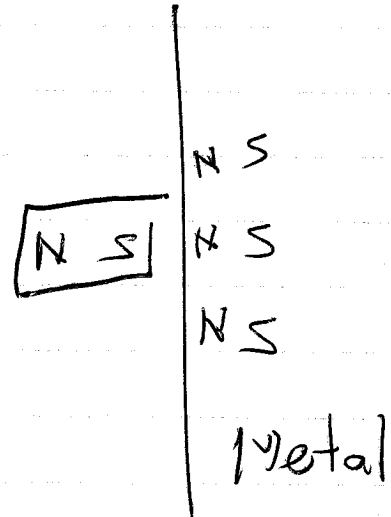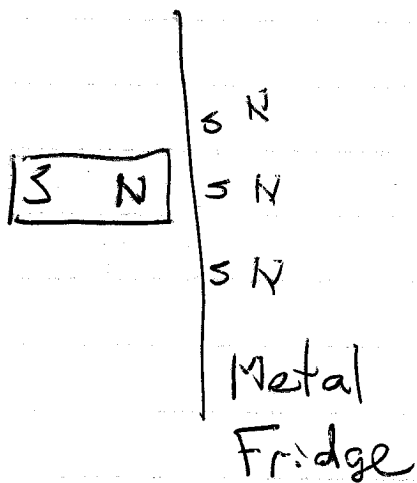

③


Quiz 1 #22

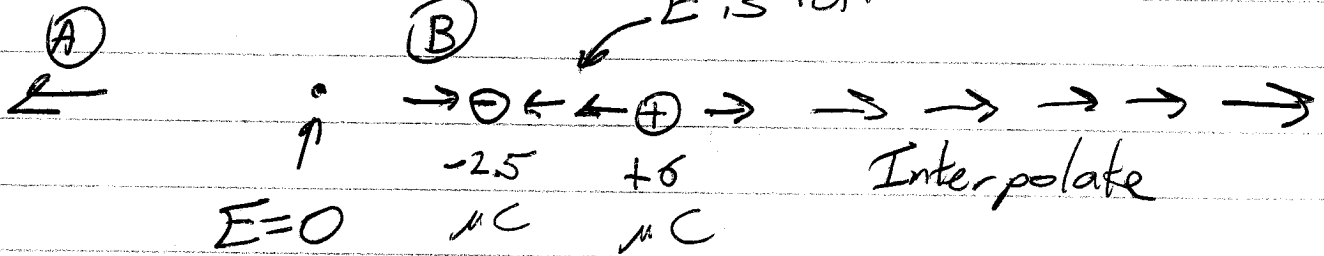


Total $Q = +6 - 2.5 = +3.5 \mu\text{C}$

"Far away" the charges "look like" a single $+3.5 \mu\text{C}$ charge, so far away, E points away.

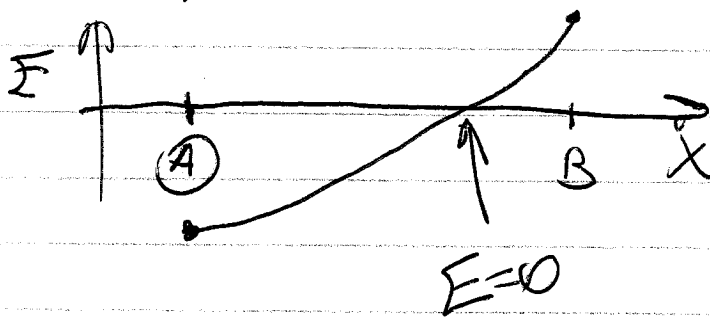At A, E points away from total $+3.5 \mu\text{C}$
 At B, E points toward $-2.5 \mu\text{C}$



#19

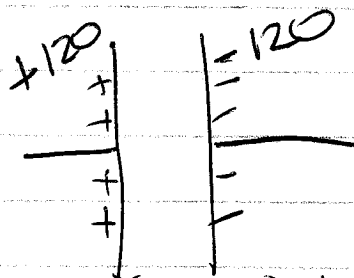


Total = 0

#18

$Q = CV = (15 \mu\text{F})(8.0\text{V}) = 120 \mu\text{C}$

#20 $\frac{1}{2} CV^2 = \frac{1}{2} (15 \mu\text{F})(8\text{V})^2 = 480 \mu\text{J}$

4

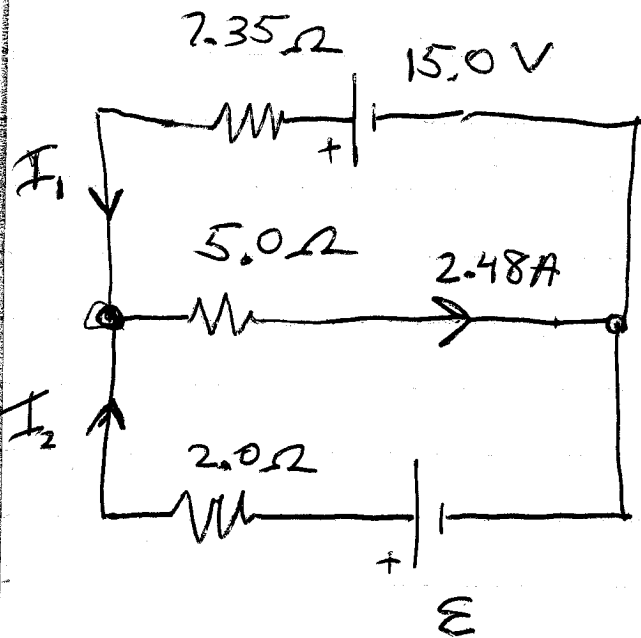

For 5Ω resistor:

$$V = IR = (2.48 \text{ A})(5.0 \Omega) = 12.4 \text{ V}$$

Voltage of 7.35Ω

The top segment has total ΔV of $15.0 \text{ V} + V_7$
 It's in parallel w/ middle segment 12.4 V

Therefore $V_7 = -2.6 \text{ V}$

Same thing by Kirchoff: Top Loop, CCW



$$+(15.0 \text{ V}) - (7.35 \Omega)I_1 - (12.4 \text{ V}) = 0$$

$$15 - 12.4 = 7.35 I_1$$

$$2.6 = 7.35 I_1$$


$$I_1 = 2.6 / 7.35 = 0.354 \text{ A}$$

• Batt

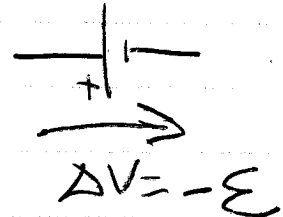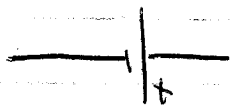

3

• Resistor

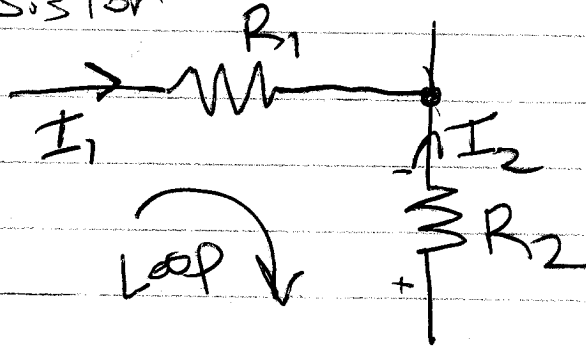

$$\Delta V = \dots - I_1 R_1 + I_2 R_2 \dots = 0$$

Loop with I_1

Loop against I_2

Solve for I_2 in example

$$I_1 + I_2 = 2.48 \text{ A}$$

$$(0.354 \text{ A}) + I_2 = 2.48 \text{ A}$$

$$I_2 = 2.13 \text{ A}$$

Lower Loop - CW


$$+\mathcal{E} - (2.13 \text{ A})(2.0 \Omega) - 12.4 \text{ V} = 0$$

$$\mathcal{E} - (4.26 \text{ V}) - 12.4 \text{ V} = 0$$

$$\mathcal{E} - 16.7 \text{ V} = 0$$

$$\mathcal{E} = 16.7 \text{ V}$$

⑧

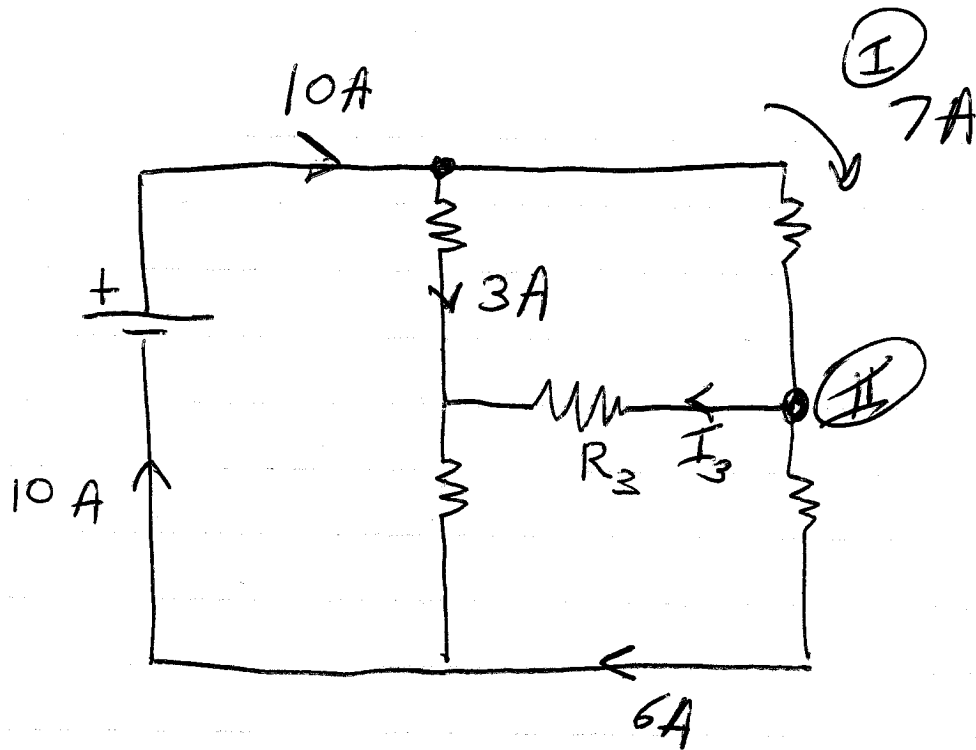



Current in R_3 ?

- 0A
- 1A
- 2A
- 3A

① $10A = \text{I} + 3A$
7A is going all the way across the top.

② 7A splits and 1A goes to R_3
 $7A = 6A + I_3$

②

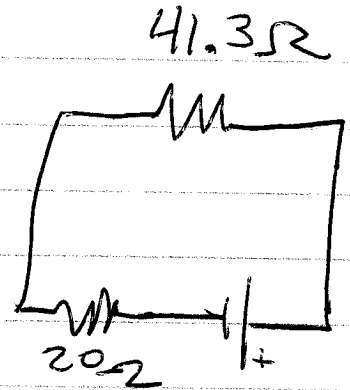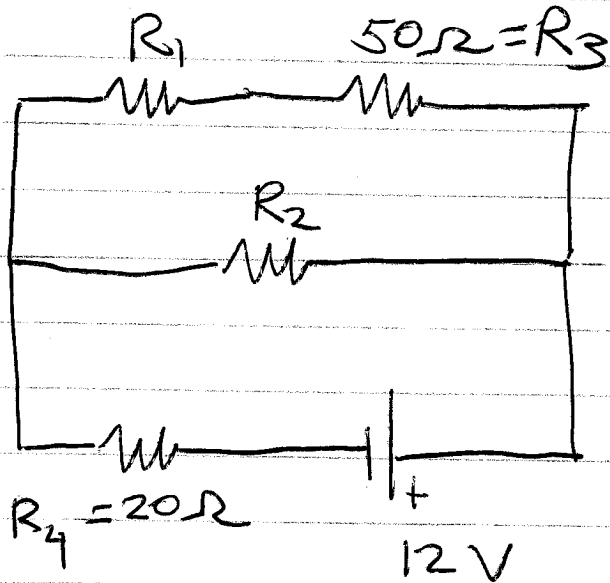

What	V	I	R	P
R_1			38Ω	
R_2	8.09		78Ω	
R_3			50Ω	
R_4		0.196	20Ω	

Overall 12.0V $\frac{12}{61.3} = 0.196$ 61.3

R_{13} 8.09 Ω 88Ω
 R_{123} 8.09 Ω 0.196 41.3Ω

~~R_{1234}~~

↖ "same" current in series

$$R_{123} = \left(\frac{1}{88} + \frac{1}{78} \right)^{-1} = 41.3\Omega$$

$$R_{\text{overall}} = 41.3 + 20 = 61.3\Omega$$