


① Phys 1402

2017-07-25

lec 13
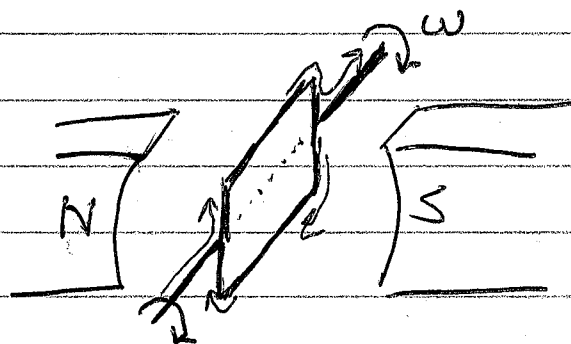
## AC Electricity

Why? Easy to generate.  
Works with transformers.




$$\Phi_B = NBA \cos(\omega t)$$

$$\mathcal{E}_{\max} = NBA \omega \quad (\text{Amplitude})$$

$$\mathcal{E} = \mathcal{E}_{\max} \sin(2\pi f t)$$

↑  
 $\sin()$  or  $\cos()$

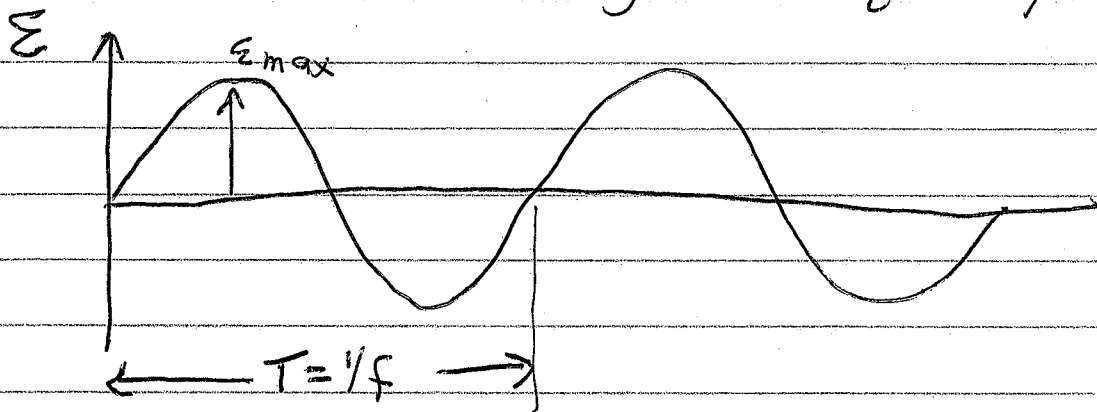$\omega = 2\pi f = \text{angular frequency}$



②

## Transformers

Primary - Apply voltage here.

Energy goes in.

Current flows because of applied voltage.

Low  $R$ , so current could be huge.

$I$  causes  $B$ .

$\Phi = NBA$  is magnetic flux (total)

IF input voltage is DC  $\Rightarrow$  Bad!  
(Only a little  $R$  to limit current.)

IF input voltage is AC:

$I$  varies

$B$  varies

$\Phi$  varies

Changing  $\Phi$  makes "Back EMF".

This reduces the effective voltage.

which limits the current.

## Secondary

$B$  from primary is "felt"

$\Phi = NBA$  is flux.

$\uparrow \uparrow$  specific values for secondary.

$\mathcal{E}$  is proportional to  $N_s$


③

Ratio of  $\mathcal{E}$ 's:

$$\frac{\mathcal{E}_s}{\mathcal{E}_p} = \frac{N_s}{N_p}$$

Reminder: IF flux isn't changing - no EMF

Side Effect - Isolation

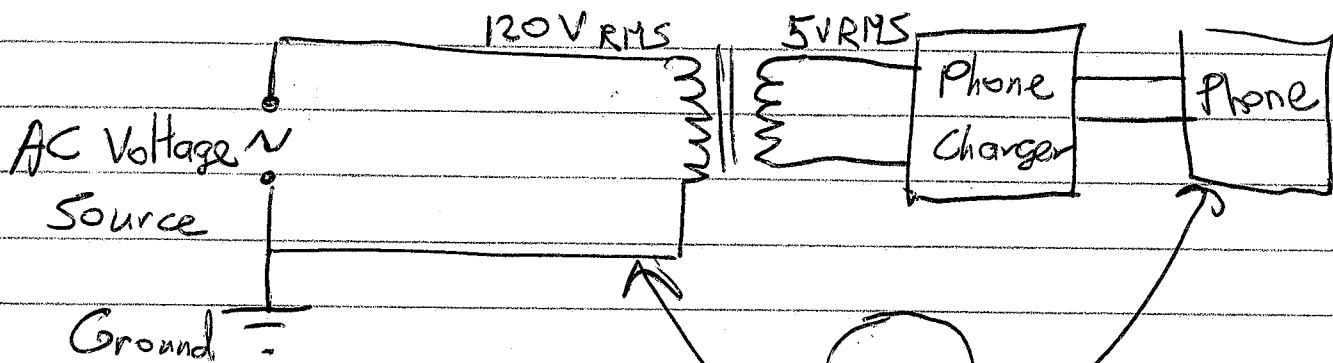

Usually: Phone isolated from ~~charger~~ "Mains"

- Cheap charger?
- Touching plug?
- Damp skin? - makes 120V deadly
- Frayed wires

④

## Circuits in AC

Resistors - Same as DC


$$V_{rms} = I_{rms} R$$

Power is also similar:

$$P_{avg} = V_{rms} I_{rms}$$

$$P_{avg} = I_{rms}^2 R$$

Inductors - oppose changing current

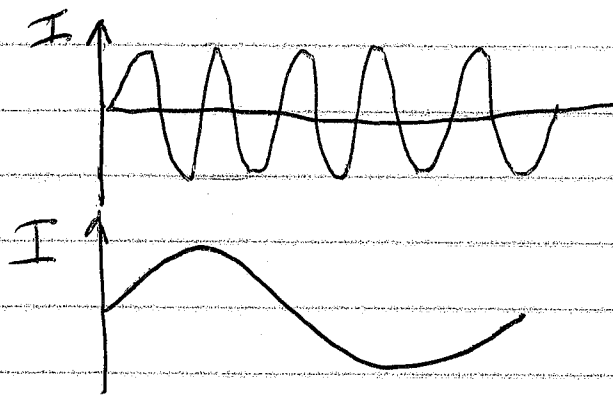

Fast change  
Needs more voltage

Slow change  
Needs less voltage.

frequency describes rapidness of change,

$$V_{rms} = I_{rms} \underbrace{2\pi f L}_{\text{Inductive Reactance}}$$

$$V_{rms} = I_{rms} X_L$$

Inductive Reactance  
( $X_L$ )

Capacitors - charging takes time,

without allowing time, current flows  
back and forth,

③

Quickly varying AC flows  
with low voltage,

$$V_{rms} = I_{rms} \left( \frac{1}{2\pi f C} \right)$$

$$V_{rms} = I_{rms} X_C$$

Capacitive Reactance  
( $X_C$ )

Review:

$$V_{rms} = I_{rms} R$$


$$V_{rms} = I_{rms} X_L$$

$$V_{rms} = I_{rms} X_C$$

$$V_{rms} = I_{rms} Z$$

$Z = \text{Impedance} = \text{like resistance for AC}$


Example of capacitor:

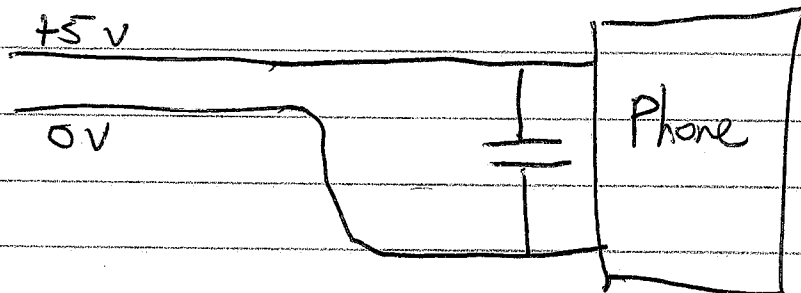

- Any stray AC goes thru capacitor.
- The DC power goes into the phone.

8

## Series AC Circuit

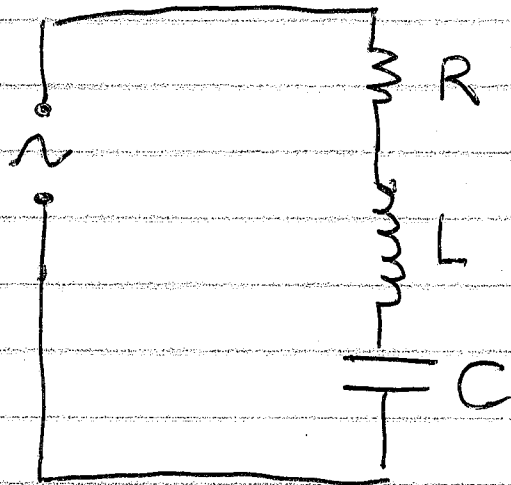

DC = Add resistances.

AC = Add impedances as vectors.

Resistor :  $\hat{x}$  direction

Inductor :  $+\hat{y}$  direction

Capacitor :  $-\hat{y}$  direction

Resistor  $\frac{x}{R}$   $y$

Inductor  $X_L = 2\pi fL$

Capacitor  $-X_C = \frac{-1}{2\pi fC}$

Total  $R$   $X_L - X_C$

Magnitude :  $Z = \sqrt{R^2 + (X_L - X_C)^2}$

⑦

Ex:  $1\text{ k}\Omega$ ,  $1.0\text{ H}$ ,  $1\text{ }\mu\text{F}$  in series

$$V = 140 \sin(500t) \quad I_{\text{rms}} = ?$$

Want to use  $V_{\text{rms}} = I_{\text{rms}} Z$

$$V_{\text{rms}} = \frac{V_{\text{max}}}{\sqrt{2}} = \frac{140}{\sqrt{2}} = 99\text{ V}$$

$$2\pi f = 500 \quad f = \frac{500}{2\pi} = ?$$

$$\downarrow$$
$$X_L = 2\pi f L = (500)(1.0) = 500\ \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{500 \times 10^{-6}} = 2000\ \Omega$$

$$(X_L - X_C) = -1500\ \Omega$$

$$Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(1000)^2 + (1500)^2}$$

$$= 1803\ \Omega$$

$$V_{\text{rms}} = I_{\text{rms}} Z$$

$$\frac{99\text{ V}}{1803\ \Omega} = 0.0549\text{ A} = I_{\text{rms}}$$

Power: Only resistor!

$$P = I^2 R = (0.0549\text{ A})^2 (1000\ \Omega) = 3.02\text{ W}$$

⑧

Since the inductor is  $+j$  and the capacitor is  $-j$ , they can ~~cancel~~ cancel.

If  $X_L = X_C$ , resonance.

$$2\pi f L = \frac{1}{2\pi f C}$$

$$(2\pi f)^2 = \frac{1}{LC}$$

$$2\pi f = \frac{1}{\sqrt{LC}}$$

$$f_R = \frac{1}{2\pi \sqrt{LC}}$$

At this frequency,  $Z$  is minimized.

$$\text{Ex: } f = \frac{1}{2\pi \sqrt{(1.0\text{H})(10^{-6}\text{F})}} = 159 \text{ Hz}$$

We were at  $f = \frac{500}{2\pi} = 80 \text{ Hz}$   
= below resonance.

At  $f_R \rightarrow Z = R$