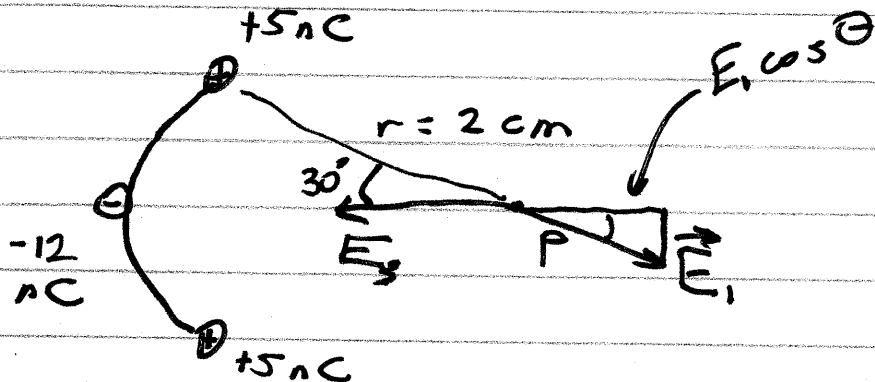


① Phys 2426 2014-09-15

HW1 #7



$\vec{E} @ P = ?$

Each contributes $E = \frac{kq}{r^2}$, but w/ different q and in diff dir.


	Magnitude (N/C)	x	y
Upper $+5 \text{ nC}$	1.125×10^5	$+9.743 \times 10^4$	$-m$
Lower $+5 \text{ nC}$	"	"	$+m$
-12 nC	E_3	$-E_3$	
		<u>Total E_x</u>	

(2)

Electric Current


Rate of flow of charge is current, I , measured in amps (A)

$$I = \frac{\Delta Q}{\Delta t}$$

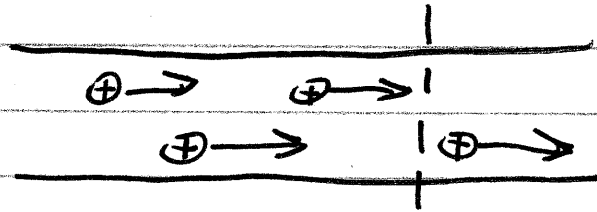

ΔQ is charge crossing the line per sec.


What makes current flow? Voltage.

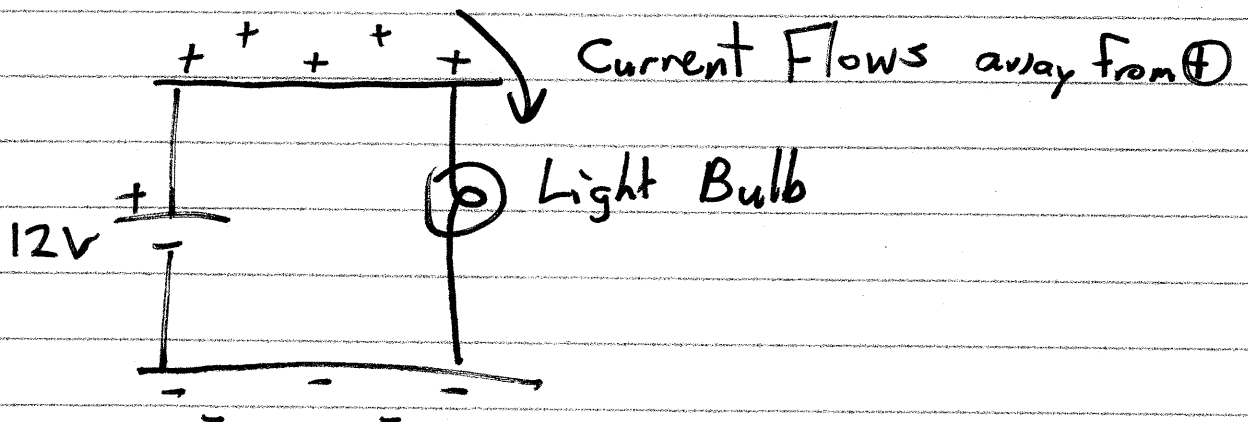

With the circuit, ΔQ can be large. Many coulombs.

③

Electron motion vs. Current

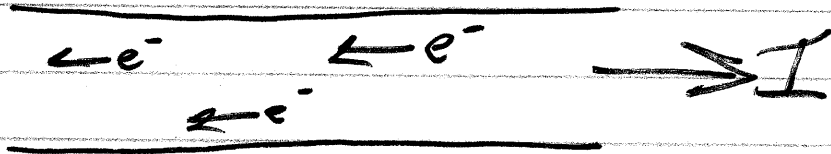


This region becomes \ominus

This region becomes more \oplus

What limits the current? Resistance

Ohm's Law $V = IR$

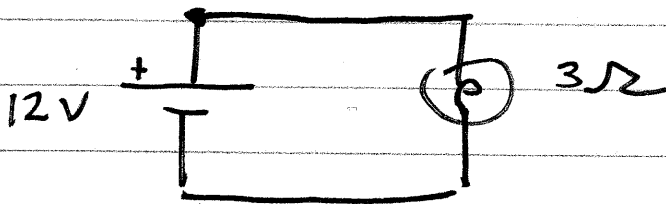

$$I = \frac{V}{R} = \frac{12V}{3\Omega} = 4A$$

* resistance, R , is in ohms (Ω)

Two connections are always needed!

Ideally, wires have $R = 0$

Voltage is $\frac{\text{Energy}}{\text{Charge}}$

$$V \cdot I = \frac{\text{Energy}}{\text{Charge}} \cdot \frac{\text{Charge}}{\text{Time}} = \frac{\text{Energy}}{\text{Time}} = P$$

power, P , is in watts (W). $1W = 1 \frac{J}{s}$

④

Cost of electricity ~ 0.12 \$/kWh

$$1 \text{ kWh} = (1 \text{ kW}) \cdot (1 \text{ hr}) = (1000 \text{ J/s}) (3600 \text{ s}) \\ = 3600000 \text{ J} = 3.6 \text{ MJ}$$

0.3 MJ for a penny

15 W light bulb on all month.

$$15 \text{ W} \cdot 1 \text{ month} = (0.015 \text{ kW}) (30 \text{ days}) \left(\frac{24 \text{ hr}}{\text{day}}\right)$$

Substitution ↗

Mult by 1 ↗

$$= 10.8 \text{ kWh}$$

$$\text{Total Cost} = (\text{Cost/ea}) (\text{Items})$$

$$= (\$0.12/\text{kWh}) (10.8 \text{ kWh})$$

$$= \$1.30$$

Battery Charge in Ah or mAh

$$I \Delta t = \Delta Q$$

$$3200 \text{ mAh} = (3200 \text{ mA}) (3600 \text{ s})$$

$$= 11520 \text{ A} \cdot \text{s} = 11520 \text{ C}$$


How many e^- ?

$$1e^- = 1.6 \times 10^{-19} \text{ C}$$

$$\frac{11520 \text{ C}}{1.6 \times 10^{-19} \text{ C}} = 7.2 \times 10^{22}$$

(3)

Series vs. Parallel

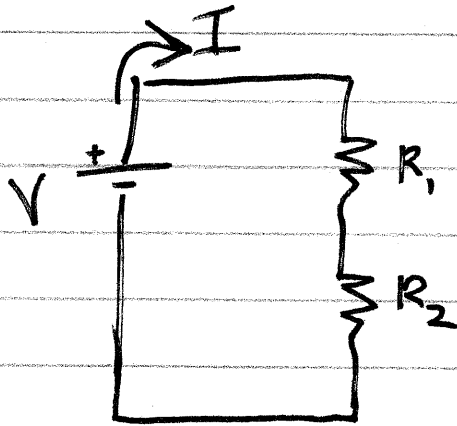


Series

Same Current
 $I = I_1 = I_2$

Batt gives total V_{tot} .

Each device takes some V .

$$V_{Tot} = V_1 + V_2$$

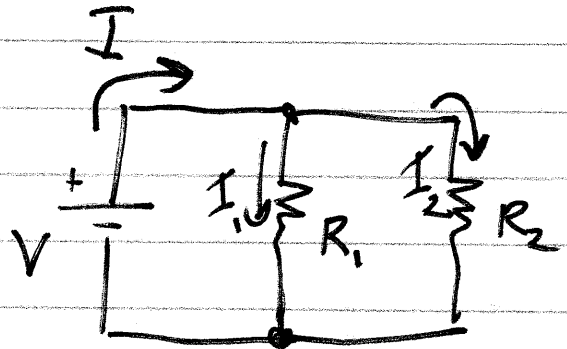

Parallel

$$I_{tot} = I_1 + I_2$$

Branch goes from node to node

Batt gives V_{tot}

One device or the other takes some V .

No V is left.

$$V_{Tot} = V_1$$
$$V_{Tot} = V_2$$