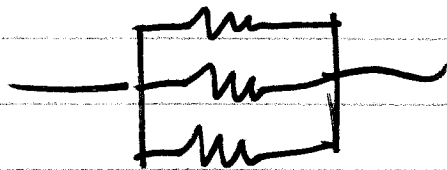


Phys 2426 2014-09-22

$$R = \rho \frac{l}{A}$$



$$= 3R$$




$$= \frac{R}{3}$$

9x smaller

$$V = IR$$

$$P = IV = I^2 R = \frac{V^2}{R}$$

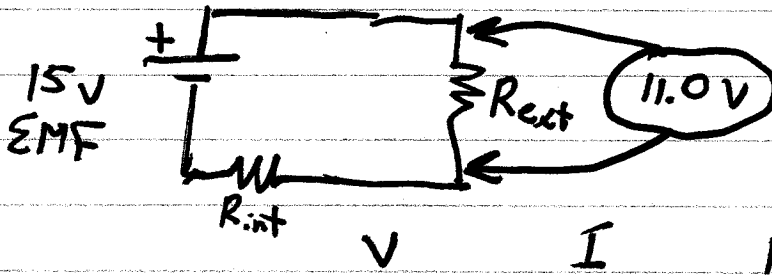Often loss. f
R is internal
or transmission



R_{int}

R_{ext}

11.0V




16.0W

Tot

15V

$$I = \sqrt{\frac{P_{device}}{R_{device}}}$$

②

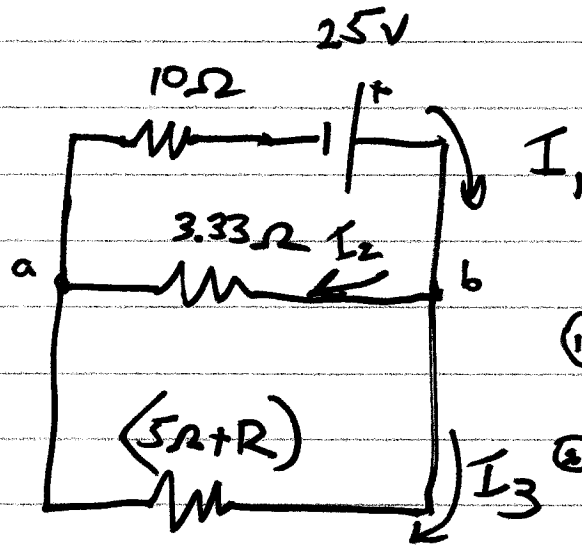

① $I_1 = I_2 + I_3$

② $+25 - 3.33 I_2 - 10 I_1 = 0$

Kirchoff's Laws


③ $+25 - (5+R) I_3 - 10 I_1 = 0$

$\Sigma I_{in} = \Sigma I_{out}$


$\Sigma_{loop} \Delta V = 0$

- KVL :
- Choose a looped path.
 - (Hint : try to follow the I arrows)
 - Itemize the devices along the loop.
 - Fill in ΔV for each.

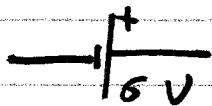
Devices (with my path going $\dots \rightarrow$)



$\Delta V = +6V$

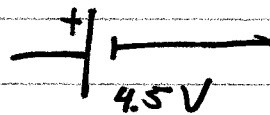

$\Delta V = -4.5V$

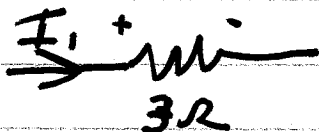


$\Delta V = -3 I_1$



$\Delta V = +7 I_2$

(3)

Ex 28.7, p. 845.

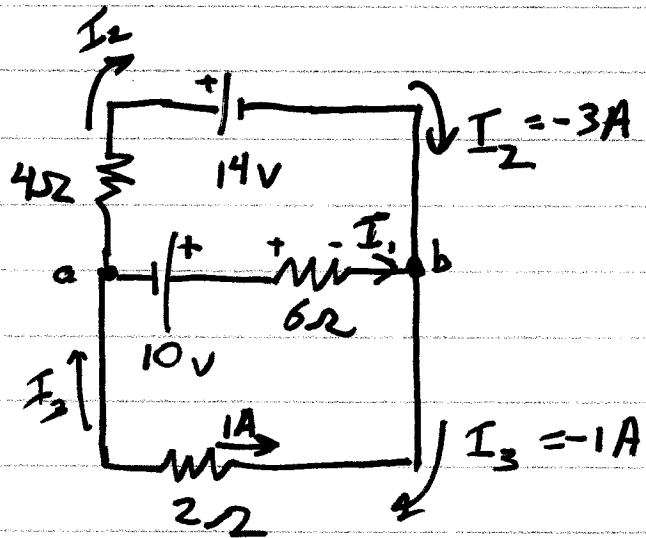

(Eq 1) $I_1 + I_2 = I_3$

Lower Loop:

$$\sum \Delta V = 0$$

(Eq 2) $0 = +10 - 6I_1 - 2I_3$

1. Solve for a variable in one eqn.

(Eq 3) $0 = -14 - 2I_3 - 4I_2$

2. Plug it into the others.

(Eq 2) $\rightarrow 0 = +10 - 6I_1 - 2(I_1 + I_2) = 10 - 8I_1 - 2I_2$ (4)

(Eq 3) $\rightarrow 0 = -14 - 2(I_1 + I_2) - 4I_2 = -14 - 2I_1 - 6I_2$ (5)

(4) $\rightarrow 2I_2 = 10 - 8I_1 \rightarrow I_2 = 5 - 4I_1$

(5) $\rightarrow 0 = -14 - 2I_1 - 6(5 - 4I_1)$

$$0 = -44 + 22I_1$$

$$I_1 = (2A)$$

$$I_2 = (-3A)$$

$$I_3 = (2A) + (-3A) = (-1A)$$