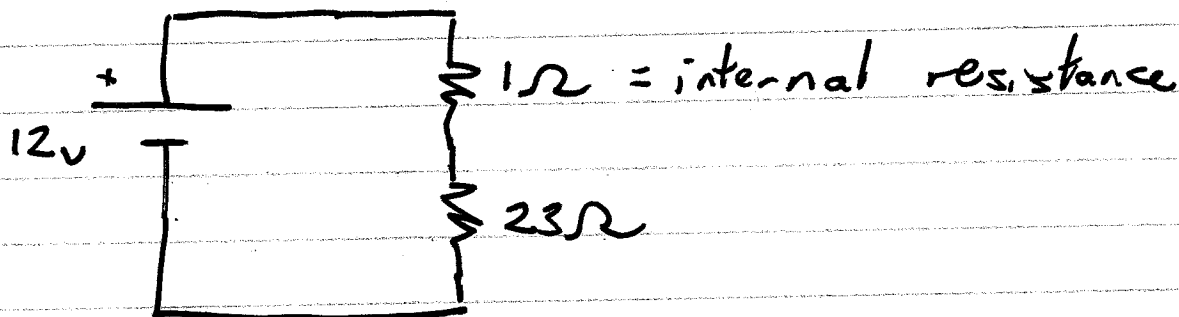


① Phys 2426 2014-09-24 Lec 8
Related to HW2 8(b):



$(12\text{ V}) I = \text{Power produced}$

For 1Ω resistor $V = 0.5\text{ V}$

$(0.5\text{ V}) I = \text{Power wasted internally}$

For 23Ω resistor $V = 11.5\text{ V}$

$(11.5\text{ V}) I = \text{Power delivered to load}$


$$\text{Efficiency} = \frac{P_{\text{delivered}}}{P_{\text{produced}}} = \frac{11.5}{12} = \frac{23}{24}$$

$$\text{Waste} = \frac{0.5}{12} = \frac{1}{24}$$

②


Charging & Discharging capacitors

With a battery:

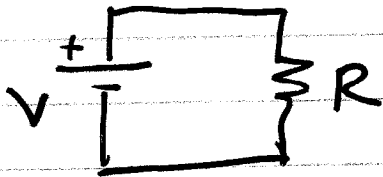


$$I = \frac{V}{R} = \text{const}$$
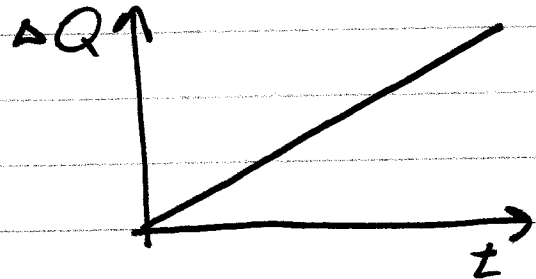
$$I = \frac{\Delta Q}{\Delta t} \rightarrow \Delta Q = \int I dt$$



With a capacitor

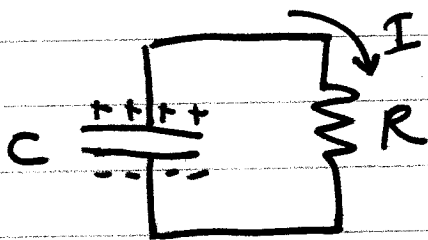

$$V_C = Q/C \quad V_R = IR$$

$$I = \frac{V_R}{R} = -\frac{Q}{RC}$$

As Q decreases, I decreases.

$$I = \frac{1}{RC} Q = -\frac{dQ}{dt}$$

$$\frac{dQ}{dt} = -\frac{1}{RC} Q$$


Solution: $Q = Q_0 e^{-t/RC}$

$$\frac{dQ}{dt} = \underbrace{Q_0 e^{-t/RC}}_Q \left(-\frac{1}{RC} \right)$$

③

Discharging a Capacitor

	<u>Initially</u>	<u>...and then</u>
Q	Q_0	decreases
V	$V_0 = Q_0/C$	decreases
I	$I_0 = V_0/R$	decreases

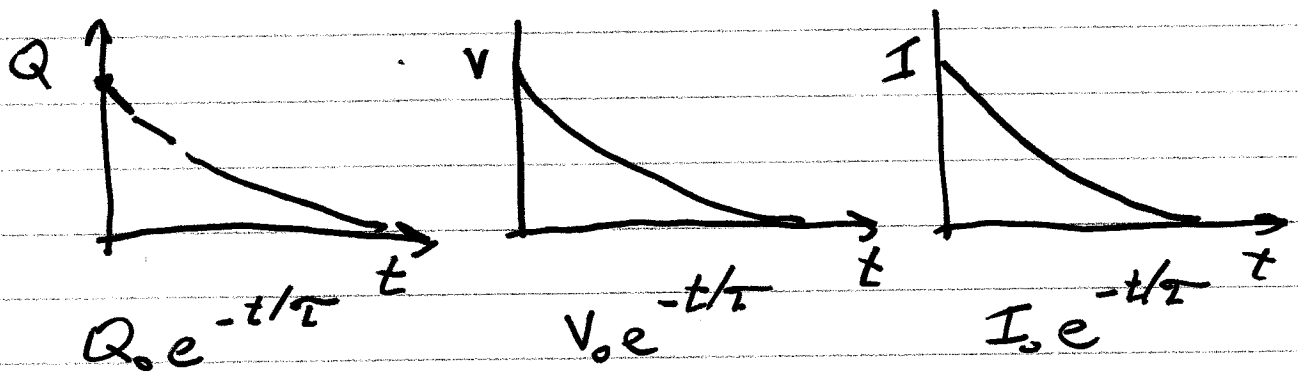

$\tau = \text{"time constant"} = RC$

Bigger R = slower drain
 Bigger C = bigger bucket

Ex: $V_0 = 100 \text{ V}$ $\tau = 5 \text{ s}$

<u>t</u>	<u>V</u>
t=0	$V = V_0 = 100 \text{ V}$
1	$V = (100 \text{ V}) e^{-1/5} = (100 \text{ V})(0.82) = 82 \text{ V}$
2	$V = \quad \quad \quad = 67 \text{ V}$
:	

$\tau = t = 5 \text{ s} \quad \quad \quad = 37 \text{ V}$

After one time constant, V is 37% of V_0 .

④

$$V = V_0 e^{-t/\tau}$$

V = voltage at a given time

t = current time on stopwatch

V_0 = initial voltage

τ = time constant

$$\frac{V}{V_0} = \text{fraction of remaining charge.}$$

$$\frac{t}{\tau} = \text{current time in "time constants"}$$

Half-life is time to reach 50%.

$$\frac{V}{V_0} = 0.5 = e^{-t/\tau}$$

$$\ln(0.5) = -t/\tau$$

$$t = -\tau \ln(0.5) = 0.693\tau$$

Useful Eqns:

$$V_C = Q/C$$

$$V_R = IR$$

$$\tau = RC$$

Ex: At $t=0$, $V=6V$

$t=2.5s$, $V=4V$

$R=1k\Omega$

$C = \tau/R$

$V_0=6$

$$e^{-2.5/\tau} = \frac{4}{6}$$


$$-2.5/\tau = \ln(4/6)$$

$$\tau = -2.5/\ln(4/6)$$

$$= 6.17s$$

5


Charging a capacitor

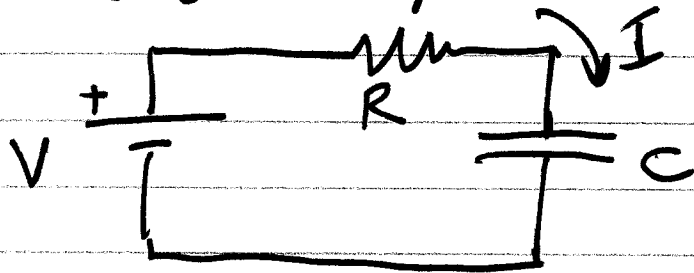

$$V_{\text{batt}} = V_R + V_C$$

	<u>Initially</u>	<u>...and then</u>	<u>Eventually</u>
Cap	$Q = 0$ $V_C = 0$	Q increases V_C increases	$Q_0 = CV_0$ $V_C = V_0$
Batt	V_0	V_0	V_0
R	$V_R = V_0$ $I = V_0/R$	V_R decreases I decreases	$V_R = 0$ $I = 0$

Initially, cap acts like a wire.

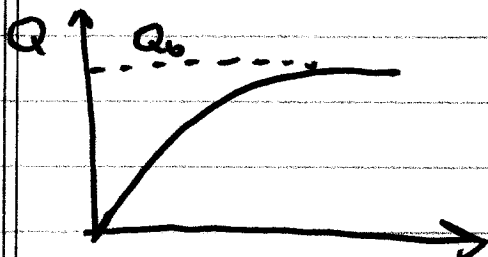

$$I = I_0 e^{-t/\tau}$$

$$Q_0 - Q = Q_0 e^{-t/\tau}$$

$$Q = Q_0 (1 - e^{-t/\tau}) \quad V = V_0 (1 - e^{-t/\tau})$$

$(1 - e^{-t/\tau})$ is fraction of final charge

$e^{-t/\tau}$ is fraction of process remaining