

① Phys 2426 2014-16-20

## AC Waveform

$$V(t) = V_0 \sin(2\pi f t + \phi_0)$$

Amplitude                      Frequency                      Phase

$$= V_0 \sin(2\pi f (t - t_0))$$

Resistor: @ every instant  $V = IR$


$$I(t) = \frac{V_0}{R} \sin(2\pi f t + \phi_0)$$

Current Amplitude  
No change in  $f$  or  $\phi_0$ .

$$V_0 = I_0 R$$

Inductor:


$$V = +L \frac{dI}{dt}$$

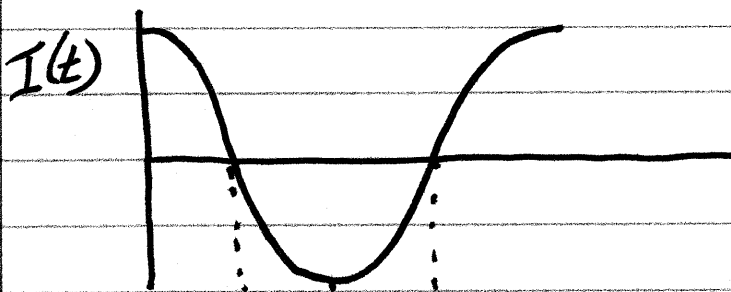

$$I(t) = I_0 \cos(2\pi f t + \phi_0)$$

$$V = +L I_0 \sin(\omega)(2\pi f)$$
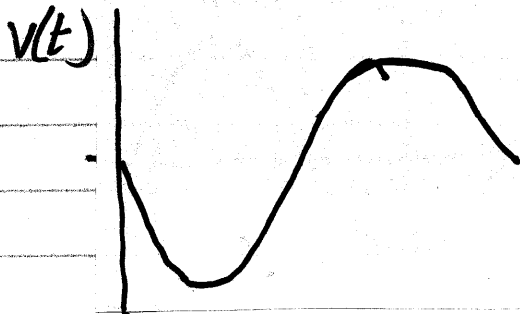
$$= \underbrace{I_0 2\pi f L}_{V_0} \sin(\omega)$$



$$V_0 = I_0 X_L$$

②

$X_L =$  inductive reactance in ohms ( $\Omega$ )

Also called  $Z_L =$  inductive impedance

$$Z_L = 2\pi f L$$

$$V_o = I_o Z_L$$

Ohm's Law for AC  $\uparrow$

Note:  $f$  didn't change.

$$\sin(\theta) = \cos(\theta - \pi/2)$$

The current and voltage in the inductor are not in phase.

Also,  $Z_L$  depends on  $f$ !

Low- $f$ :  $Z_L = 2\pi f L = \text{small}$ .


Current can be high w/o voltage.

High- $f$ :  $Z_L = 2\pi f L = \text{huge}$

High- $f$  current is blocked.

Remember: Inductor hates change (in current)

### 3 Capacitor in AC

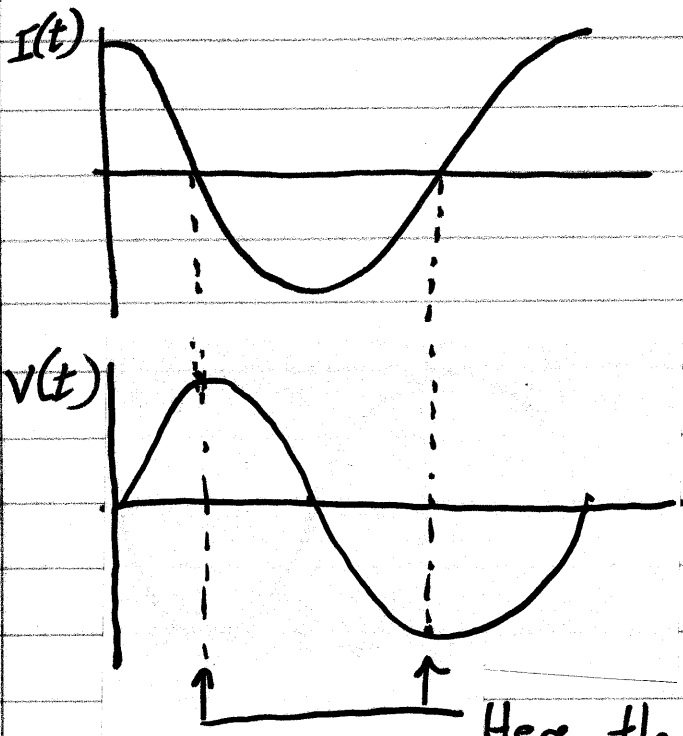

$$V_c = Q/C$$

The change in  $V$  is a change in  $Q$ .  
 As  $Q$  decreases,  $I$  goes out.  
 $I(t)$  is current flowing ~~in~~ <sup>in</sup> is  $\oplus \ominus$

Here, the cap is "charged"

$$V = Q/C$$

$$\frac{dV}{dt} = \frac{-I}{C}$$

$$V = V_0 \sin(2\pi f t + \phi_0)$$

$$I = -C \frac{dV}{dt} = -C V_0 \cos(2\pi f t + \phi_0) (2\pi f)$$

$$= - \underbrace{2\pi f C V_0}_{I_0 = \text{current amplitude}}$$

$$Z_c = \frac{1}{2\pi f C}$$

$$V_0 = I_0 Z_c$$

Low- $f \rightarrow$  high  $Z_c$

$f=0 \rightarrow Z_c = \infty$

High- $f \rightarrow$  Low  $Z_c$

④

## Combining Components - Series AC

DC: Resistances add

AC: Impedances add like vectors

$$Z_R = R \quad \text{in } x\text{-direction}$$

$$Z_L = 2\pi fL \quad \text{in } y\text{-direction}$$

$$Z_C = \frac{1}{2\pi fC} \quad \text{in } (-y)\text{-direction}$$

$|\vec{Z}_{\text{Tot}}|$  is net impedance in series

$$Z_R = \text{total } R$$

$$Z_L = \text{total } Z_L\text{'s}$$

$$Z_C = \text{total } Z_C\text{'s}$$

$$X = Z_L - Z_C$$

$$Z = \sqrt{R^2 + X^2}$$

More resistors in series always increases  $Z$ .

More L's or C's could increase or decrease  $Z$ .

$Z$  depends on  $f$ !

5

Ex: 120 V  
30  $\Omega$  resistor

$$I = \frac{V}{R} = \frac{120V}{30\Omega} = 4A$$

If  $f = 60$  Hz, what  $C$  would have same  $Z$ ?

$$Z_c = \frac{1}{2\pi f C} \rightarrow C = \frac{1}{2\pi f Z_c} = 8.8 \times 10^{-5} F = 88 \mu F$$

What  $L$  would have the same  $Z$ ?

$$Z_L = 2\pi f L \quad L = \frac{Z_L}{2\pi f} = 0.080 H = 80 mH$$

(For ref: "Outer coil" had  $L = 78 \mu H$ )


What if  $R = 30 \Omega$  and  $C = 88 \mu F$  are in series?

$$\left. \begin{array}{l} Z_R = 30\Omega \\ X = Z_L - Z_c = -30\Omega \end{array} \right\} Z = \sqrt{30^2 + 30^2} = 42.4\Omega$$

What about  $R + L$ ?

What about  $L + C$ ?
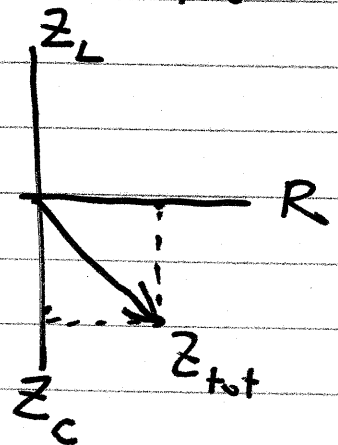
$$\left. \begin{array}{l} X = 0 \\ R = 0 \end{array} \right\} Z = 0$$



⑥

IF  $Z_L = Z_C$  it is called resonance.

The inductor & capacitor cancel each other.

$$Z_L = 2\pi f L \quad Z_C = \frac{1}{2\pi f C}$$

$$2\pi f L = \frac{1}{2\pi f C}$$

$$(2\pi f)^2 = \frac{1}{LC}$$

$$2\pi f = \frac{1}{\sqrt{LC}}$$

$$f = \frac{1}{2\pi\sqrt{LC}}$$

① resonant  $f$ ,  $X=0$  for series LC

② high  $f$   $Z_L$  is larger and dominates.

③ low- $f$   $Z_C$  is larger and dominates.

④  $f_R$   $R$  is largest

