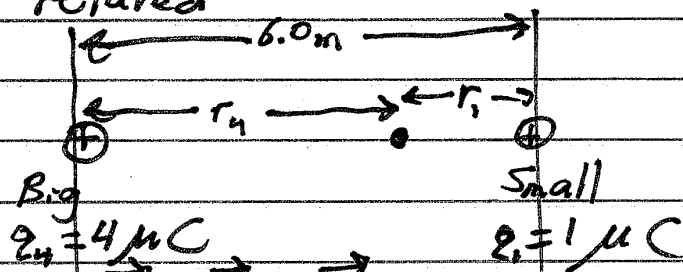


① Phys 2426 2015-09-10 Lec 5

SMTE-0095 Due Fri! Register Today!

HW1 #16 - related





Everywhere;  $\vec{E} = \vec{E}_4 + \vec{E}_1$

For  $\vec{E} = 0$ :  $\vec{E}_4 = -\vec{E}_1$

Opposite:  $\vec{E}_4 = -\vec{E}_1$

Equal:  $|\vec{E}_4| = |\vec{E}_1|$

$\vec{E}_4$   
 $\vec{E}_1$   
Opposite?

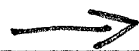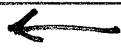

$$\frac{k|q_4|}{r_4^2} = \frac{k|q_1|}{r_1^2}$$



$$r_1 + r_4 = (6.0 \text{ m})$$

$$q_4 r_1^2 = q_1 r_4^2$$

$$4 r_1^2 = r_4^2$$

$$2 r_1 = r_4$$

②

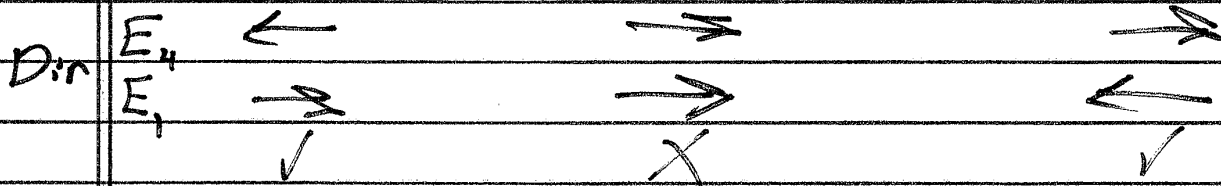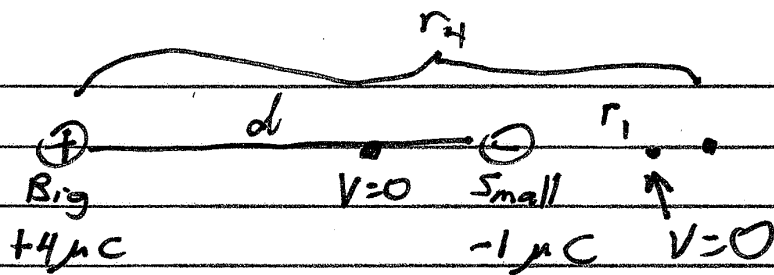

close to small?

X

✓

$$\frac{k|q_4|}{r_4^2} = \frac{k|q_1|}{r_1^2} \quad d + r_1 = r_4$$

Potential?  $V = \frac{kq}{r}$

"Close to the small charge" is our only restriction.

"Small x"  $r_4 + r_1 = d$   $\frac{q_4}{r_4} = \frac{q_1}{r_1}$


"Large x"  $d + r_1 = r_4$   $\frac{q_4}{r_4} = \frac{q_1}{r_1}$

③

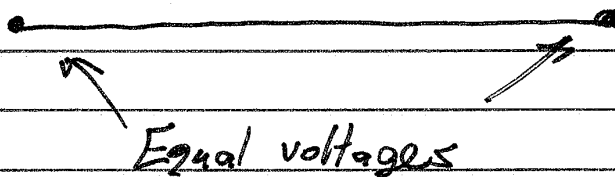
## Voltage in Circuits

- Voltage is not "stuff"
- Voltage does not move or flow.
- Absolute voltages don't matter, only relative voltages. ( $\Delta V$ )


Wires -  $\vec{E} = 0$  in a conductor  
 $\Delta V = -\int \vec{E} \cdot d\vec{l} = 0$



Height Analogy

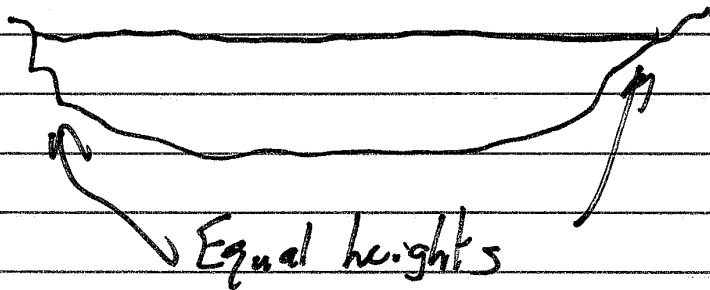


Pressure  
(Airchose)

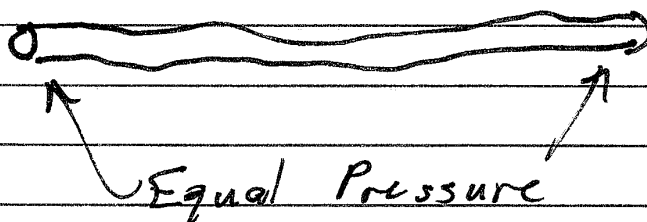

④

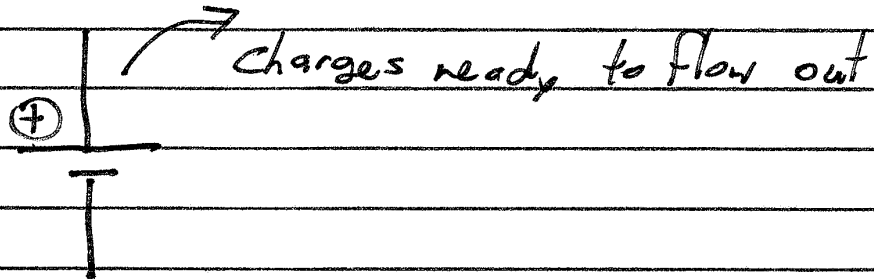Batteries - Generate a specific  $\Delta V$



Schematic Symbol  
for battery

Capacitor - Storage tanks for charge



Capacitor

$$Q = CV$$

$V = \Delta V$  From one side to the other


$Q =$  charge of one plate  
(other plate has  $-Q$ )

$C =$  capacitance in farads (F)

$$C = K\epsilon_0 A/d$$



⑤

## Charging a Capacitor

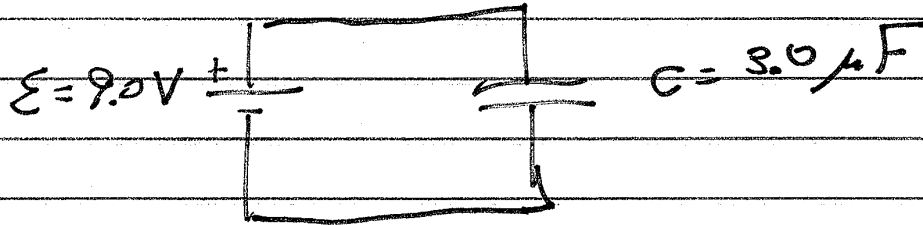

$$\begin{aligned} Q &= CV \\ &= (3.0 \mu\text{F})(9.0 \text{ V}) \\ &= 27.0 \mu\text{C} \end{aligned}$$

Using a cap to charge a cap

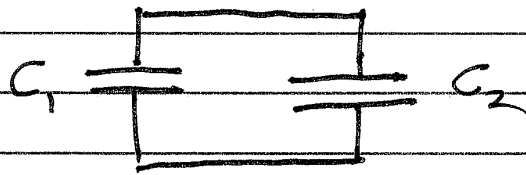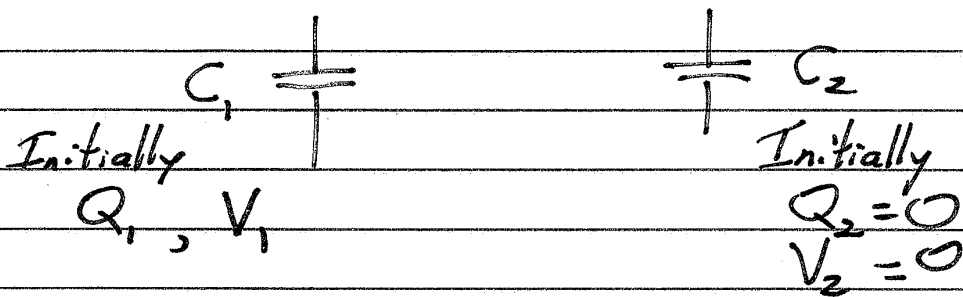

Final:  $V_1 = V_2$        $Q_1 + Q_2 = \text{const}$

$$\begin{aligned} C_1 V_1 &= Q_1 \\ C_2 V_2 &= Q_2 \end{aligned}$$