

2426 ① Phys 2426 2015-09-17 Lec 7

HW 2 - Work on it!
- Use "Ask Your Teacher"

Want to transfer energy quickly.
Usual phone charger = 5.0 V.

$$\text{Rate of Energy Flow} = P = I V$$

For small wires, $I = 2.0 \text{ A}$ max.
 $P = (5 \text{ V})(2 \text{ A}) = 10 \text{ W}$

Qualcomm Quick Charge
 $V = 5 \text{ V}, 9 \text{ V}, 12 \text{ V}$

Then $P = (12 \text{ V})(2 \text{ A}) = 24 \text{ W}$


2426 (2)

Circuit Analysis Principles

- * Cons. Charge
- * Cons. Energy per charge


Cons. Charge

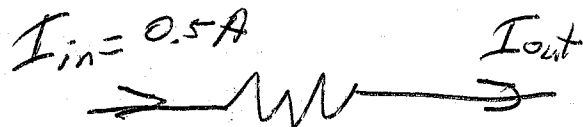Must account for all current,
what goes in must come out.
Current flows through components.



We know $I_{out} = 0.5A$

At a junction, current "splits".

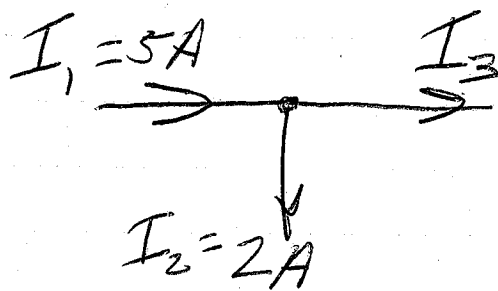

We know $I_3 = 3A$

$$I_1 = I_2 + I_3$$

In general: $\sum I_{in} = \sum I_{out}$

2426


③

Cons. Energy per charge

- When a charge completes any loop, its total energy gain must equal its total energy loss.

$$\text{For any loop: } \sum V_{\text{gain}} - \sum V_{\text{loss}} = 0$$

$$\sum \Delta V = 0$$

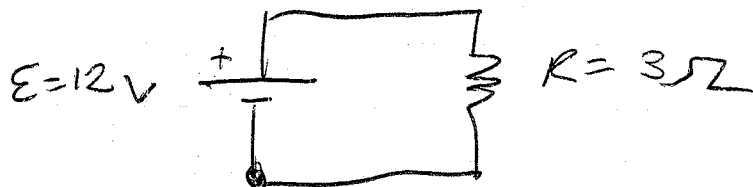

My Loop: start @ lower left, go CW.

$$\text{Battery} \quad V_{\text{gain}} = 12 \text{ V} \quad \Delta V = +12 \text{ V}$$

$$\text{Resistor} \quad V_{\text{loss}} = IR \quad \Delta V = -IR$$

$$12 \text{ V} - IR = 0$$


$$12 \text{ V} = I (3 \Omega)$$

$$I = 4 \text{ A}$$

$$\text{Loop eqn says } V_{\text{batt}} = V_R$$

2426 (7)

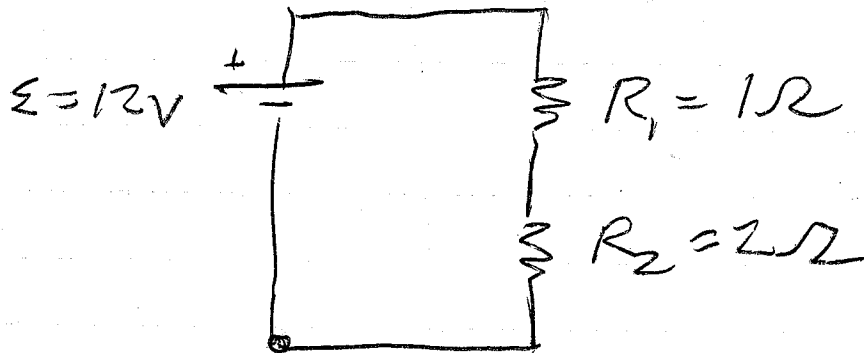Series Circuit - current passes thru one component after another.



Charge: There is only one current.
 $I_{\text{batt}} = I_1 = I_2 = I$

Voltage: Loop from Lower-Left, CW

Batt:	$V_{\text{gain}} = 12 \text{ V}$
R_1 :	$V_{\text{loss}} = I (1\Omega)$
R_2 :	$V_{\text{loss}} = I (2\Omega)$

$$(12 \text{ V}) - I(1\Omega) - I(2\Omega) = 0$$

$$(12 \text{ V}) - I(1\Omega + 2\Omega) = 0$$

$$(12 \text{ V}) = I(1\Omega + 2\Omega)$$


$$V = I R$$

Series: $R_{\text{eq}} = R_1 + R_2 + \dots$

2426

5

Parallel Circuit - current has options

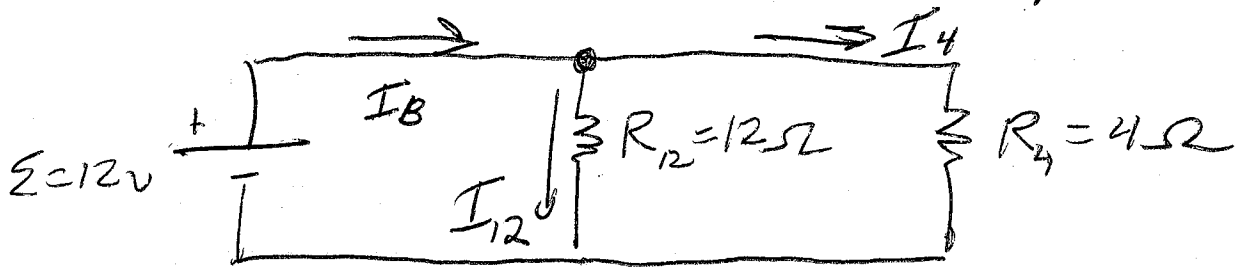

Current: At top junction

I_{batt} is inward

I_4 is outward

I_{12} is outward

$$I_B = I_4 + I_{12}$$

Voltage: Can follow different loops

Batt - R_{12}

Batt - R_4

$$12\text{V} - I_{12} R_{12} = 0$$

$$12\text{V} - I_4 R_4 = 0$$

$$I_{12} = \frac{12\text{V}}{12\Omega} = 1\text{A}$$

$$I_4 = \frac{12\text{V}}{4\Omega} = 3\text{A}$$

$$I_B = 3\text{A} + 1\text{A} = 4\text{A}$$

Batt "sees": $\mathcal{E} = 12\text{V}$ $I = 4\text{A}$ $R_{\text{eq}} = 3\Omega$

R_4 "sees": $R_4 = 4\Omega$ $I = 3\text{A}$ $V_4 = 12\text{V}$

R_{12} "sees": $V_{12} = 12\text{V}$


2426 (6)

	<u>Series</u>	<u>Parallel</u>
Current	$I = I_1 = I_2 = I_3 \dots$	$I_T = I_1 + I_2 + \dots$
Voltage	$V_T = V_1 + V_2 + \dots$	$V = V_1 = V_2 = \dots$
Resistance	$R_{eq} = R_1 + R_2 + \dots$	$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots$
Power	$P_T = P_1 + P_2 + \dots$	$P_T = P_1 + P_2 + \dots$

For any circuit: $\Sigma P_{gen} = \Sigma P_{used}$

2426 ⑦

Combination Circuit

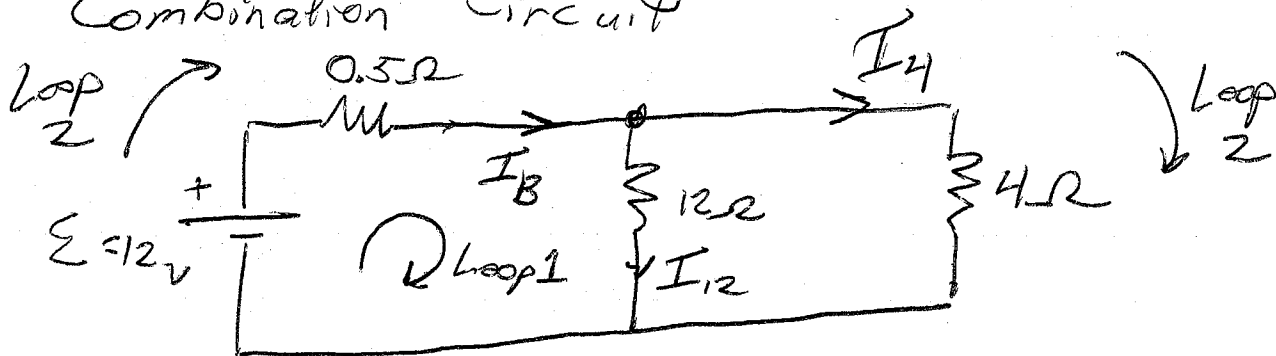

Method 1:

$$I_B = I_4 + I_{12}$$

$$(12\text{V}) - 0.5 I_B - 12 I_{12} = 0$$

$$(12\text{V}) - 0.5 I_B - 4 I_4 = 0$$

Method 2:

