

① Phys 2426 2015-09-24 Lec 9

Exam 1 Tue 9/29

Practice test (Last Year's Exam) posted.
tinyurl.com/spirkocal

Topics:

Electrostatics, charge, E-field

Elec Potential (V), relation to E

Batteries & Capacitors

DC current & Ohm's Law

Complex DC Circuits


- Equivalent R

- Kirchoff's Laws

- Meters for V, I, R

RC Circuits

②

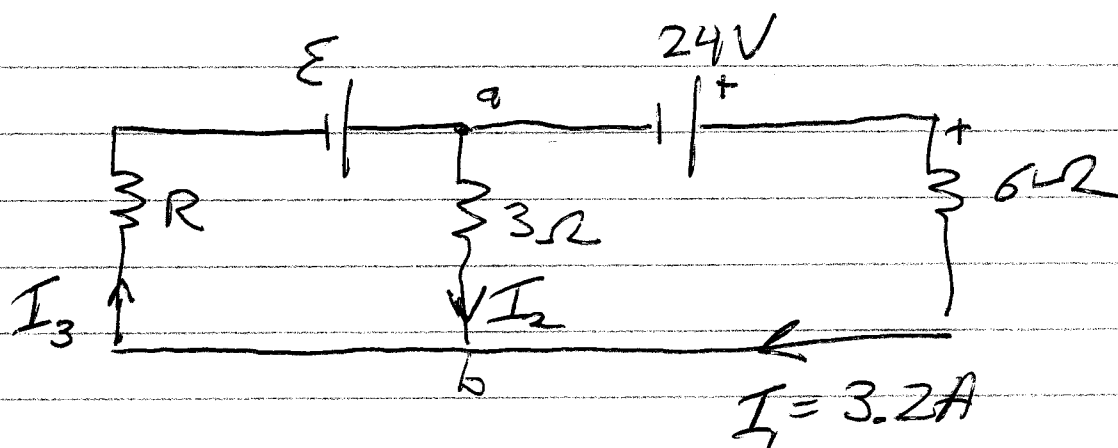

Current:
$$I_3 = I_2 + (3.2 A)$$

Loops: Out:
$$\mathcal{E} - I_3 R + 24 - I_1 \cdot 6 = 0$$

Left:
$$\mathcal{E} - I_3 R - I_2 \cdot 3 = 0$$

$$(\mathcal{E} - I_3 R) = \underbrace{-24 + I_1 \cdot 6}_{= I_2 \cdot 3}$$




w/o Kirchoff:
$$V_6 = 6 \cdot 3.2 = (19.2 V)$$

$$a \rightarrow b \quad \Delta V = +24 V - 19.2 V = 4.8 V$$


b is $4.8V$ higher than a

$$I_2 = (4.8V) / (3\Omega) = 1.6 A \quad b \rightarrow a$$

3

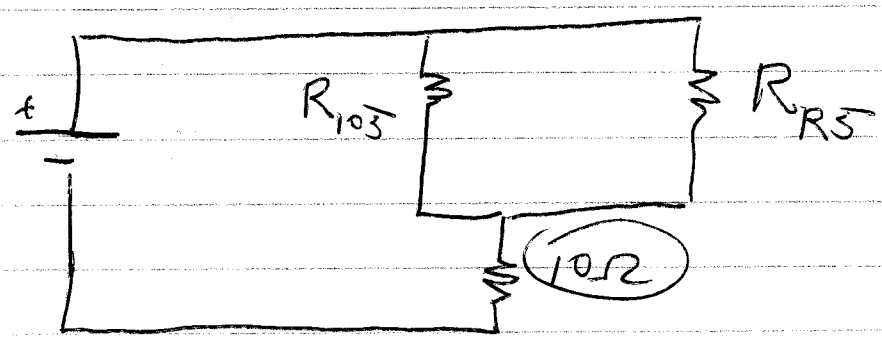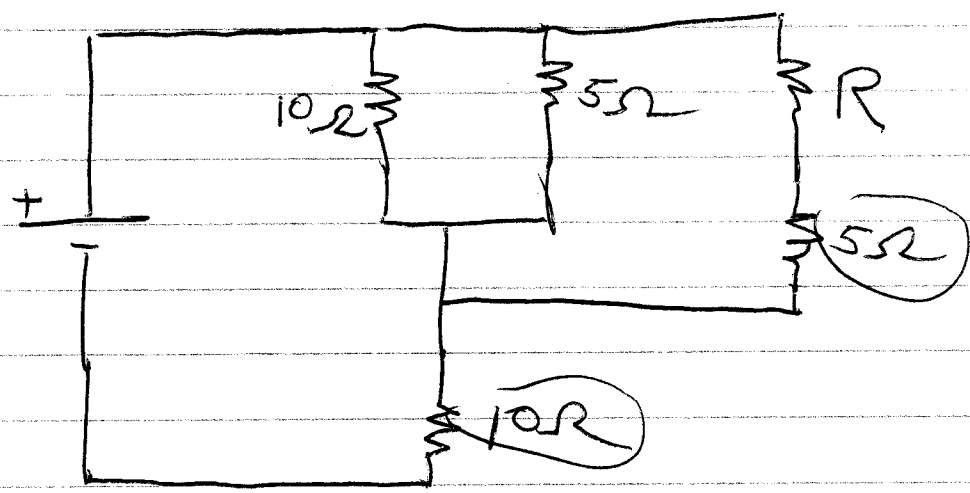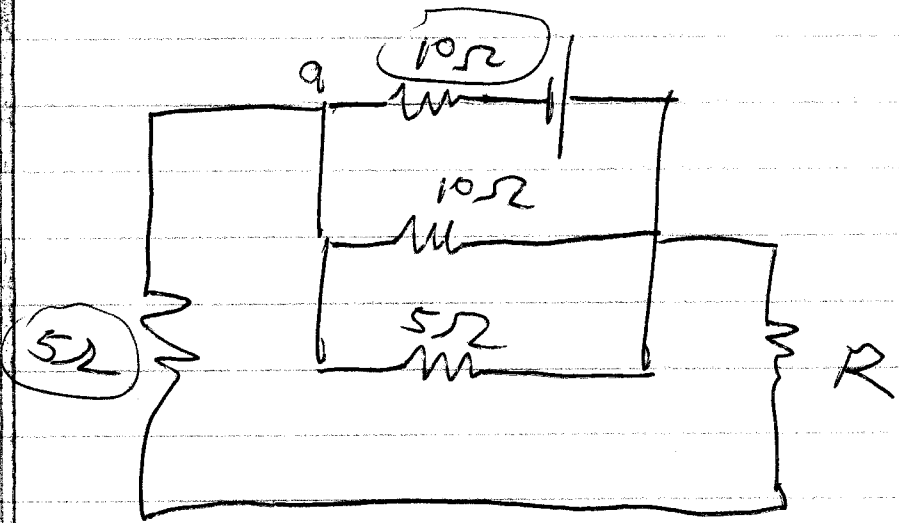

4

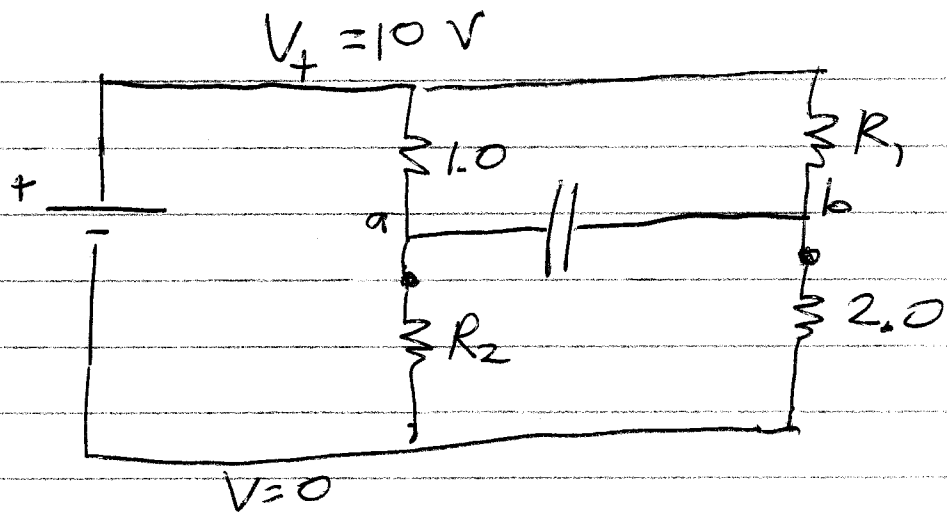

$$Q = CV \quad V = \text{const} \quad I = 0$$

$$I_2 = \frac{10}{1 + R_2}$$


$$V_2 = I R_2$$

$$V_a = V_2$$

$$I_1 = \frac{10}{R_1 + 2}$$

$$V_b = 2 I_1$$

$$V_c = V_a - V_b$$

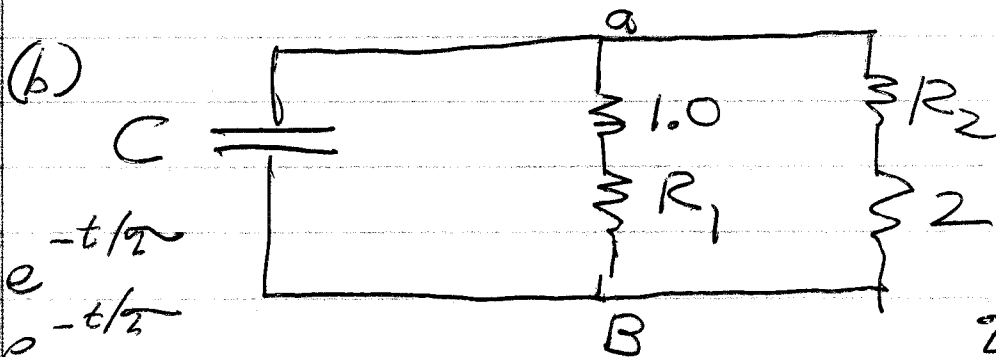


$$\tau = RC$$

$$V = V_0 e^{-t/\tau}$$

$$\frac{V}{V_0} = e^{-t/\tau}$$

$$\frac{1}{6} = e^{-t/\tau}$$
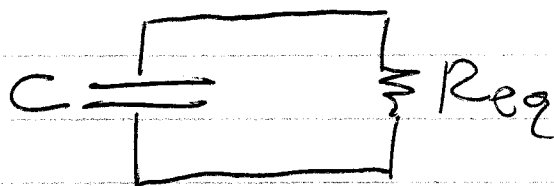
$$\ln\left(\frac{1}{6}\right) = \frac{-t}{\tau}$$



⑤

After 3 time constants, how much charge is left in a discharging cap?

$$Q = Q_0 e^{-t/\tau}$$

$$\left(\frac{Q}{Q_0}\right) = e^{-t/\tau}$$

Answer, as worded


$$= e^{-3\tau/\tau} = e^{-3}$$

$$= 0.0498$$

$$= 5\%$$

$$\tau = RC$$

Thunderstorm as a parallel plate cap:

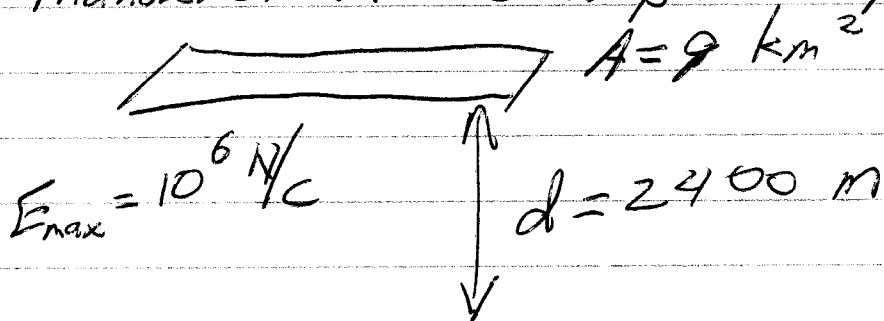


$$E = 4\pi k \sigma$$

$$\sigma = \frac{E}{(4\pi k)} = \frac{9 \times 10^9 \frac{\text{Nm}^2}{\text{C}^2}}{4\pi} = 8.84 \times 10^{-6} \frac{\text{C}}{\text{m}^2}$$

$$Q = \sigma A = \sigma (9 \times 10^6 \text{ m}^2) = 80 \text{ C}$$

This is +80 C on ground, -80 C in cloud.

6

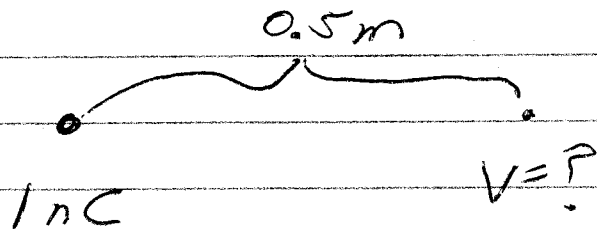

$$V = \frac{kq}{r} = \frac{(9 \times 10^9) (1 \times 10^{-9})}{0.5}$$

$$= 18 \text{ V}$$

1.0 nC spread out on a ring w/ radius 0.5 m. What is V @ center?

$$V = \int \frac{k dq}{r}$$

$$= \frac{k}{r} \int dq$$

$$= \frac{kq}{r} = (18 \text{ V})$$

