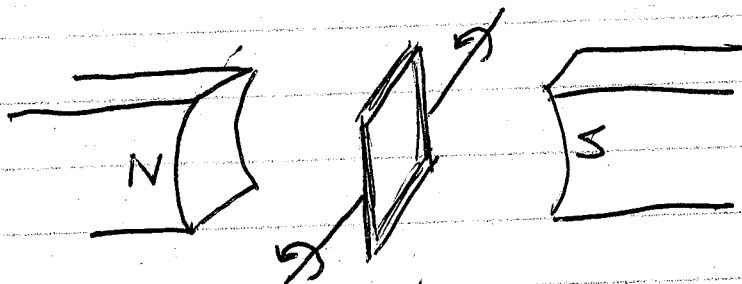


① Phys 2426 2016-12-18 Lec 16

AC Electricity

Alternator



Spinning coil generates voltage.

$$\mathcal{E} = - \frac{d\Phi_B}{dt}$$

$$\Phi = NBA \cos \theta$$

$$= - \frac{d}{dt} NBA \cos \theta = -NBA \left(-\sin \theta \left(\frac{d\theta}{dt} \right) \right)$$

$$= \underbrace{NBA \omega}_{\text{Amplitude}} \sin \theta$$

$$\theta = \omega t = 2\pi f t$$

$\sin \theta$ repeats when $\theta = 2\pi$

$$2\pi f t = 2\pi$$

$$f t = 1$$

This is a special time, $t = T = \text{Period}$

$$f = 1/T = \text{Frequency}$$

②

Frequency f in $\boxed{\text{Hz}}$ $1 \text{ Hz} = 1 \text{ cycle/s}$


Angular Freq ω in s^{-1} $1 \text{ s}^{-1} = 1 \boxed{\text{rad/s}}$

$$\omega = 2\pi f$$

$$\sin(\omega t) = \sin(2\pi f t)$$

US AC: $E_{\text{max}} = 170 \text{ V}$ $E_{\text{rms}} = 120 \text{ V}$
 $f = 60 \text{ Hz}$ $\omega = 377 \text{ s}^{-1}$

Graph of AC Signal

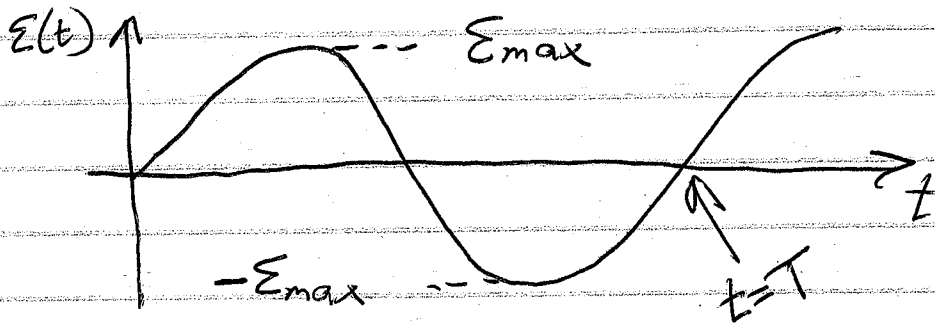

The voltage is usually between 0 and E_{max} .
The average-ish voltage is:

$$E_{\text{RMS}} = \frac{1}{\sqrt{2}} E_{\text{max}}$$

↳ Root Mean Square

$$\frac{170 \text{ V}}{\sqrt{2}} = 120 \text{ V}$$

③

Resistors in AC

Ohm's Law

$$V = IR$$

osc \nearrow \nearrow const
must oscillate

$$I = \frac{V}{R} = \frac{E_{\max} \sin(2\pi ft)}{R}$$

$$I_{\max} = \frac{E_{\max}}{R}$$

Power:


$$P = VI$$

$$= E_{\max} \sin(2\pi ft) \frac{E_{\max} \sin(2\pi ft)}{R}$$

$$= \frac{E_{\max}^2}{R} \sin^2(2\pi ft)$$

$$\frac{E_{\max}^2}{R} = P_{\max}$$
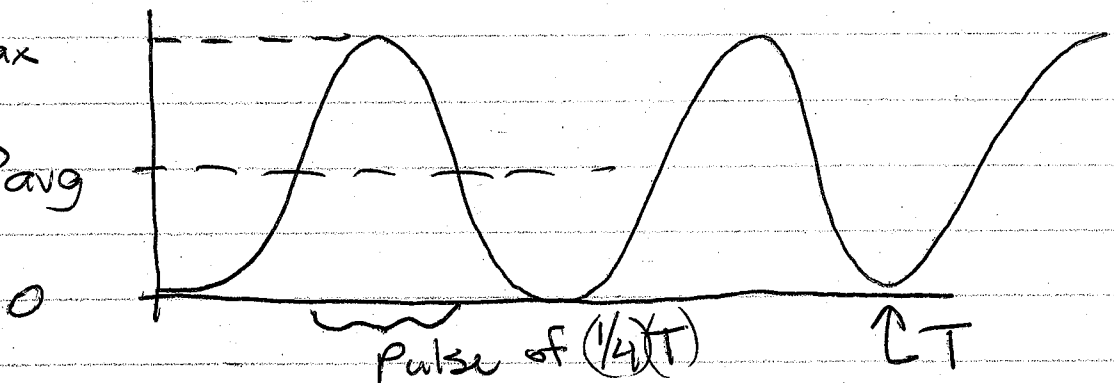
$$\frac{1}{2} P_{\max} = P_{\text{avg}}$$



4

Average Power

For Resistor: $P_{avg} = \frac{1}{2} P_{max}$

$$P_{avg} = \frac{\frac{1}{2} E_{max}^2}{R} = \frac{E_{rms}^2}{R}$$

In DC: $P = \frac{V^2}{R}$

$$\frac{\frac{1}{2} E_{max}^2}{R} = \frac{E_{RMS}^2}{R}$$

$$E_{rms} = \frac{1}{\sqrt{2}} E_{max}$$

For a resistor

$$P_{avg} = I_{rms} V_{rms}$$

$$V_{rms} = I_{rms} R$$

Energy & Power

$$P = \frac{dEnergy}{dt}$$

$$P_{avg} = \frac{\Delta Energy}{\Delta t}$$

$$Energy = P_{avg} \Delta t$$

⑤

Ex: 60 W Light Bulb

Current:
$$P_{avg} = V_{rms} I_{rms}$$
$$(60W) = (120V) I_{rms}$$
$$0.5A = I_{rms}$$

Resistance:
$$V_{rms} = I_{rms} R$$
$$(120V) = (0.5A) R$$
$$240 \Omega = R \quad \text{Hot} \quad \text{cold}$$

Measured w/ ohmmeter: $R = 60 \Omega$

Energy use in a month:

$$\text{Energy} = P_{avg} \Delta t = (60W) (720 \text{ hr}) \left(\frac{3600s}{h} \right)$$
$$= 1.55 \times 10^8 \text{ J}$$

$$= (60W) \left(\frac{1 \text{ kW}}{1000W} \right) (720 \text{ hr}) = 43.2 \text{ kWh}$$

$$\text{Cost} = \text{Rate} \cdot \text{Amount} = \left(\frac{\$0.12}{\text{kWh}} \right) (43.2 \text{ kWh})$$
$$= \$5.18$$

$$\text{LED Bulb Cost} = (\$5.18) (9/60)$$
$$= \$0.78$$

⑥

Inductors in AC

Assume $I = I_{\max} \sin(2\pi f t)$

$$V_L = L \frac{dI}{dt} = L I_{\max} \cos(2\pi f t) (2\pi f)$$

$$V_L = \underbrace{(2\pi f L)}_{V_{\max}} I_{\max} \cos(2\pi f t)$$

$$V_{\max} = I_{\max} (2\pi f L)$$

Differences from Ohm's Law

- Proportionality depends on frequency.

$$X_L = 2\pi f L = \text{Reactance}$$

$$Z_L = \text{Impedance}$$

- $\sin()$ changed to $\cos()$.

$$\cos(\theta) = \sin\left(\theta + \frac{\pi}{2}\right)$$