

AC Components

Resistors

$$V_R = I R$$

$$V_0 \sin(\omega t) = I_0 \sin(\omega t) R$$

$$V_{rms} = I_{rms} R$$

$$P_R = V I$$

$$P = I^2 R$$

$$P = I_0^2 \sin^2(\omega t) R$$

$$P_{avg} = I_{rms}^2 R$$

Inductors

$$V_L = L \frac{dI}{dt}$$

$$I = I_0 \sin(\omega t)$$

$$V_L = L I_0 \omega \cos(\omega t)$$

$$= V_0 \cos(\omega t)$$

$$P = V I$$

$$= V_0 I_0 \sin(\omega t) \cos(\omega t)$$

$$= V_0 I_0 \frac{1}{2} \sin(2\omega t)$$


$$P_{avg} = 0$$

$$V_{rms} = I_{rms} X_L$$

• Block high-f

$X_L =$ Inductive Reactance

$$X_L = \omega L = 2\pi f L$$

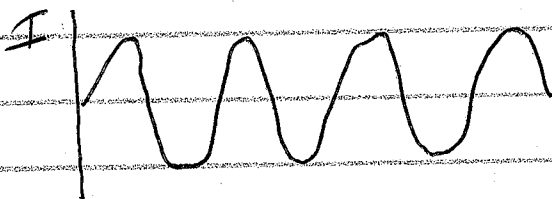

$$\text{Energy} = \frac{1}{2} L I^2$$

- High Freq
- High X_L
- Without high V_{rms} , little current

②

Capacitor - Break in circuit w/ lots of surface area.

$$V_c = Q/C$$

$$Q = CV$$

$$I = C \frac{dV_c}{dt}$$

Inductor Review

$$V_L = L \frac{dI}{dt}$$

• Current makes V_c increase

• Const $V \rightarrow$ Zero I

• Doesn't use power on average.

• Voltage makes $I \uparrow$

• Const $I \rightarrow$ Zero V

$$I = I_0 \sin(\omega t)$$

$$Q = \int I dt = \frac{I_0}{\omega} \cos(\omega t)$$

$$V = \frac{Q}{C} = \left(\frac{I_0}{\omega C} \right) (-\cos(\omega t))$$

\downarrow
 V_0

$$V_{rms} = I_{rms} X_C$$


• Blocks Low-f

$X_C =$ Capacitive Reactance

$$= \frac{1}{\omega C} = \frac{1}{2\pi f C}$$

③

LC Circuit

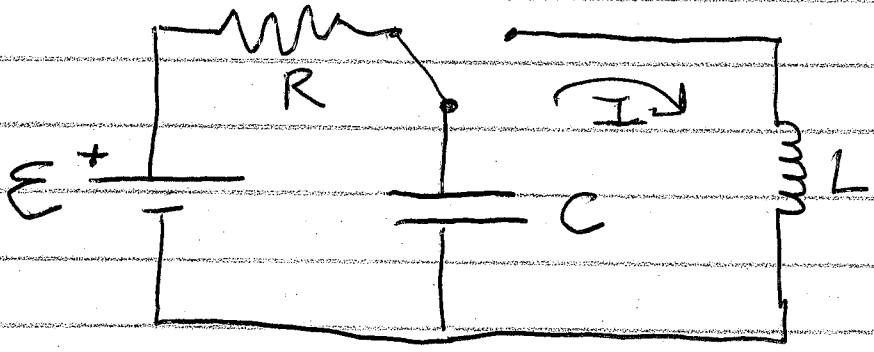

Preparation: Charge the cap thru the resistor.

Eventually: $V_C = E$

At $t=0$: Flip the switch to the inductor.
The voltage makes the current increase.

Energy = const

$$\frac{1}{2} C E_0^2 = \frac{1}{2} L I_0^2$$

$$V_C = V_L$$

$$Q/C = L \frac{dI}{dt}$$

$$I = -\frac{dQ}{dt}$$

$$\frac{dQ}{dt} / C = L \frac{d^2 I}{dt^2}$$

$$\omega^2 = \frac{1}{LC}$$

$$+I = -LC \frac{d^2 I}{dt^2}$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$\frac{1}{LC} I = \frac{d^2 I}{dt^2}$$

$$f = \frac{1}{2\pi\sqrt{LC}}$$



Solution: $I = I_0 \sin(\omega t) + B \cos(\omega t)$

$$\frac{d^2 I}{dt^2} = -I_0 \omega^2 \sin(\omega t)$$

$$= -I_0 \frac{1}{LC} \sin(\omega t)$$

①

Transformers

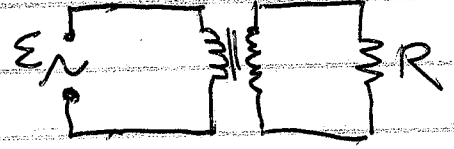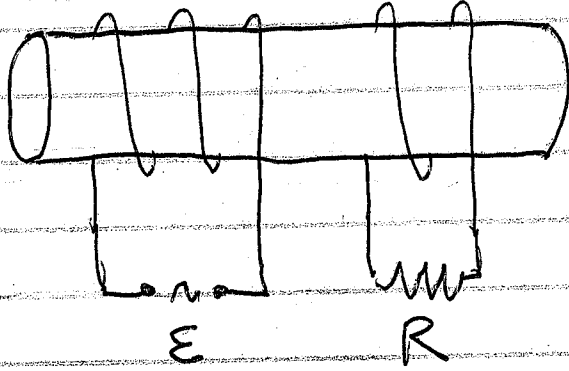

In a transformer:

- E is applied to the primary
 - AC current flows
 - Oscillating B
- Secondary coil "feels" B
 - Φ_B oscillates
 - \mathcal{E} generated
- Load (R) attached to secondary
 - \mathcal{E}_2 pushes I_2 in load.

$$\Phi_p = N_p \Phi_1$$
$$\Phi_s = N_s \Phi_1$$


$$\Phi_1 = BA = \text{flux in 1 loop}$$

$$\boxed{\mathcal{E}_p I_p = \mathcal{E}_s I_s}$$

$$\mathcal{E}_p = N_p \mathcal{E}_1$$
$$\mathcal{E}_s = N_s \mathcal{E}_1$$

$$\text{Voltage Ratio} = \frac{\mathcal{E}_s}{\mathcal{E}_p} = \frac{N_s}{N_p} = \text{Turns Ratio}$$

3

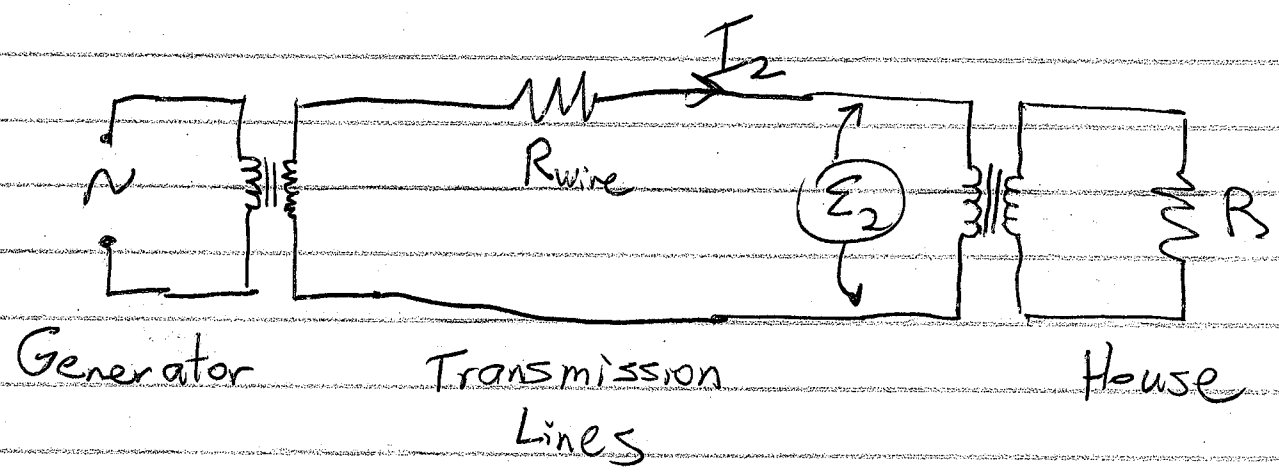

$$\text{Power Lost} = I^2 R_{\text{wire}}$$

$$\text{Power Transmitted} = \mathcal{E}_2 I_2$$