

① Phys 2426 2016-10-25 Lec 18

Reddit Educational GIFs (Don't get Lost)  
3-Phase AC Motor

Resistor - Opposes Current

$$V = IR$$
$$V_{rms} = I_{rms} R$$

Inductor - Opposes Change in Current

$$V_L = L \frac{dI}{dt}$$

$$X_L = 2\pi f L$$

$$V_{rms} = I_{rms} X_L$$

Capacitor - Opposes high Charge.

$$V_C = Q/C$$

Current changes charges


$$I = dQ/dt$$

$$X_C = \frac{1}{2\pi f C}$$

$$V_{rms} = I_{rms} X_C$$

AC Current

$I(t)$

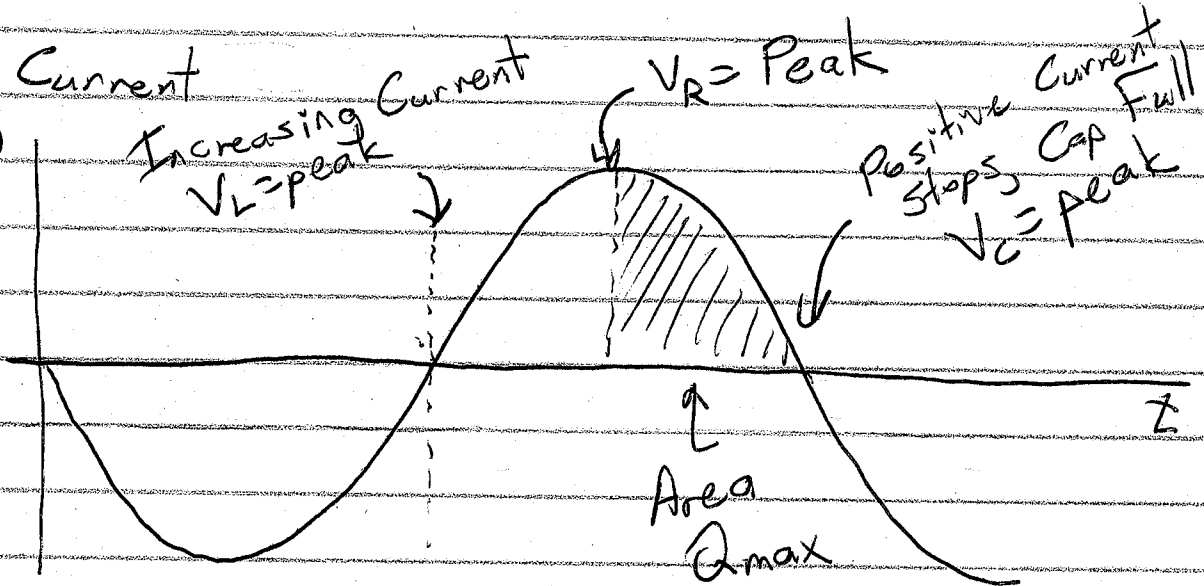

When  $V_C = \text{max}$ ,  $V_L = -(\text{max})$

② Phys 2426 2016-10-25

Series AC Circuit

$$I = I_0 \sin(2\pi ft)$$


$$I_R = I_L = I_C = I$$

$$V_R = I_0 R \sin(2\pi ft)$$

$$V_L = L \frac{dI}{dt} = L I_0 2\pi f \cos(2\pi ft)$$

$$= I_0 (2\pi f L) \cos(\omega t) = I_0 X_L \cos(\omega t)$$

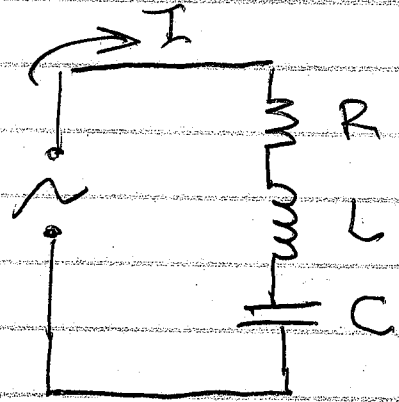
$$V_C = \frac{Q}{C} = \frac{1}{2\pi f C} I_0 \cos(\omega t)$$



$V_{Tot} = V_R + V_L + V_C$  as functions

Two Methods:

- Use trig identities
- Vector Addition

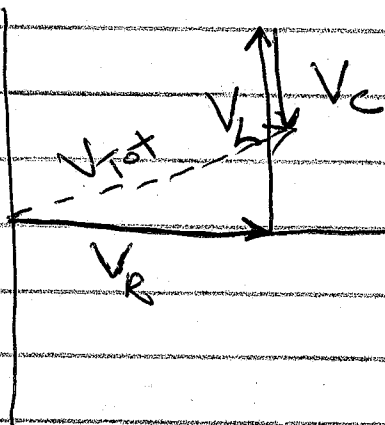

$$x: V_R$$
$$y: V_L - V_C$$

$$\text{mag: } \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$\phi = \text{atan} \left( \frac{V_L - V_C}{V_R} \right)$$

③ Phys 2426

2016-10-25

$$V_{\text{tot}} = V_R + V_L + V_C \quad (\text{vectors})$$

$$IZ = IR + IX_L + IX_C \quad (\text{vectors})$$

↑  
Impedance

① Reactance  $X = X_L - X_C$

② Impedance  $Z = \sqrt{R^2 + X^2}$

③  $V_{\text{net}} = IZ$

Ex:  $1 \text{ k}\Omega$ ,  $1.0 \text{ H}$ ,  $1 \mu\text{F}$  in series  
 $V = 140 \sin(500t) = V_{\text{max}}(\sin(2\pi f t))$

$$V_{\text{rms}} = \frac{140}{\sqrt{2}} = 99 \text{ V} \quad 2\pi f = 500$$

$$X_L = 2\pi f L = (500)(1.0) = 500 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{(500)(1 \times 10^{-6})} = 2000 \Omega$$

$$X = -1500 \Omega$$

$$Z = \sqrt{1000^2 + 1500^2} = 1803 \Omega$$


$$I = \frac{V}{Z} = \frac{99}{1803} = 0.0549 \text{ A}$$

Power:  $P = I^2 R$   
 $= 3.02 \text{ W}$

$$VA = I V = (0.0549)(99) = 5.44 \text{ VA}$$

④ Phys 2426 2016-10-25
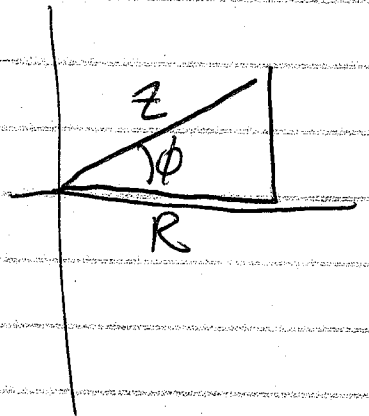
$$\frac{R}{Z} = \frac{1000}{1803} = 0.555 = \cos \phi$$



$$\frac{P}{IV_{\text{net}}} = \frac{3.02}{5.44} = 0.555$$

$$3.02 = (0.555)(5.44)$$

$$P_{\text{avg}} = \cos \phi V_{\text{rms}} I_{\text{rms}}$$

Power Factor

Pure R :  $\cos \phi = 1$

Mix LR:  $\phi > 0$   $\cos \phi < 1$

$$\tan \phi = \frac{X}{R}$$

$$\text{p.f.} = \cos \phi = \frac{R}{Z}$$

$$P_{\text{avg}} = (V_{\text{rms}})(I_{\text{rms}}) \cos \phi = I_{\text{rms}}^2 R$$

Resonance - IF  $X_L = X_C$ , they cancel.

$$X_L = X_C$$

$$2\pi f L = \frac{1}{2\pi f C}$$

$$f^2 = \frac{1}{(2\pi)^2 L C}$$

$$f = \frac{1}{2\pi \sqrt{LC}}$$

This is a special frequency: resonant frequency.  
The inductor & capacitor cooperate to  
pass current at  $f_R$ . Only  
the resistor impedes the current.

