

① Phys 2426

2016-09-13

Lec 7

For a single resistor: $V = IR$

$$P = IV$$


In simple circuit, $V = \mathcal{E}$.

↳ Battery voltage
↳ Device voltage

With multiple loads, the configuration is important.

Series Configuration

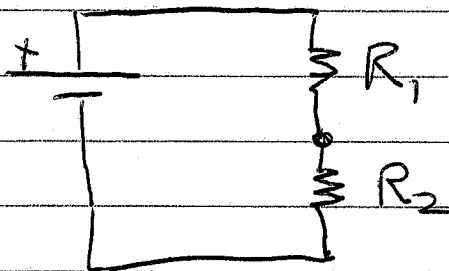- The current from one device is forced into the next device.




$$I_1 = I_2 = I$$

$$V_1 + V_2 = V_{net}$$

- In series, devices have the same current
- In series, an individual charge loses its energy a bit at a time, eventually losing all.

②

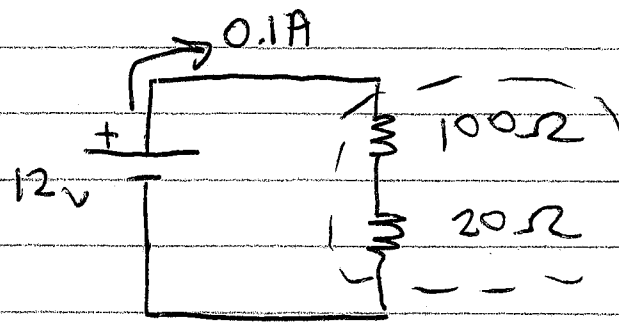


$$V_1 + V_2 = V_{net}$$

$$I(100\Omega) + I(20\Omega) = (12V)$$

$$I(120) = 12$$

↑
 $I = 0.1 A$
 looks like Ohm's Law

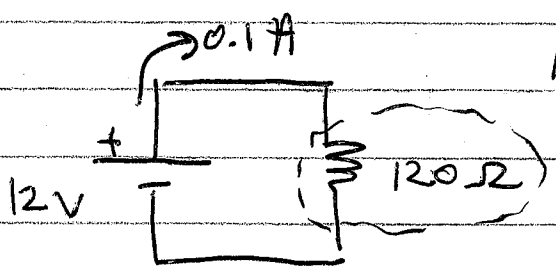

Equivalent Circuit

In general:

$$V_1 + V_2 + \dots = V_{net}$$

$$IR_1 + IR_2 + \dots = IR_{net}$$

$$R_1 + R_2 + \dots = R_{net}$$

Notes:

- Inserting $R_3 = 0$ does nothing
 ↳ "good" wire
- Inserting $R_3 = \infty$ blocks the current
 ↳ "broken" wire
- An ammeter in series:
 - measures the same current as your device.
 - has $R = 0$ to avoid affecting the result.

③

Internal Resistance, - resistance built in to a battery that acts like it's in series.

- Adds to R_{net} .
- "Drops" some voltage.

$$V_{net} = V_1 + V_2$$


$$\mathcal{E} = V_{int} + V_{ext}$$

$$\mathcal{E} = IR_{int} + V_{ext}$$

$$\mathcal{E} - IR_{int} = V_{ext}$$

Ex: Lights dim when microwave runs.

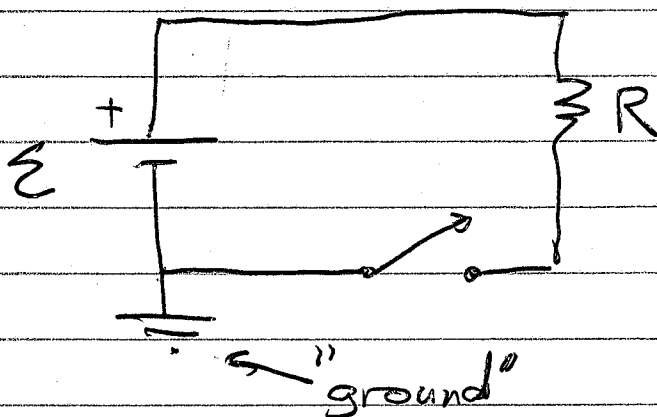- I increases
- More voltage is lost,
- Less $V_{ext} \rightarrow$ dim lights




$$\mathcal{E} = V_R + V_{switch}$$

Diagram illustrating the voltage equation $\mathcal{E} = V_R + V_{switch}$. The EMF \mathcal{E} is shown on the right with an upward arrow. The voltage across the resistor V_R is shown on the left with an upward arrow. The voltage across the switch V_{switch} is shown on the right with an upward arrow.

4

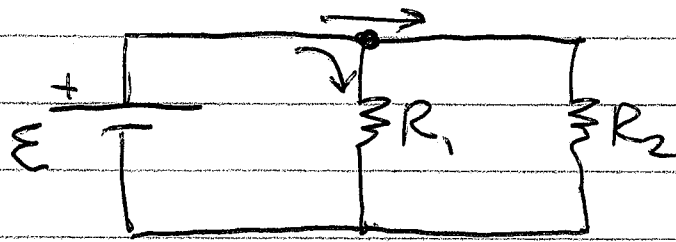Parallel Configuration - Circuit has branches where current must choose a path. For true parallel, current splits and merges.



$$I_1 + I_2 = I_{\text{net}}$$

$$V_1 = V_2 = V$$

- The current splits, and the branch currents add up to the total.
- Any one charge loses the same voltage regardless of which branch it chooses.

$$(I = pVA)$$

$$I_1 + I_2 = I_{\text{net}}$$

$$\frac{V}{R_1} + \frac{V}{R_2} = \frac{V}{R_{\text{net}}}$$


$$\frac{1}{R_1} + \frac{1}{R_2} = \frac{1}{R_{\text{net}}}$$

Inverse resistances add in parallel.
Similar to pythagorean theorem.
Inverse is (-1) power.


5

Combination Circuit - can analyze many (not all) circuits with equivalents.

Ex:

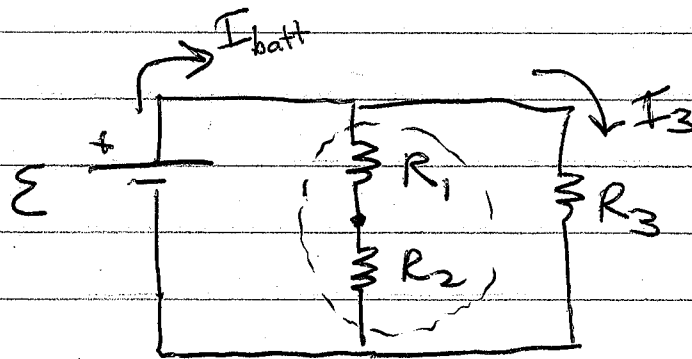

Find some series or parallel part.

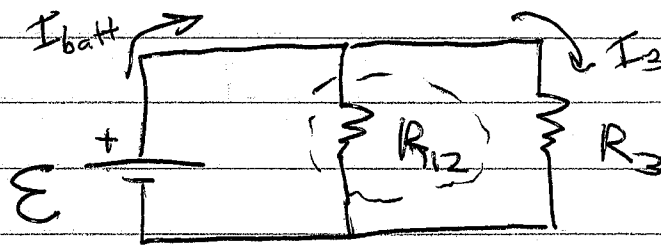

$$R_{12} = R_1 + R_2$$

What details are the same?

$$I_{batt}$$

$$\varepsilon$$

$$I_3$$

$$V_3$$



$$I_1 = I_2 = I_{12}$$

$$V_1 + V_2 = V_{12}$$

Note: V_{12} doesn't really transfer

6

Ex:

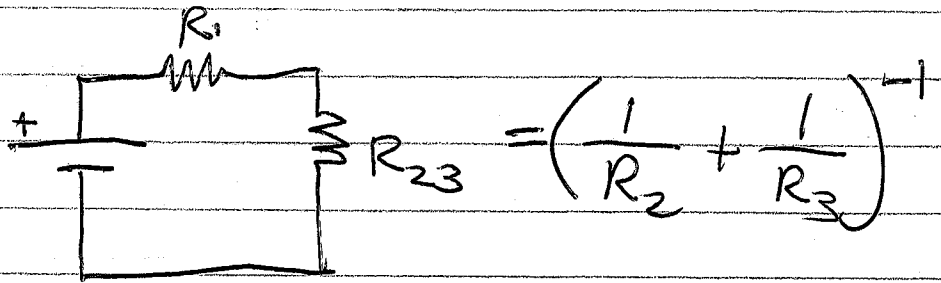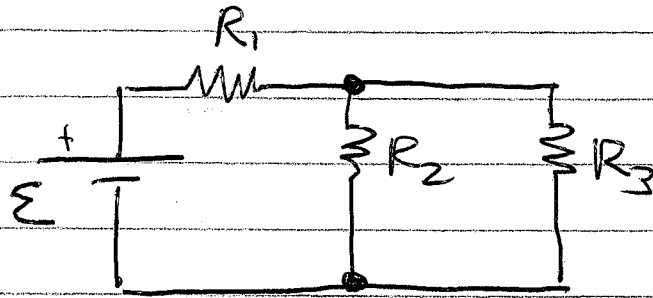

What transfers from easy to complicated version?

$$\begin{array}{l} I_{\text{batt}} \\ I_1 \\ I_2 + I_3 = I_{23} \end{array}$$

$$\begin{array}{l} \mathcal{E} \\ V_1 \\ V_2 = V_3 = V_{23} \end{array}$$