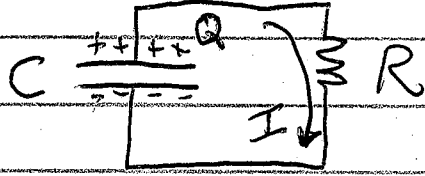


① Phys 2426

2017-09-26

lec 7

Trying to power a resistor with a capacitor:



Capacitor: $Q = CV$
 Resistor: $V = IR$

This current drains the cap: $I = -\frac{dQ}{dt}$

$\frac{V}{R} = -C \frac{dV}{dt}$ ← $\frac{V}{R} = -\frac{d}{dt}(CV)$

$\frac{dV}{dt} = -\frac{1}{RC} V$


Note: $\frac{d}{dt} e^t = e^t$ $\frac{d}{dt} e^{-t/\tau} = -\frac{1}{\tau} e^{-t/\tau}$

$\frac{d}{dt} (V_0 e^{-t/\tau}) = V_0 \frac{-1}{\tau} e^{-t/\tau}$

$V = V_0 e^{-t/\tau}$ is the solution

as long as $\tau = RC$

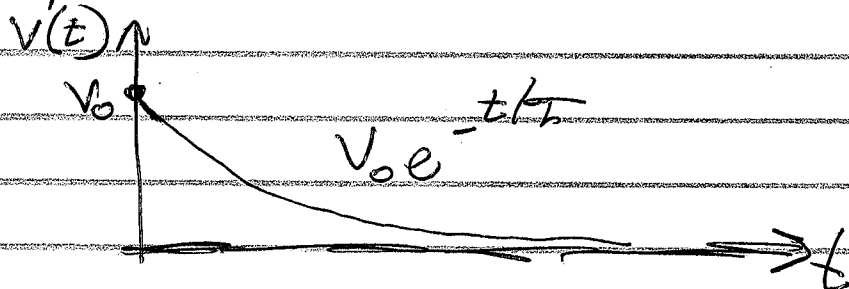Analogy: Drain a tank of water thru a straw.



②

What is $e^{-t/\tau}$?

Fraction of charge remaining.

What is t/τ ?

Amount of time since start, measured as a "number of time constants"

	t/τ	$\exp(-t/\tau)$	
Start	0.0	1.0	100%
Half-Life \rightarrow	0.5	0.61	61%
	0.693	0.5	50%
	1.0	0.37	37%
	2.0	$(0.37)^2 = 0.14$	14%
	:		
	5.0	0.01	1%

After 5.0 time constants, basically done.

Note: $e = 2.718$ vs. $e = 1.6 \times 10^{-19} \text{ C}$

$$\tau = RC$$

(3)

RC Circuit Set up For Discharge

$$\text{Initial Voltage} = 8.0 \text{ V}$$

$$\text{Resistor} = 500 \Omega$$

After 2.0 s, current is measured:

$$I = 0.010 \text{ A}$$

What is C?

How? Want to use $\tau = RC$

Need τ :

$$V = V_0 \exp(-t/\tau)$$

$$(5.0 \text{ V}) = (8.0 \text{ V}) \exp(-(2.0 \text{ s})/\tau)$$

$$V = IR = (0.010 \text{ A})(500 \Omega) = 5.0 \text{ V}$$

$$\frac{5.0 \text{ V}}{8.0 \text{ V}} = 0.625 = \exp(-t/\tau)$$

$$\ln(0.625) = -(2.0 \text{ s})/\tau$$

$$-0.47 = -(2.0 \text{ s})/\tau$$



$$0.47 \tau = (2.0 \text{ s})$$

$$\tau = 4.26 \text{ s}$$


$$\tau = RC \rightarrow C = \frac{\tau}{R} = \frac{4.265}{500 \Omega} = 0.00851 \text{ F} \\ = 8.51 \text{ mF} = 8510 \mu\text{F}$$

(4)

Charging:

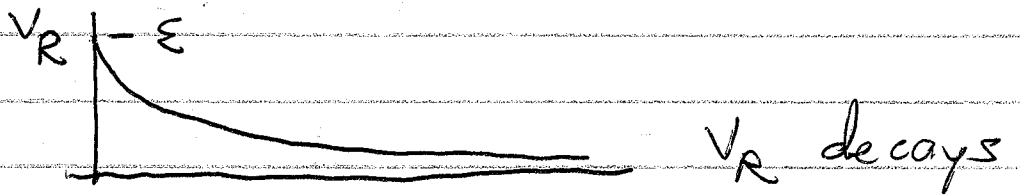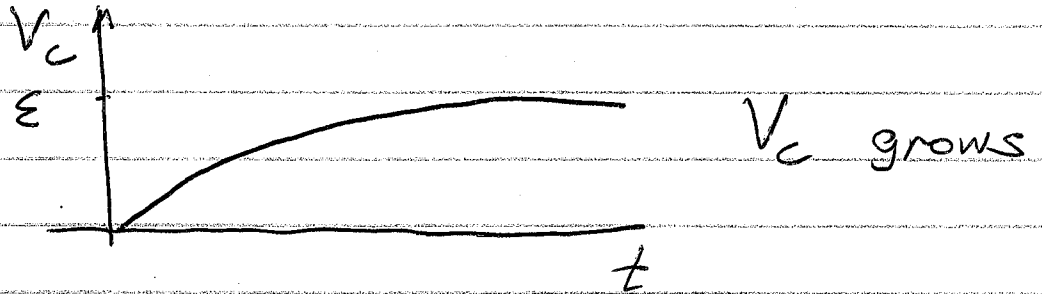
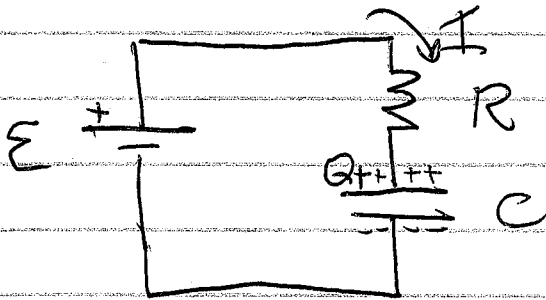
$$V_c + V_R = E = \text{Battery voltage}$$



$V \neq$

$$V_c + \epsilon e^{-t/\tau} = E$$

$$V_c = E - \epsilon e^{-t/\tau} = V_f (1 - e^{-t/\tau})$$

$$\uparrow V_f = E$$

I "looks like" V_R
 Q "looks like" V_c
 $I = +dQ/dt$

⑤

Temperature Coefficients

$\alpha \Delta T =$ relative change

For resistance $\frac{\Delta R}{R_0} = \alpha \Delta T$

$$\frac{R - R_0}{R_0} = \alpha (T - T_0)$$

$$R = R_0 + R_0 \alpha (T - T_0) \\ = R_0 (1 + \alpha (T - T_0))$$


$\alpha = 0.005$ means 0.5% increase per degree

$\alpha = \oplus$ = metals

$\alpha = \ominus$ = semiconductor

6

Gauss's Law

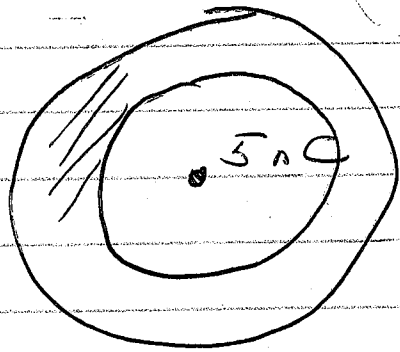

metal shell w/
 $Q_{net} = 8 \text{ nC}$

Small r : Inside shell
only 5 nC matters

$$E = \frac{k(5 \text{ nC})}{r^2}$$

$$\Phi = 4\pi k Q_{enc} = 4\pi (9 \times 10^9 \text{ Nm}^2/\text{C}^2)(5 \text{ nC}) \\ = 180\pi \text{ (N/C) m}^2$$

Large r : Outside shell:

$$\Phi = 4\pi k (5 + 8 \text{ nC}) = 468\pi \text{ (N/C) m}^2$$

$$E = \frac{k(13 \text{ nC})}{r^2}$$

Middle r : Embedded in metal.

$$E = 0$$

$$\Phi = EA = 0$$

$$Q = 0 = +5 \text{ nC} + Q_{inner}$$

$$Q_{inner} = -5 \text{ nC}$$

$$Q_{net} = Q_{in} + Q_{out}$$

$$8 \text{ nC} = -5 \text{ nC} + Q_{out}$$

$$13 \text{ nC} = Q_{out}$$