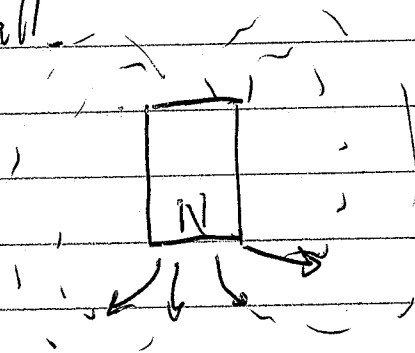


EM Induction - Voltage generated by varying magnetic flux.

$$\mathcal{E} = - \frac{d\Phi_B}{dt}$$

↑ Lenz's Law


The direction of the EMF is such that the induced current (if it exists) creates a magnetic field that opposes the change in flux that started it all.



As the magnet approaches:

- $\vec{B}$  points down
- $|\Phi_B|$  is increasing.

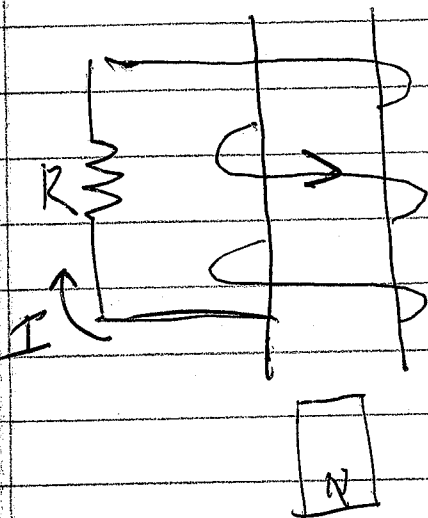- Coil fights that by making  $\vec{B}_{ind} = (\text{up})$
- Induced  $I$  is to right on front side.
- $I$  is up thru  $R$ .



As the magnet leaves:


- $|\Phi_B|$  is decreasing
- $B_{ind} = (\text{Down})$
- $I = \text{reverse of previous}$ .

②

## AC Electricity

- Varying Voltage  $\rightarrow$  Varying  $I$
- Varying  $I \rightarrow$  Varying  $B$
- Varying  $B \rightarrow$  Induced  $\mathcal{E}$

## AC Generator

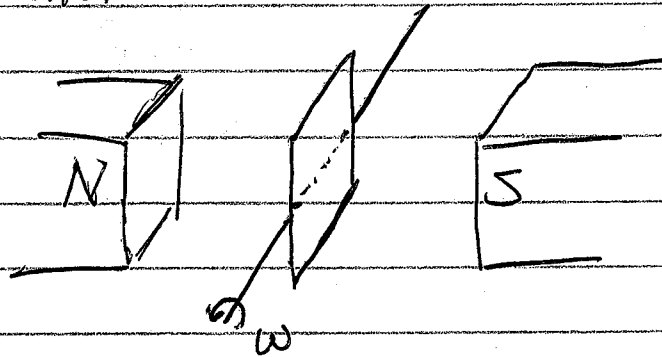

Magnetic Flux

$$\Phi_B = NBA \cos(\omega t)$$


$$\mathcal{E} = NBA\omega \sin(\omega t)$$

- $\omega =$  angular speed in  $\text{rad/s} = \text{s}^{-1}$
- $f =$  frequency in  $\text{rev/s} = \frac{\text{cycles}}{\text{s}} = \text{Hz}$

$$\omega = 2\pi f$$

AC Wave Form  $\mathcal{E} = \mathcal{E}_{\text{max}} \sin(2\pi f t)$   
Amplitude  $\rightarrow$

(2)

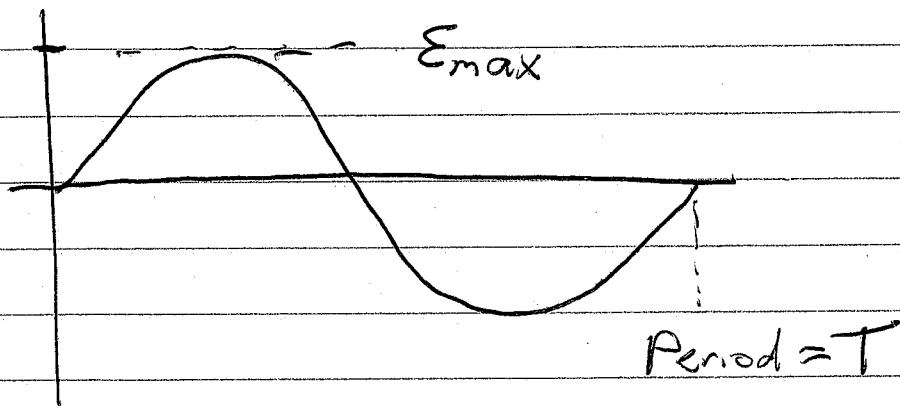

$\sin(\theta)$  repeats when  $\Delta\theta = 2\pi$

$\sin(2\pi ft)$  repeats when  $\Delta(2\pi ft) = 2\pi$   
 $f\Delta t = 1$

$$fT = 1$$

$$f = 1/T \quad T = 1/f$$

## Resistors in AC

$$V = IR$$

$$V_{\max} \sin(2\pi ft) = IR$$

Ohm's Law for instantaneous values

$$\frac{V_{\max}}{R} \sin(2\pi ft) = I = I_{\max} \sin(2\pi ft)$$

$$V_{\max} = I_{\max} R$$

Ohm's Law for Amplitudes


(14)

## Resistor Power in AC

Used Power is  $P = IV = I^2 R$

$$P = (I_{\max} \sin(2\pi ft))^2 R$$

$$= I_{\max}^2 R \sin^2(2\pi ft)$$

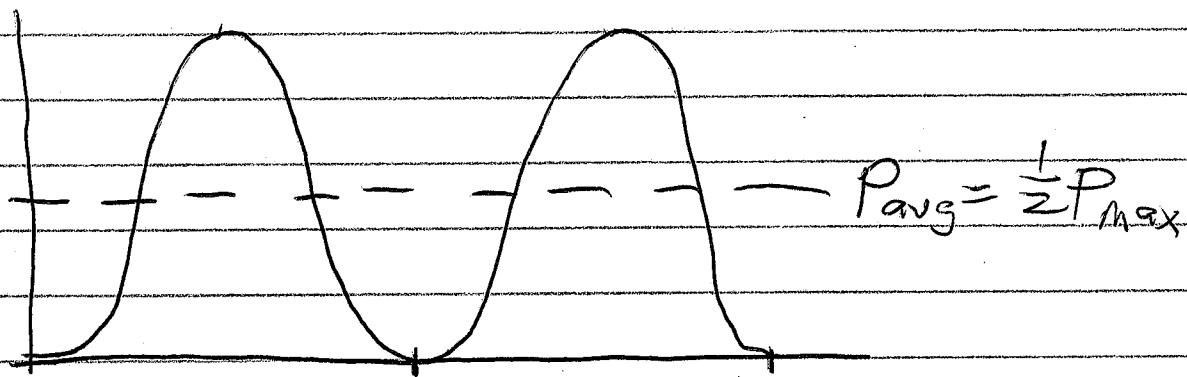

$$\sin^2 \theta = \frac{1}{2} (1 - \cos(2\theta))$$

$$P_{\max} = I_{\max}^2 R$$

← looks like DC formula

$$v_{\text{avg}} = \frac{\Delta x}{\Delta t}$$

$$P_{\text{avg}} = \frac{\Delta \text{Energy}}{\Delta t}$$

$$P_{\text{avg}} = \frac{1}{2} P_{\max} = \frac{1}{2} I_{\max}^2 R = I^2 R$$

$$\frac{1}{\sqrt{2}} I_{\max} = I_{\text{RMS}}$$

$$V_{\text{RMS}} = I_{\text{RMS}} R$$

⑤

In the US:  $V_{RMS} = 120\text{ V}$   
 $f = 60\text{ Hz}$


Ex: 6W Bulb

$$P_{avg} = V_{RMS} I_{RMS}$$
$$6\text{ W} = (120\text{ V}) I_{RMS}$$
$$0.05\text{ A} = I_{RMS}$$

$$V_{RMS} = I_{RMS} R$$
$$120\text{ V} = (0.05\text{ A}) R$$
$$2400\ \Omega = R$$

### Capacitors in AC

$$Q = CV$$

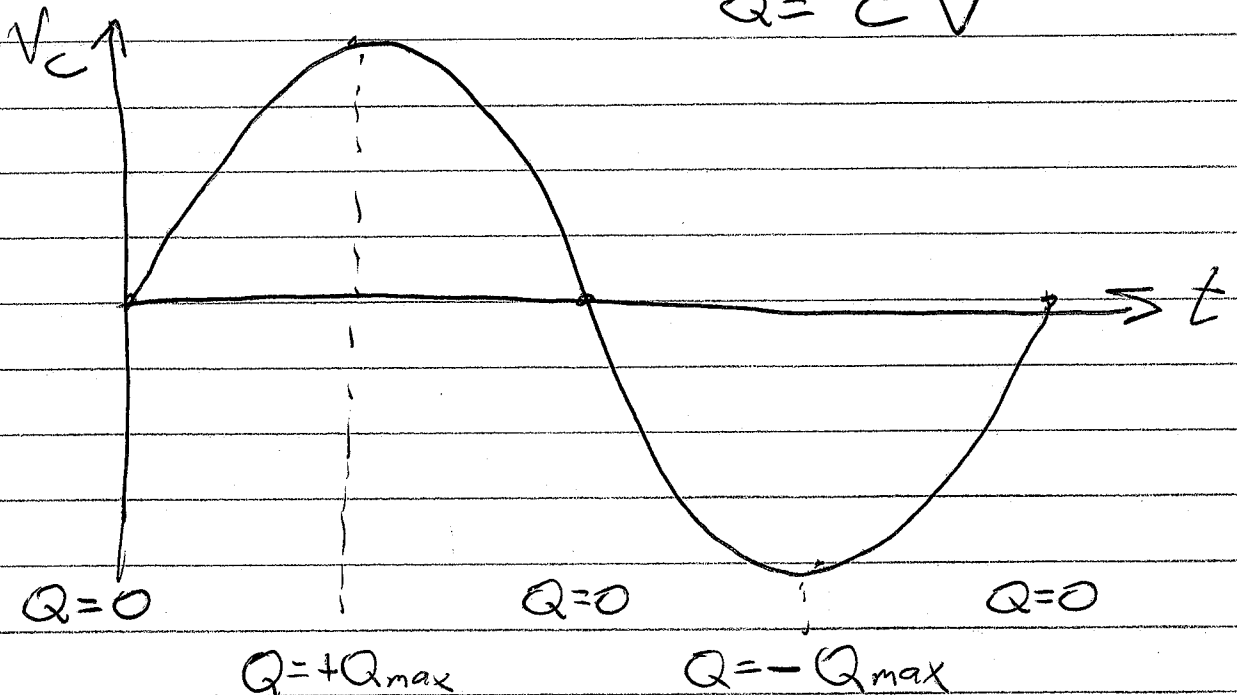

$Q$  increasing

$$I = +I_{max}$$

$$I = 0$$

$Q$  decreasing

$$I = -I_{max}$$

$$I = 0$$