

## Capacitors in AC

What we know:

- Store Charge
- Take time to charge or discharge
- Store Energy

$$Q = CV$$

$$\tau = RC$$

$$\text{Energy} = \frac{1}{2} CV^2$$

What happens in AC?

$$Q = CV$$

Time derivative  $\rightarrow$

$$\dot{Q} = C \dot{V}$$

$$I = C \frac{dV}{dt}$$


$$V = V_{\max} \sin(2\pi f t)$$

If  $V = V_{\max} \sin(2\pi f t)$

$$\dot{V} = V_{\max} \cos(2\pi f t) 2\pi f$$

$$I = V_{\max} 2\pi f C \cos(2\pi f t)$$

⊗ = High Energy

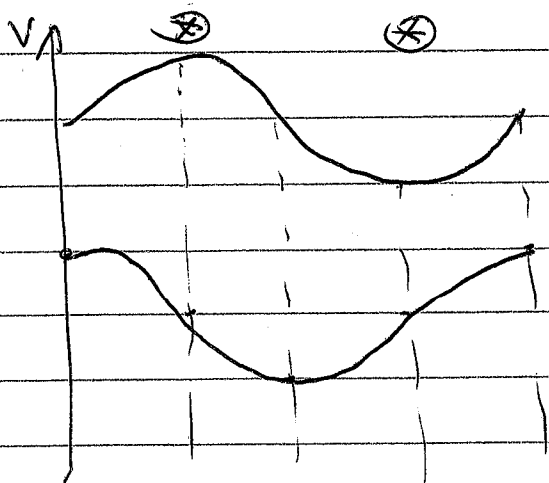

$$P = VI$$

$$= V_{\max} I_{\max} \sin() \cos()$$

$$= V_{\max} I_{\max} \frac{1}{2} \sin(2(2\pi f t))$$

Average  $P = 0$

$$V = IR$$

②

AC Ohm's Law For Cap:

$$I_{\max} = V_{\max} 2\pi f C$$

$$V_{\max} = I_{\max} \left( \frac{1}{2\pi f C} \right)$$

$$V_{\max} = I_{\max} X_c$$


Reactance ( $X_c$ ) is in ohms ( $\Omega$ )

Capacitors have high reactance when:


- Low  $C$

- Low  $f$  (DC, is  $f=0$ )

Capacitors "block" DC and low- $f$ .

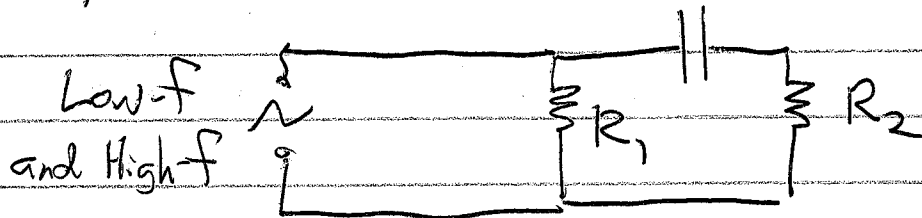

$R_2$  gets more high- $f$

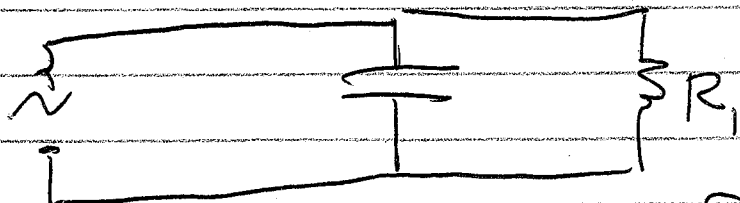

$R_1$  gets low- $f$

③

Inductors - Devices that "feel" their own magnetic field,

Ex: Solenoid Coil  $B = \frac{\mu_0 N I}{l}$

Faraday's Law:  $\mathcal{E} = - \frac{d\Phi_B}{dt}$

Flux of coil's field:  $\Phi_B = B \cdot A$  (one loop)

$\Phi_B = NBA$  (whole coil)

$$\Phi_B = N \left( \frac{\mu_0 N I}{l} \right) A$$


$$\Phi_B = \left( \frac{\mu_0 N^2 A}{l} \right) I = L I$$

Inductance ( $L$ ) is measured in henries ( $H$ )

Take derivative:  $\mathcal{E} = L \dot{I}$

The EMF of  $L$  fights  $\dot{I}$

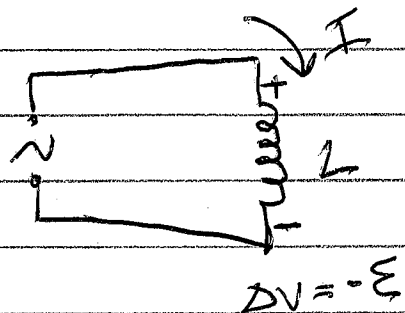As a passive device, we drop the  $\ominus$  sign.



④

$$\text{If } V = V_{\max} \sin(2\pi ft)$$

$$\text{Guess } I = -I_{\max} \cos(2\pi ft)$$

$$\dot{I} = I_{\max} \sin(2\pi ft) \cdot 2\pi f$$

$$V = I_{\max} 2\pi f L \sin(2\pi ft)$$

$$V_{\max} = I_{\max} 2\pi f L$$

$$V_{\max} = I_{\max} X_L$$

For the inductor:

Low  $f \Rightarrow$  Low  $X_L \Rightarrow$  Easy current flow.

Power of Inductor:

$$P = VI = \sin(\quad) \cos(\quad)$$
$$= \frac{1}{2} \sin(2\quad)$$

$$P_{\text{avg}} = 0$$


Energy of Inductor

$$\text{Energy} = \frac{1}{2} L I^2$$

$$\text{Capacitor Energy} = \frac{1}{2} C V^2$$

5

### Solenoid Relay:

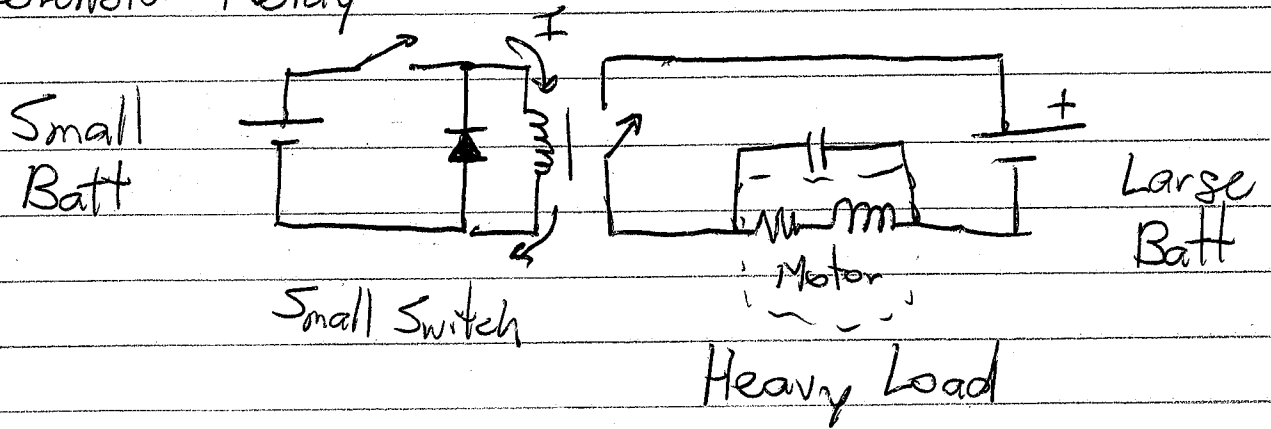


When you disconnect a ~~resistor~~ coil,  $|I|$  is huge,  
 This generates large EMF,  
 This wrecks switches.

Protection options: 1. Diode  
 2. Capacitor

### Series AC Circuit Intro

$V_{max}$   
 $f$

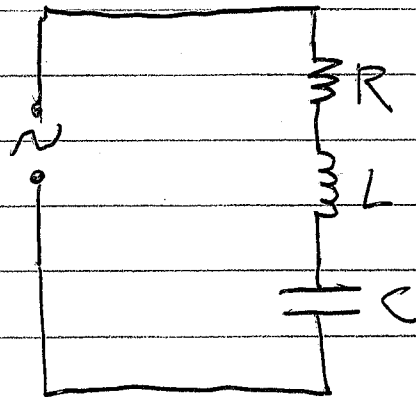

$$V_R = I_{max} R \sin(2\pi f t)$$

$$V_L = L \dot{I} = I_{max} 2\pi f L \cos(2\pi f t)$$

$$V_C = \frac{1}{C} \int I dt = I_{max} \frac{1}{2\pi f C} (-\cos(2\pi f t))$$

Propose  $I = I_{max} \sin(2\pi f t)$

$$V_{tot} = V_R + V_L + V_C$$