

AC Ohm's Law

$$V_{rms} = I_{rms} Z$$

Impedance (Z) is a generalized resistance used for AC.


Resistor : $Z = R$

Inductor : $Z = X_L = 2\pi f L$

Capacitor : $Z = X_C = 1/(2\pi f C)$

Series AC Circuit:

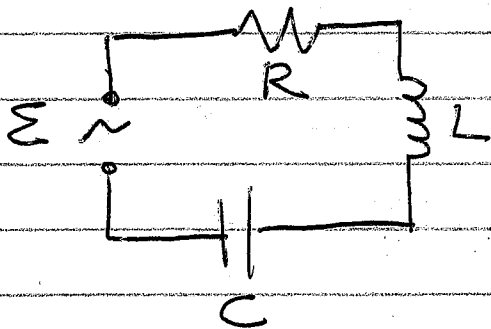- Same Current (I) everywhere, (Both $I(t)$ and I_{rms})
- Voltage Adds, but only as $V(t)$.



$$\Sigma = V_R + V_L + V_C$$

(As functions of time)

$$\Sigma = V_R \cos \theta + V_L \sin \theta - V_C \sin \theta$$

(For $I = I_{max} \cos \theta$)

$$\theta = 2\pi f t$$

$$\Sigma = V_R \cos(2\pi f t) + (V_L - V_C) \sin(2\pi f t)$$

$$\Sigma = \Sigma_{max} \cos(2\pi f t + \phi)$$

$$\Sigma_{max}^2 = V_R^2 + (V_L - V_C)^2$$

$$\tan \phi = \frac{V_L - V_C}{V_R}$$

equivalent

②

Dealing with AC Circuits:

- Think of R as the x -direction
- X_L is the $+y$ -dir
- X_C is the $-y$ -direction

Series: Z 's add as vectors.

Problem: Can't divide by vectors.

Solution: Use complex numbers = phasors.

Series Result: Total x : R

Total y : $X_L - X_C = X$

Total Magnitude: $Z = \sqrt{R^2 + X^2}$

③

Ex: $R = 1 \text{ k}\Omega$ $L = 1.0 \text{ H}$ $C = 1.0 \mu\text{F}$
In series

$$V_{\text{tot}} = 140 \sin(500t) \\ = V_{\text{max}} \sin(2\pi f t)$$

$$I_{\text{rms}} = ?$$

$$V_{\text{max}} = (140 \text{ V})$$

$$2\pi f = (500 \text{ s}^{-1})$$

$$V_{\text{rms}} = \frac{140 \text{ V}}{\sqrt{2}} = 99 \text{ V}$$

$$f = \frac{500}{2\pi} = 79.6 \text{ Hz}$$

Want to use :

$$V_{\text{rms}} = I_{\text{rms}} Z$$

$$\text{Need } X_L = 2\pi f L = 500 \Omega$$

$$(99 \text{ V}) = I_{\text{rms}} (1803 \Omega)$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{2\pi f \times 1 \times 10^{-6}} \\ = 2000 \Omega$$

$$I_{\text{rms}} = 0.0549 \text{ A}$$

$$X = X_L - X_C = -1500 \Omega$$

$$\tan \phi = \left(\frac{-1500}{1000} \right)$$

$$Z = \sqrt{1000^2 + 1500^2} \\ = 1803 \Omega$$

Power in AC — only the resistor.

$$P = V_R I_R = I^2 R = (0.0549 \text{ A})^2 (1000 \Omega) \\ = 3.02 \text{ W}$$

Compare to

$$V_{\text{tot}} I = (99 \text{ V})(0.0549 \text{ A}) = 5.4 \text{ VA}$$

$$\cos \phi = \frac{3.02}{5.4}$$

④

Because X_L and X_C subtract, they can cancel!

Cause

Effect

$$X_L = X_C$$

$$X = 0$$

$$2\pi fL = \frac{1}{2\pi fC}$$

$$Z = \sqrt{R^2 + X^2} = \sqrt{R^2} = R$$

$$2\pi f = \frac{1}{\sqrt{LC}}$$

(As small as possible)

$$f_R = \frac{1}{2\pi\sqrt{LC}}$$

$$V_{rms} = I_{rms} R$$

↑
Resonance freq.

For const V_{rms} , this freq
gives large I_{rms}

this is a resonant circuit.

Above example: $f_R = \frac{1}{2\pi\sqrt{(1.0)(1 \times 10^{-6})}} = 159 \text{ Hz}$

At resonance: $X_L = 2\pi fL = 2\pi(159)(1.0) = 999 \Omega$
 $X_C = 1/2\pi fC = 999 \Omega$


Impedance $Z = R = 1000 \Omega$ — coincidence!

$$I_{rms} = \frac{99V}{1000\Omega} = 0.099 A$$

5

Transformers - Use AC to generate voltage,
current

Two coils w/ interconnected B fields.

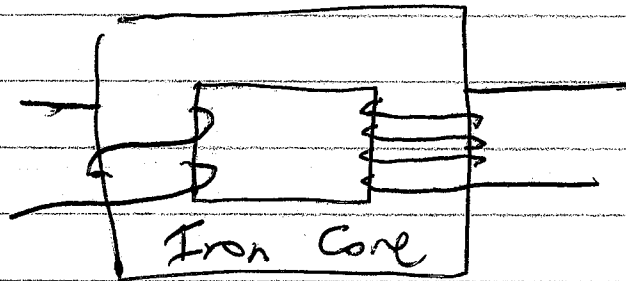

- Force AC Current thru "primary"
- This causes AC B oscillations
- This causes oscillating Φ_B
- This generates oscillating \mathcal{E}_p and \mathcal{E}_s .

Flux per loop: $\Phi_1 = \iint \vec{B} \cdot d\vec{A} = BA$

Take ratios of secondary to primary:

$$\frac{\Phi_s}{\Phi_p} = \frac{N_s \Phi_1}{N_p \Phi_1} = \frac{N_s \frac{d\Phi_1}{dt}}{N_p \frac{d\Phi_1}{dt}} = \frac{N_s}{N_p} = \frac{\mathcal{E}_s}{\mathcal{E}_p}$$


Power Transfer:

$$\mathcal{E} \mathcal{E}_p I_p = \mathcal{E}_s I_s$$

↑
Efficiency

⑥

Ex: Cell phone charger transformer

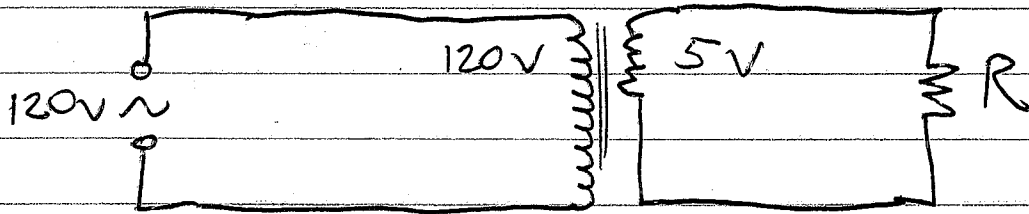

If $N_s = 100$, what is N_p ?

$$\frac{\epsilon_s}{\epsilon_p} = \frac{N_s}{N_p} \quad \frac{5V}{120V} = \frac{100}{N_p}$$

$$N_p = 2400$$

If $I_s = 1.5 A$ and $\epsilon = 1.0$

$$\epsilon_p I_p = \epsilon_s I_s$$

$$(120) I_p = (5)(1.5) \rightarrow I_p = 0.0625 A$$

Transmission Lines are resistors.

$$P_{\text{lost}} = I^2 R_{\text{wire}}$$

Why did any sparks shoot to helicopter?

