

① Phys 2426 2017-07-06 Lec 3

HW1 Due Sun Night (SMTE-0095 also)
Quiz 1 Monday

For two vectors to total zero;
They must be equal and opposite.


$$E_1 = E_2 \quad \text{Magnitudes!}$$

$$\frac{kQ_1}{r_1^2} = \frac{kQ_2}{r_2^2}$$


$$\frac{Q_1}{Q_2} = \frac{r_1^2}{r_2^2}$$

$$\frac{\sqrt{Q_1}}{\sqrt{Q_2}} = \frac{r_1}{r_2}$$

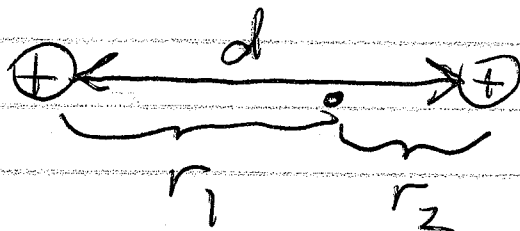IF the point is in between:
 $r_1 + r_2 = d$



IF the point is outside;

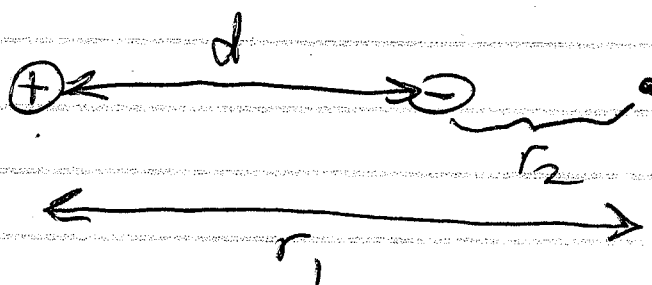

$$d + r_2 = r_1$$

(2)

Names for quantity measured in volts (V):

- Electric Potential (not potential energy)
- Potential Difference
- Electromotive Force (EMF)
- Voltage

Two main uses in electrostatics:

- Gives energy to charges

$$\Delta U = q \Delta V$$

Energy = Charge \cdot (~~the~~ Energy per Charge)

- Electric Field is negative gradient of V .

$$E_x = - \frac{dV}{dx}$$

↑
Component of \vec{E}

Vector \vec{E} points "downhill"


Average value $|E_{avg}| = \frac{\Delta V}{\Delta x}$

Recall $U_g = mgy$ $F_g = -mg = - \frac{dU_g}{dy}$

3

Parallel Plate Capacitor

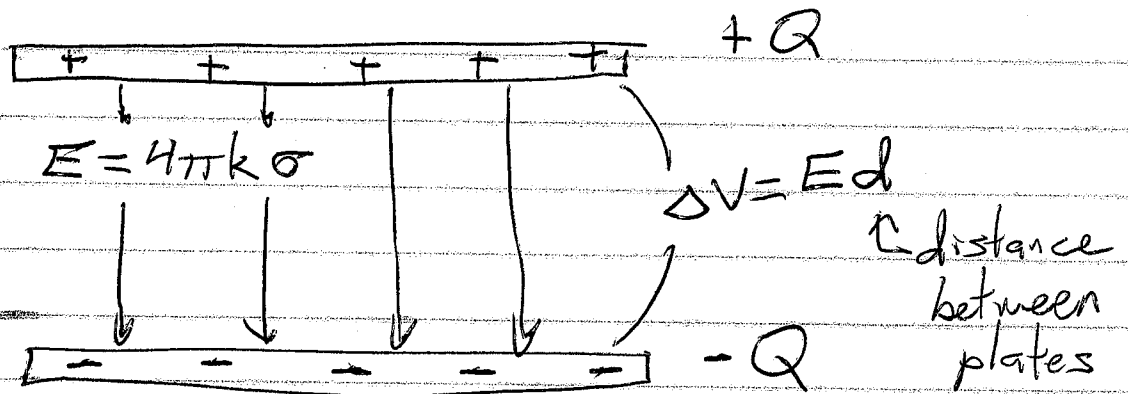- Stores Charges by keeping \oplus and \ominus nearby but separate.
- Need 2 hunks of metal



Charge density: $\sigma = Q/A$
 Note: E is propto Q

IF $E = -\frac{\Delta V}{\Delta x} \rightarrow \Delta V = -\int E dx = -E \Delta x$

ΔV is propto $Q \Rightarrow Q = CV$

Charge on one plate or other \rightarrow Capacitance \uparrow ΔV

$$Q = \sigma A = \frac{E}{4\pi k} A = \frac{V/d}{4\pi k} A = \frac{A}{4\pi k d} V = \frac{\epsilon_0 A}{d} V$$

④

Batteries vs. Capacitors

- Both store energy
- Both supply charges @ voltage.

Battery - chemical reaction generates voltage. Every q has same voltage.

$$\text{Total energy} = \int V dq = \boxed{VQ}$$

Ex: 3300 mAh battery

$$Q = 1.2 \times 10^4 \text{ C}$$

$$V = 4.5 \text{ V}$$

$$\text{Energy} = (1.2 \times 10^4 \text{ C})(4.5 \text{ V}) = 54000 \text{ J}$$

$$= 54 \text{ kJ}$$

Cost \$0.12 = 1 kWh = 3.6 MJ


$$\$1 = 30 \text{ MJ}$$

Capacitors - store energy in E-field 0.2¢

$$\text{Energy} = \int V dq = \int \frac{q}{C} dq = \frac{1}{C} \frac{q^2}{2}$$


$$q = CV \quad = \frac{1}{2} \frac{Q^2}{C} = \boxed{\frac{1}{2} QV}$$

$$= \frac{1}{2} CV^2$$

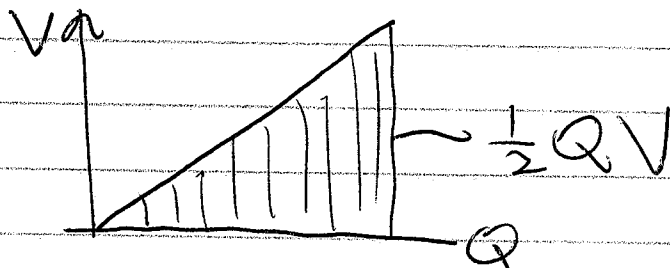

⑤ Capacitor in DC Circuit

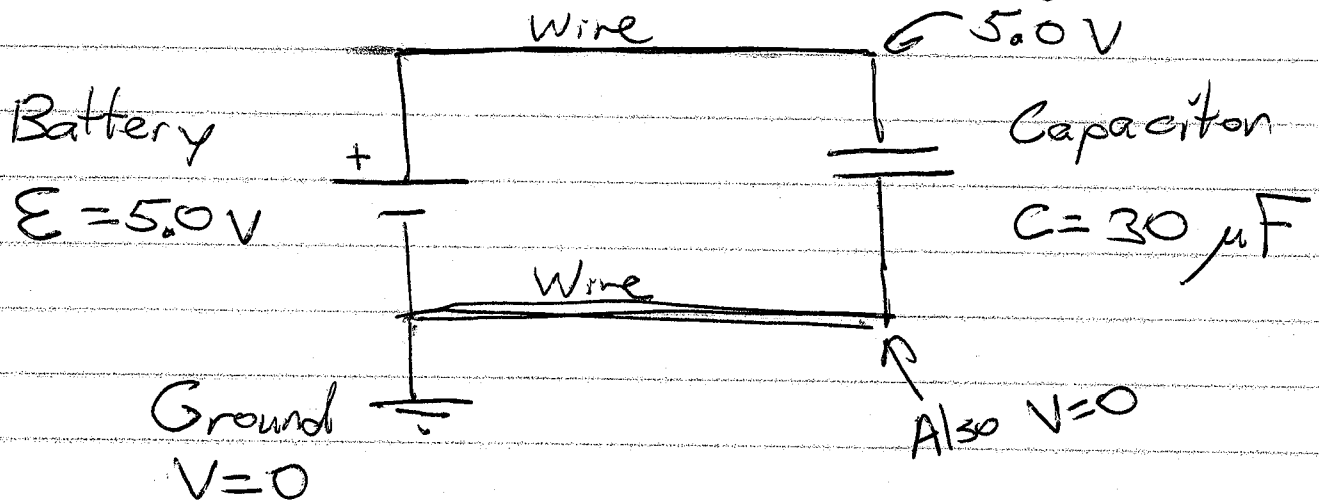
- Charges (and hence current) cannot flow through a capacitor.
- Metals are special in electrostatics,
 - $E=0$ inside metal
 - $\Delta V = -\int E_x dx = 0$
 - $V = \text{const}$
 - Wires are each "at a voltage" -



$V_c = 5.0 \text{ V}$
 (Cap is in parallel with battery.)

$$Q = CV = (30 \mu\text{F})(5.0 \text{ V}) = 150 \mu\text{C}$$

In Parallel:

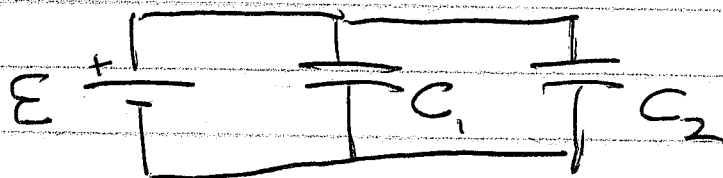

$$\mathcal{E} = V_1 = V_2$$

$$Q_{\text{Tot}} = Q_1 + Q_2$$


Acts like

$$Q_{\text{Tot}} = C_{\text{eff}} \mathcal{E}$$

⑥

Capacitor Puzzle

Initially:

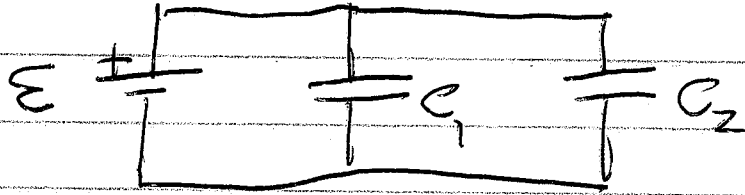

$$q_{1i} = C_1 \mathcal{E}$$


$$q_{2i} = C_2 \mathcal{E}$$

Then: Remove Battery.

Disconnect capacitors. q_1 is "stuck"

q_2 is "stuck"

Flip C_2 upside down.

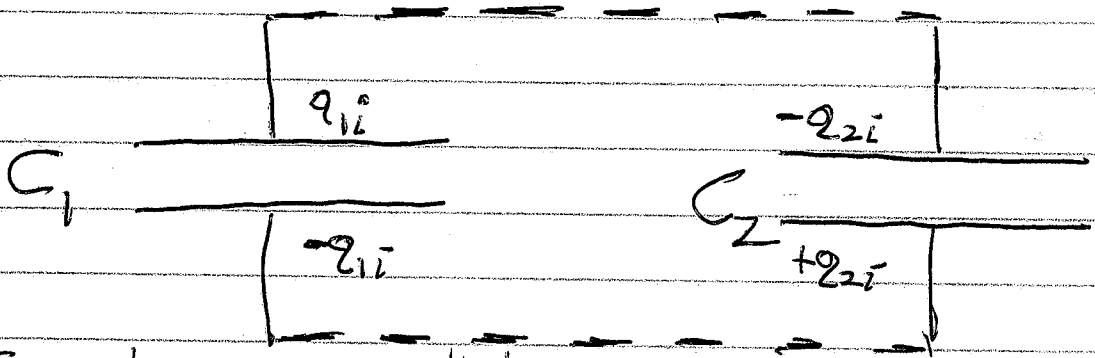

Connect in parallel.

$$q_{1f} = \dots$$
$$q_{2f} = \dots$$

parallel $\Rightarrow V_1 = V_2 = V$

Total charge can't change.

$$C_1 \mathcal{E} - C_2 \mathcal{E} = C_1 V + C_2 V$$

Before reconnect = After reconnect