

Phys 2426

2017-07-12

lec 6

## RC Circuits - Charging and Discharging

Common traits:


Capacitor	$C = 250 \mu\text{F}$
	$V_c$ varies
	$Q$ varies
	$I_c$ varies
Resistor	$R = 11 \text{ k}\Omega$
(in series w/ Cap)	$V_R = \text{varies}$
	$I_R = I_C$

In both:  $I = I_0 e^{-t/\tau}$   
Decaying Exponential  
 $\tau = RC$

$$\text{Ex: } \tau = (11 \times 10^3 \Omega) (250 \times 10^{-6} \text{ F}) \\ = 2.75 \text{ s}$$

Can express  $t$  relative to  $\tau$ :

$$\text{Ex: } t = 5.0 \text{ s}$$

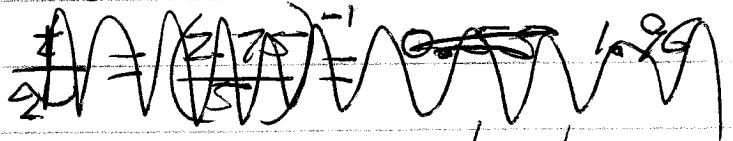

The time is <sup>1.82</sup> ~~0.505~~ time constants,

$$\frac{t}{\tau} = \frac{5.0 \text{ s}}{2.75 \text{ s}} = 1.82$$

②

$$\text{If } I = I_0 e^{-t/\tau} \quad \frac{I}{I_0} = e^{-t/\tau}$$

is the relative current.

$\frac{t}{\tau}$	$e^{-t/\tau}$
0	1
1	0.37
⋮	
5	

$$0.01 = 1\% \text{ left}$$

99% finished

Five time constants gets you 99% completed.


$$\text{Note: } \ln(e^{-t/\tau}) = -t/\tau$$

$$\text{Ex: } \ln(0.5) = -0.69$$

At  $0.69\tau$ , you're half way.

③

Discharging Circuit

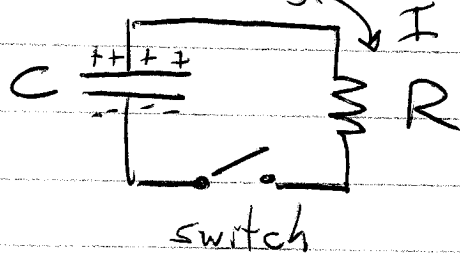

At  $t=0$   $Q=Q_0$   
and the switch gets closed.

Kirchoff's Voltage Law:  
CW Loop

$$+V_C - V_R = 0$$

$$\frac{Q}{C} - IR = 0$$

$$C_{cap}: Q = CV$$

$$V = Q/C$$

$$I = \frac{Q}{RC}$$

$$I = -\frac{dQ}{dt}$$

$$-\frac{dQ}{dt} = \frac{Q}{RC}$$

Guess:  $Q_0 e^{-t/\tau}$

$$\frac{dQ}{dt} = \frac{-1}{RC} Q$$

$$\frac{dQ}{dt} = Q_0 e^{-t/\tau} \cdot \frac{-1}{\tau}$$

$$= \frac{-1}{RC} Q_0 e^{-t/\tau} = \frac{-1}{RC} Q_0 e^{-t/\tau}$$

We now know  $\tau = RC$


$Q_0$  could be anything.

$$I = -\frac{dQ}{dt} = \frac{Q_0}{RC} e^{-t/\tau} = I_0 e^{-t/\tau}$$

$$V = IR = I_0 R e^{-t/\tau} = V_0 e^{-t/\tau}$$

4

Charging Circuit

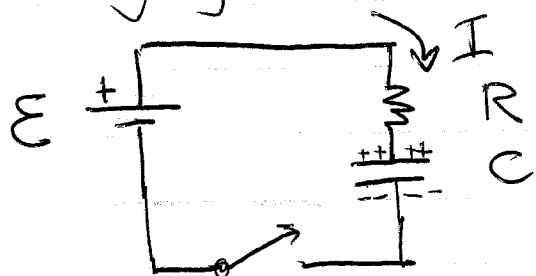

Initially:  $V_c = 0$   
 $Q = 0$

KVL: CW

$$V_{\text{Batt}} - V_R - V_c = 0$$

$$I = \frac{dQ}{dt}$$

$$\varepsilon - IR - \frac{Q}{C} = 0$$

$$\frac{d}{dt} \Rightarrow 0 - R \frac{dI}{dt} - \frac{1}{C} \frac{dQ}{dt} = 0$$

$$-R \frac{dI}{dt} - \frac{1}{C} I = 0$$

$$\frac{dI}{dt} + \frac{1}{RC} I = 0$$

$$\frac{dI}{dt} = -\frac{1}{RC} I$$

$$I = I_0 e^{-t/\tau} \quad \text{w/ } \tau = RC$$

$$Q = \int_0^t I(t) dt = \int_0^t I_0 e^{-t/\tau} dt$$

$$= I_0 e^{-t/\tau} (-\tau) \Big|_0^t$$

$$= -\tau I_0 [e^{-t/\tau} - 1] = \tau I_0 (1 - e^{-t/\tau})$$



$$= Q_{\text{max}} (1 - e^{-t/\tau})$$

5

## Charging Capacitor

$$I = I_0 e^{-t/\tau}$$

$$Q = Q_{\max} (1 - e^{-t/\tau})$$

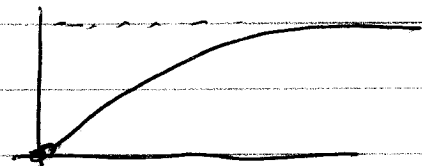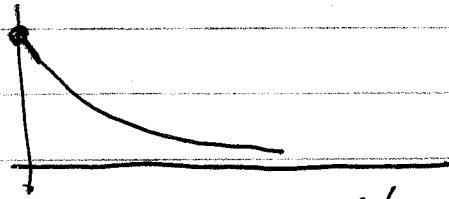

$$V_R = IR = V_{\max} e^{-t/\tau}$$

$$V_C = \frac{Q}{C} = V_{\max} (1 - e^{-t/\tau})$$

$$V_R + V_C = V_{\max} = \mathcal{E}$$

Ex:  $C = 250 \mu\text{F}$   
 $R = 11 \text{ k}\Omega$   
 $\mathcal{E} = 12 \text{ V}$

$$\tau = RC = 2.75 \text{ s}$$

What is  $V_C$  after  $5.0 \text{ s}$ ?

$$V_C = \mathcal{E} (1 - e^{-t/\tau})$$

$$= (12 \text{ V}) (1 - e^{-1.82})$$

$$= (12 \text{ V}) (1 - 0.162)$$

$$= 10.1 \text{ V}$$

16.2% left

⑥

What  $R$  if  $V_c = 5.0 \text{ V}$  @  $t = 5.0 \text{ s}$

$$V_c = \mathcal{E} (1 - e^{-t/\tau})$$

$$5.0 = 12 (1 - e^{-t/\tau})$$

$$\frac{5}{12} = 1 - e^{-t/\tau}$$

$$e^{-t/\tau} = 1 - \frac{5}{12} = \frac{7}{12} = 0.5833$$

$$-\frac{t}{\tau} = \ln(0.5833) = -0.539$$

$$\tau = 0.539 \tau$$

Now plug in known  $\tau$ :


$$\tau = \frac{5.0}{0.539} = 9.28 \text{ s}$$

$$\tau = RC$$

$$R = \frac{\tau}{C} = \frac{9.28}{250 \times 10^{-6}} = 37100 \Omega$$

$$= 37.1 \text{ k}\Omega$$

⑦

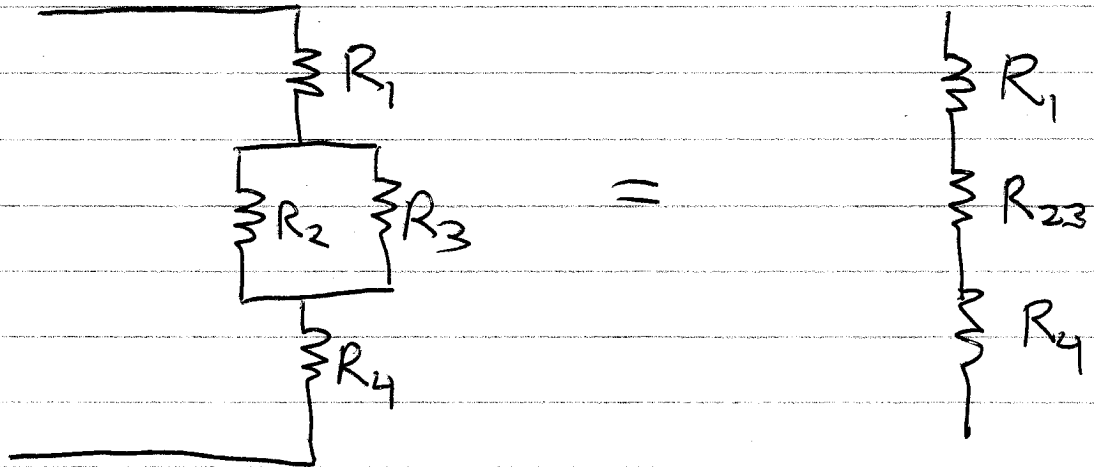

Parallel Equiv:  $R_{23} = \left( \frac{1}{R_2} + \frac{1}{R_3} \right)^{-1}$

$$V_2 = V_3 = V_{23}$$

When substituting a parallel equiv.,  
the voltage transfers back.

V      I      R      P

R<sub>1</sub>

R<sub>2</sub>

R<sub>3</sub>

R<sub>4</sub>

Overall

R<sub>23</sub>