


① Phys 2426

2017-07-20

Lec 11

Hooking up a voltmeter in series,

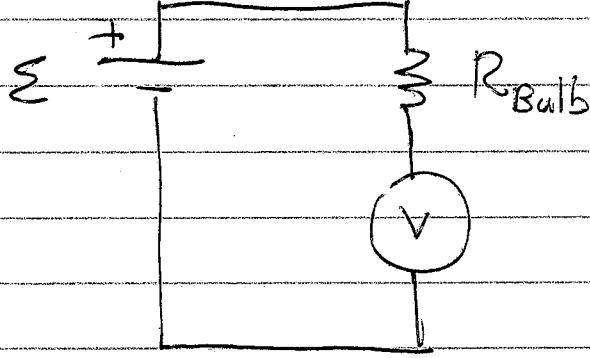- A voltmeter blocks current,
- In series, $I_1 = I_2 = \dots$




$$R_{eq} = R_B + R_V = \infty$$

$$I = 0$$

(Bulb is off.)

$$\mathcal{E} + \cancel{\Delta V_{Bulb}} + \Delta V_{meter} = 0$$

②

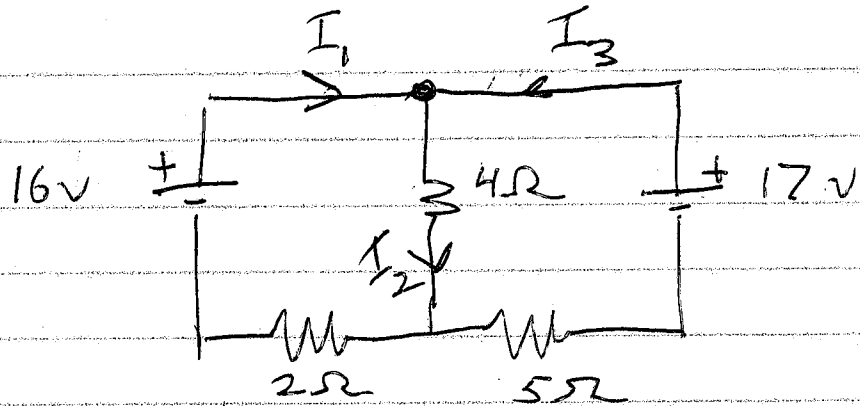

Klunky schematic drawing.
 Roger's Online Equation Editor

$$I_1 + I_3 = I_2$$

Left Loop: $+ (16V) - 4I_2 - 2I_1 = 0$
 ↻

Right Loop: $+ (17) - 4I_2 - 5I_3 = 0$
 ↻

$$I_1 = 2A \quad \leftarrow \#23$$

$$I_3 = 1A$$

$$I_2 = 3A$$

#21 Subtract two loops, i.e. Outer Loop CW

#9: $R = \frac{\rho l}{A}$

Initially: All 1's

$$\text{Final: } R = \frac{1 \left(\frac{1}{2} \right)}{\left(\frac{1}{2} \right)^2} = 2$$

3

$$R_1 = \frac{\rho l_1}{\pi r_1^2}$$

$$R_2 = \frac{\rho l_2}{\pi r_2^2}$$


$$0.4 = \frac{\rho l_1}{\pi r_1^2}$$

$$R_2 = \frac{\rho \frac{1}{2} l_2}{\pi (r_1/2)^2}$$


$$R_2 = \left(\frac{\rho l_2}{\pi r_1^2} \right) \frac{1/2}{(1/2)^2}$$

$$R_2 = (0.4) \left(\frac{4}{2} \right) = 0.8$$
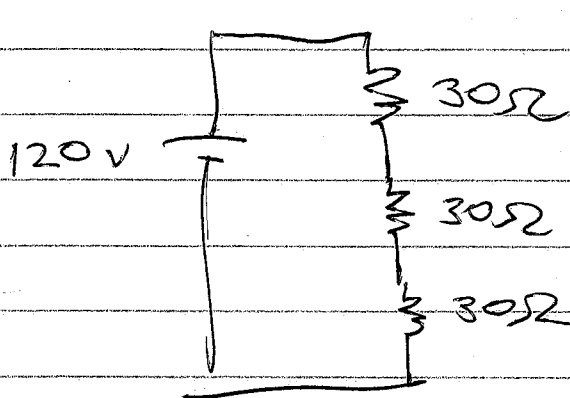
#16 Ammeter hooked up wrong.
• Ammeter allows free flow of current.



$$I = \frac{120V}{90\Omega} = 1.3A$$

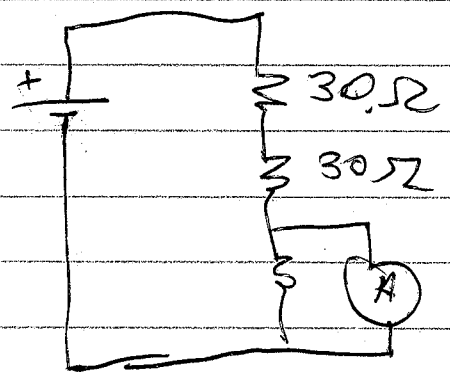

$$I = \frac{120V}{60\Omega} = 2A$$

(4)

#10 Discharging

$$V = V_0 e^{-t/\tau}$$

At 10% of initial, $V = 0.1 V_0$

$$0.1 = e^{-t/\tau}$$

$$\ln(0.1) = -t/\tau$$

$$-\ln(0.1) \tau = t$$

$$-(-2.3) \tau = 2.3 \tau = t$$


5

Lenz's Law

- Coils hate change.
- If there is magnetic flux, and we try to reduce the flux, the coil will try to boost the magnetic field to restore the flux.



Drop the ring.

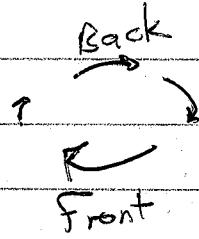

- Flux was downward.
- Field is decreasing.
- EMF tries to push I so B_{ind} is down.


Current in ring will be CW as viewed from top.

Ex: Magnetic braking.

6

Inductors

Recall the Solenoid

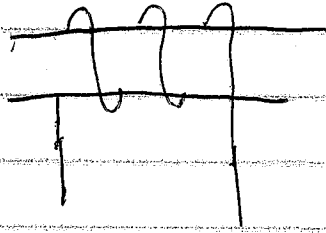

$$B = \mu_0 N I / l$$

$$\Phi_B = N B A$$

↑ Total flux includes factor of N .

Total of all turns

$$\Phi_B = \left(\frac{\mu_0 N^2 A}{l} \right) I$$


$$\Phi_B = L I$$

L = Inductance in henries

$$\mathcal{E} = - \frac{d\Phi_B}{dt} = -L \frac{dI}{dt}$$

\mathcal{E}_{emf} when current changes

Resistor $\Delta V = -IR$

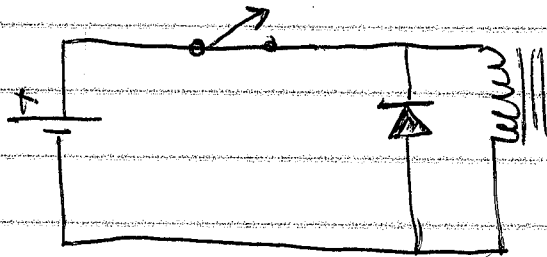

$$\text{Energy} = \frac{1}{2} L I^2$$

$$\text{Cap Energy} = \frac{1}{2} C V^2$$