

1402
p.1

AC Electricity - Why

- Easy to generate
- Works with transformers

Transformer Primary Coil:

- Apply Voltage - gives energy to transformer
- Current flows
- I causes B
- $\Phi = NBA$ is Flux in coil (not per turn)
($\Phi = BA$ is Flux per turn)
- If flux Φ varies EMF is generated
This is "Back EMF", which reduces current.
- $V_{rms} = I_{rms} (\omega)$
↳ High proportionality constant

Secondary


- It "feels" B
- $\Phi_B = NBA$
↳ different N and Φ
- $\mathcal{E} = NBA \omega$ is proportional to N
- Compare: $\frac{\mathcal{E}_s}{\mathcal{E}_p} = \frac{N_s}{N_p}$

1402
p.3

① Phys 1402 2017-07-25 Lec 13

AC Electricity

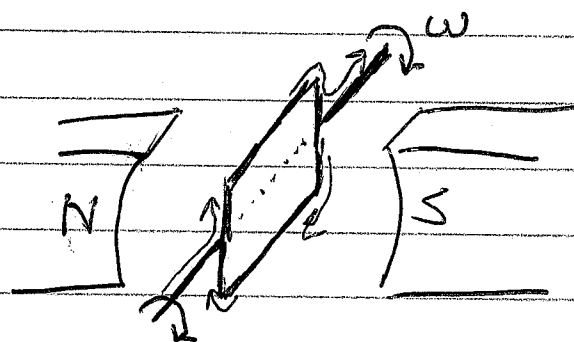Why? Easy to generate.
Works with transformers.




$$\Phi_B = NBA \cos(\omega t)$$

$$\mathcal{E}_{\max} = NBA \omega \quad (\text{Amplitude})$$

$$\mathcal{E} = \mathcal{E}_{\max} \sin(2\pi f t)$$

↑
 $\sin()$ or $\cos()$

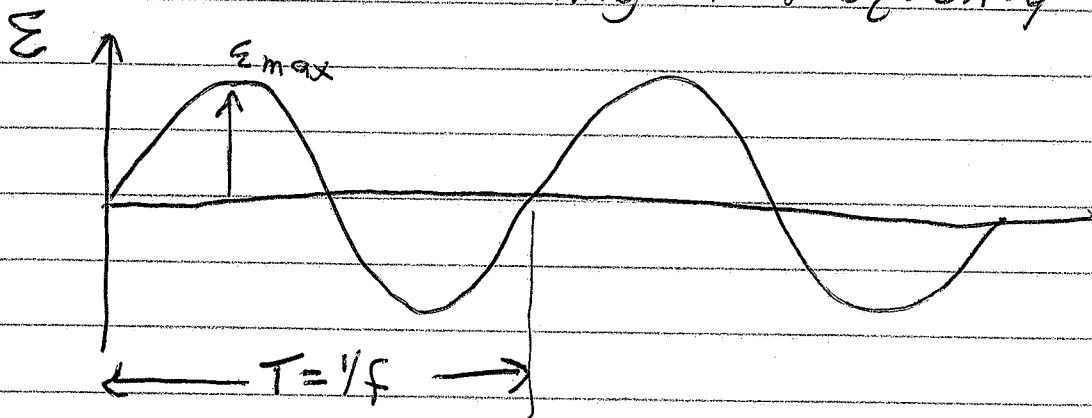$\omega = 2\pi f = \text{angular frequency}$




③

Ratio of \mathcal{E} 's:

$$\frac{\mathcal{E}_s}{\mathcal{E}_p} = \frac{N_s}{N_p}$$

Reminder: If flux isn't changing - no EMF

Side Effect - Isolation

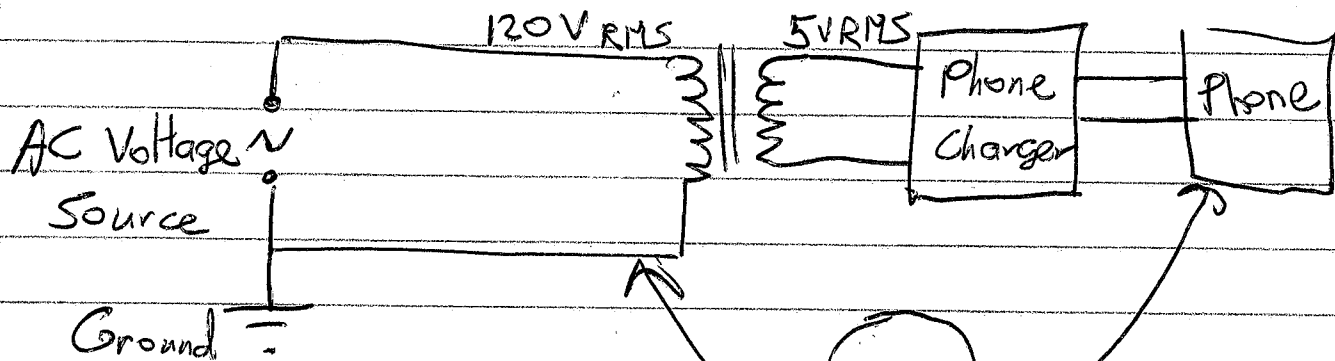

Shouldn't
be a problem

Usually: Phone isolated from ~~charger~~ "Mains"

- Cheap charger?
- Touching plug?
- Damp skin? - makes 120V deadly
- Frayed wires

2

AC Components

Resistor $V = IR$

Let's say $I = I_0 \sin(2\pi ft)$

$$V = I_0 \sin(2\pi ft) R$$
$$= (I_0 R) \sin(2\pi ft)$$

$$V = V_0 \sin(2\pi ft)$$

Convert both to RMS

$$V_{rms} = I_{rms} R$$
$$P_{avg} = I_{rms}^2 R$$

Inductor $V = L \frac{dI}{dt}$


$$V = L I_0 \cos(2\pi ft) 2\pi f$$
$$= I_0 2\pi f L \cos(\quad)$$
$$= V_0 \cos(\quad)$$

$$V_0 = I_0 2\pi f L$$

$$V_{rms} = I_{rms} 2\pi f L$$

$$V_{rms} = I_{rms} X_L$$
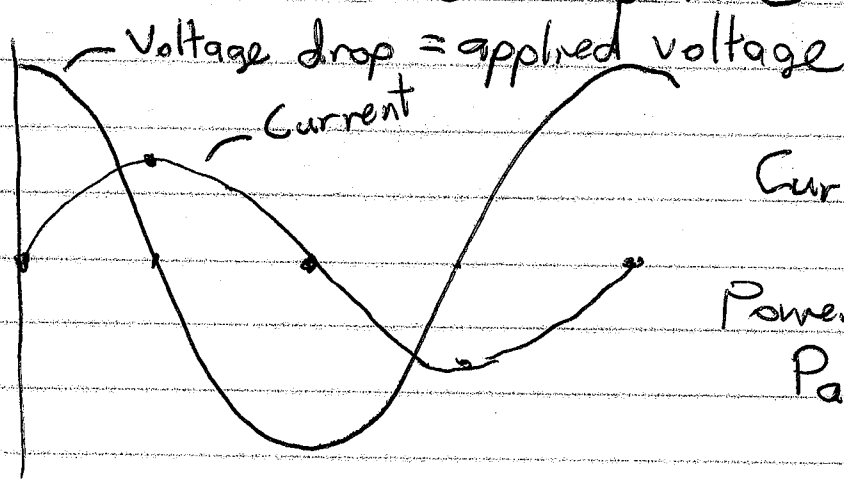
$$X_L = 2\pi f L = \text{inductive reactance}$$



Current "lags"

Power oscillates

$$P_{avg} = 0$$

(3)

Capacitor

$$V = Q/C$$

$$Q = \int I = \int I_0 \sin(2\pi f t) dt$$
$$= \frac{-I_0}{2\pi f} \cos(2\pi f t)$$

$$V = \frac{-I_0}{2\pi f C} \cos(2\pi f t)$$


$$V = V_0 (-\cos())$$

$$V_0 = I_0 \frac{1}{2\pi f C}$$

$$V_{rms} = I_{rms} \frac{1}{2\pi f C}$$

$$X_c = \frac{1}{2\pi f C} = \text{capacitive reactance}$$

$$V_{rms} = I_{rms} X_c$$

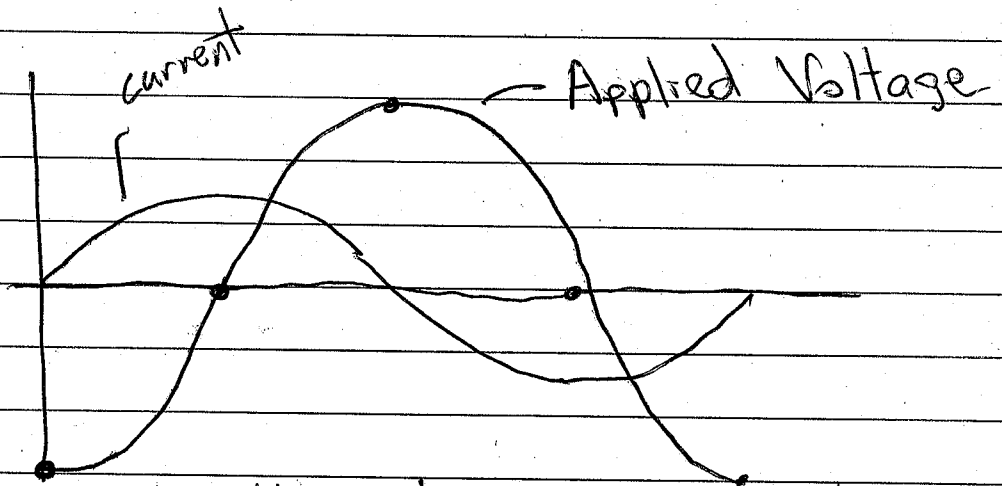

Voltage Lags in capacitor.

+ Current increases Q and V

- current decreases Q and V

$$P_{avg} = 0$$

④

Series AC Circuit

$$I_1 = I_2 = \dots \quad \text{still true}$$

$$V_{\text{Tot}} = V_1 + V_2 + \dots \quad \text{true as function of time}$$

$$V_{\text{Tot}} = V_{R0} \sin() + V_{L0} \cos() - V_{C0} \cos()$$

To do this without trig, Add Impedances as vectors.

$$\text{Resistor: } Z_R = R \hat{x}$$

$$\text{Inductor: } Z_L = X_L \hat{y}$$

$$\text{Capacitor: } Z_C = X_C (-\hat{y})$$

$$\text{Total } \hat{x}: R$$

$$\text{Total } \hat{y}: X_L - X_C$$

$$\text{Total magnitude: } Z = \sqrt{R^2 + (X_L - X_C)^2}$$

⑤

Ex: $R = 1.0 \text{ k}\Omega$ $L = 1.0 \text{ H}$ $C = 1.0 \mu\text{F}$
In series

Apply $V = 140 \sin(500t)$

Want to use: $V_{\text{rms}} = I_{\text{rms}} Z$

$$V_{\text{rms}} = \frac{140}{\sqrt{2}} = 99 \text{ V}$$

$$2\pi f = 500 \quad f = \frac{500}{2\pi} \approx 160 \text{ Hz}$$

$$X_L = 2\pi f L = (500)(1.0) = 500 \Omega$$

$$X_C = \frac{1}{2\pi f C} = \frac{1}{500 \times 10^{-6}} = 2000 \Omega$$

$$X_L - X_C = -1500 \Omega = 1500 \Omega \text{ capacitive}$$

$$Z = \sqrt{1000^2 + 1500^2} = 1803 \Omega$$

$$I_{\text{rms}} = \frac{99 \text{ V}}{1803 \Omega} \approx 0.0549 \text{ A}$$

Other calculations:

Power Used: $P = I_{\text{rms}}^2 R$
 $= 3.02 \text{ W}$

Not $V_{\text{rms}} I_{\text{rms}} = (99 \text{ V})(0.0549 \text{ A}) = 5.44 \text{ VA}$

Capacitor Voltage: $V_{\text{rms}} = (0.0549 \text{ A})(2000 \Omega)$
 $= 110 \text{ V}$

Bigger than applied voltage!

⑥

Resonance

$$X_L = X_C$$

At resonance, $Z = R$

- This is the minimum possible Z .

- Happens at $f_R = \frac{1}{2\pi\sqrt{LC}}$

- At any other f , Z is larger and less current flows.